



Contents

1	(Overview				
	1.1	Description0				
	1.2	2 Features 0				
	1.3	Applications0				
2	F	Reference Design				
	2.1	Block Diagram				
	2.2	2 Related Solutions				
	2.3	3 System Specifications				
3	0	Design				
	3.1	Schematics04				
	3.2	2 BOM				
	3.3	9 PCB Layout				
4	Г	Test Results10				
	4.1	Efficiency and Regulation				
	4.2	2 Time Domain Waveforms 11				
	4.3	3 Thermal Measurements				
	4.4	EMC Measurements 14				
5	S	art-Up15				
6	F	Frequency Spread Spectrum				
7	D	Disclaimer				



1 Overview

1.1 Description

New automotive designs are adopting 48V power systems to reduce the weight and power loss in the vehicle's cable harnesses. However, this presents a challenge when trying to comply with EMC regulations. Success is achievable with thoughtful component placement regarding PCB layout, as well as techniques such as frequency spread spectrum (FSS).

This reference design showcases a 12V to 48V buck converter that is capable of delivering 15A of current while complying with Class 5 CISPR-25 EMC standards.

1.2 Features

- Wide 4V to 60V Operating Input Range
- Dual N-Channel MOSFET Driver
- 0.8V Reference Voltage with ±1.5% Accuracy Over-Temperature
- Low-Dropout Operation: Maximum Duty Cycle at 99.5%
- Configurable Frequency Range: 100kHz
 to 1000kHz
- External Sync Clock Range: 100kHz to 1000kHz
- 180° Out-of-Phase SYNCO Pin
- Configurable Soft Start (SS)
- Power Good (PG) Output Voltage Monitor
- Selectable Cycle-by-Cycle Current Limit
- Output Over-Voltage Protection (OVP)
- Over-Current Protection (OCP)
- Internal LDO with External Power Supply
 Option
- Configurable Forced CCM and AAM
- External Frequency Spread Spectrum (FSS) Modulation
- External Input Over-Voltage Protection (OVP)
- External Reverse-Polarity Protection (RPP)
- Available in TSSOP20-EP and QFN-20 (3mmx4mm) Packages
- Available in a Wettable Flank Package
- AEC-Q100 Qualified

1.3 Applications

- Automotive Power Systems
- Industrial Systems





All MPS parts are lead-free and adhere to the RoHS directive. For MPS green status, please visit the MPS website under Quality Assurance. "MPS", the MPS logo, and "Simple, Easy Solutions" are registered trademarks of Monolithic Power Systems, Inc. or its subsidiaries.



2 Reference Design

2.1 Block Diagram



Figure 1: Block Diagram

Buck converter with 48V nominal input, 12V/15A output capability, input EMI filter, reverse-polarity protection (RPP), over-voltage protection (OVP), and frequency spread spectrum (FSS) modulation.

2.2 Related Solutions

This reference design is based on the following MPS solutions:

Table 1: MPS Solutions

MPS Integrated Circuit	Description
<u>MPQ2908A</u>	4V to 60V input, current mode, synchronous step-down controller, AEC-Q100 qualified

2.3 System Specifications

Table 2	System	Specifications
---------	--------	----------------

Parameter	Specification
Input voltage range	18VDC to 60VDC
Output voltage	12VDC
Maximum output current	15A (with 12V output)
Switching frequency	430kHz
Board form factor	94mmx78mmx12mm
Peak efficiency	94.2%
12V output ripple	22mV _{P-P}



3 Design

3.1 Schematics



Figure 2: Schematics (Sheet 1)



Figure 3: Schematics (Sheet 2)



MPQ2908 Reference Design 48V Buck Converter for Automotive Systems



Figure 4: Schematics (Sheet 3)



3.2 BOM

Table 3: MPQ2908 Bill Of Materials

Designator	Qty	Value	Package	Part Number	Manufacturer
C1, C2, C7	3	2.2µF, 100V	1206	CGA5L3X7S2A225K160AB	TDK
C3, C4, C9A, C9B, C9C, C9D, C10A, C10B	8	4.7µF, 100V	1210	C3225X7S2A475M200AB	TDK
C5	1	47µF, 100V	10mmx 10mm	EMVE101ADA470MJA0G	United Chemi-Con
C6	1	22nF, 100V	1206	C1206C223K1RECAUTO	KEMET
C8, C11A, C11B, C14, C15	5	100nF, 100V	0603	GCJ188R72A104KA01D	Murata
C9	1	1µF, 16V	0603	GCM188R71C105KA64J	Murata
C10	1	6.8nF, 16V	0603	VJ0603Y682KXJCW1BC	Vishay Vitramon
C10C, C10D	2	NS	1210	C3225X7S2A475M200AB	TDK
C11, C12	2	100nF, 16V	0603	C0603X104J4RECAUTO	KEMET
C13	1	1µF, 100V	0805	GCM21BC72A105KE36L	Murata
C16	1	220nF, 100V	0805	C0805C224K1RACTU	KEMET
C17	1	4.7µF, 16V	0603	GRM188R61C475KAAJD	Murata
C18, C19, C20, C21	4	22µF, 25V	1210	GRM32ER61E226KE15L	Murata
C22	1	22pF, 25V	0603	06033A220JAT2A	Kyocera AVX
C23	1	1µF, 25V	0603	CC0603KRX5R8BB105	Yageo
C24	1	10nF, 16V	0603	C0603C103M3RACTU	KEMET
C25, C29	2	NS	0805		
C26, C27	2	NS	0603		
C28	1	1nF, 16V	0603	CC0603JRNPO8BN102	Yageo
C31	1	NS	0805	GCJ188R72A104KA01D	Murata
D1, D3, D5, D6	4	1N4148	SOD-323	1N4148WSQ-7-F	Diodes
D2	1	10V Zener	SOD-523	BZT585B10T-7	Diodes
D4	1	65V Zener	SOT-23	SZBZX84C62LT1G	ON Semiconductor
D7	1	PMEG6010CEJ	SOD-323	PMEG6010CEJ,115	Nexperia
D8	1	RB168MM150TFTR	SOD-123	RB168MM150TFTR	Rohm
J1, J2, J3, J4	4	74650073R		74650073R	Wurth Electronics
L1, L2	2	2.2μH, 8A, 20mΩ	7030	HCMA0703-2R2-R	Eaton
L3	1	6.8μH, 26A, 4.17mΩ	1510	XAL1510-682MEB	Coilcraft
L4, L5	2	0.33μH, 19.2A, 3.52mΩ	5030	XAL5030-331MEC	Coilcraft



MPQ2908 Reference Design 48V Buck Converter for Automotive Systems

Q1, Q2	2	SQJA80EP	PowerPAK- SO-8L-4	SQJA80EP-T1_GE3	Vishay
Q3	1	SBC846BLT1G	SOT-23-3	SBC846BLT1G	ON Semiconductor
Q4, Q5	2	SQJA82EP-T1_GE3	PowerPAK- SO-8L-4	SQJA82EP-T1_GE3	Vishay
R1, R5, R19	3	1kΩ, 5%	0603	RC0603JR-071KL	Yageo
R2, R6, R9	3	100Ω, 5%	0603	RC0603JR-07100KL	Yageo
R3, R4	2	20Ω, 5%	0603	RC0603JR-0720KL	Yageo
R7	1	2.2Ω, 5%	0603	ERJ-3GEYJ2R2V	Panasonic
R8	1	3mΩ, 1%	2512	PA2512FKF7W0R003E	Yageo
R10	1	45.3kΩ, 1%	0603	CR0603-FX-4532ELF	Bourns
R11	1	84.5kΩ, 0.5%	0603	ERJ-PB3D8452V	Panasonic
R12	1	6.04kΩ, 1%	0603	ERJ-3EKF6041V	Panasonic
R13	1	33kΩ, 1%	0603	ERJ-3EKF3302V	Panasonic
R14, R18	2	NS	0603	RC0603JR-070RL	Yageo
R15, R16, R22	3	0Ω, 5%	0603	RC0603JR-070RL	Yageo
R17	1	10Ω, 5%	0805	ERJ-P06J101V	Panasonic
R20	1	NS	0603	ERJ-3GEYJ103V	Panasonic
R21	1	11kΩ, 5%	0603	ERJ-3GEYJ113V	Panasonic
U1	1	MPQ2908A	TSSOP- 20EP	MPQ2908AGF-AEC1	MPS
U2	1	TLC555QDRQ1	SOIC-8	TLC555QDRQ1	Texas Instruments



3.3 PCB Layout



Figure 5: PCB Layer 1



Figure 6: PCB Layer 2





Figure 7: PCB Layer 3



Figure 8: PCB Layer 4



4 Test Results

4.1 Efficiency and Regulation

V_{OUT} = 12V, L = 6.8µH, f_{sw}= 400kHz, CCM, copper thickness = 35µm, T_A = 25°C.

Figure 9: Efficiency vs. Load Current With OVP and EMI filter



Figure 11: Line Regulation

With OVP and EMI filter, measured at output connector







Figure 10: Load Regulation Without OVP and EMI filter



Figure 12: Line Regulation

With OVP and EMI filter, measured at output capacitor





Time Domain Waveforms

V_{IN} = 48V, V_{OUT} = 12V, L = 6.8µH, T_{A} = 25°C, CCM.



Figure 16: Start-Up through V_{IN} I_{OUT} = 0A





RD00002 Rev. 0.8

2/10/2020







MPS Proprietary Information. Patent Protected. Unauthorized Photocopy and Duplication Prohibited. © 2020 MPS. All Rights Reserved.

















MPQ2908 Reference Design 48V Buck Converter for Automotive Systems



4.2 Thermal Measurements

 V_{IN} = 48V, V_{OUT} = 12V, L = 6.8µH, f_{SW} = 400kHz T_A = 25°C, CCM mode, no airflow.

Figure 28: Thermal Image



Figure 29: MOSFET Case Temperature: 123°C I_{OUT} = 15A, heatsink mounted, 2hr runtime





4.3 EMC Measurements

 $V_{IN} = 48V$, $V_{OUT} = 12V$, $I_{OUT} = 15A$, $L = 6.8\mu$ H, $C_{OUT} = 88\mu$ F, $f_{SW} = 400$ kHz, $T_A = 25^{\circ}$ C, FSS activated.





5 Start-Up

- 1. Connect the load to:
 - a) Positive (+): VOUT
 - b) Negative (-): GND
- 2. Set the load current between 0A and 15A. Be aware that electronic loads represent a negative impedance to the regulator, and will trigger over-current protection or short-circuit protection if set to an exceedingly high current.
- 3. Preset the output power supply between 24V and 60V, then turn off the power supply.
- 4. Connect the power supply terminals to:
 - a) Positive (+): VIN
 - b) Negative (-): GND
- 5. Turn the power supply on. The board should automatically start up. The default V_{OUT} is 12V.
- 6. The external resistor dividers (R11 and R12) set the output voltage. If $V_{OUT} = 12V$, R11 and R12 must be 84.5k Ω and 6.04k Ω , respectively. R11 and R12 can be calculated with Equation (1):

$$R_{12} = \frac{R_{11}}{\frac{V_{out}}{0.8} - 1} \tag{1}$$

7. If the part is working at high V_{IN} and f_{SW} , ensure the junction temperature (T_J) of the high-side MOSFET does not exceed 175°C.



6 Frequency Spread Spectrum

Most switch-mode power supplies (SMPS) will generate a lot of noise when working from 48V systems. This board has an optional frequency spread spectrum (FSS) modulation feature that can be used to improve its EMC performance when the device fails to comply with EMC regulations by a few dB.

FSS makes the switching power supply commute on several side bands around its fundamental switching frequency, instead of having just one fixed frequency. This side bands are created by modulating the switching frequency with a triangle modulation waveform. The emission power of the fundamental switching frequency and its harmonics is distributed into smaller pieces, which significantly reduces peak EMI noise.

FSS is especially effective in reducing the noise level during low-frequency operation, and its effect decreases as the measurement frequency increases.

MPS has conducted an in-depth webinar on FSS, explaining how it works, and what improvements can be expected from FSS. For more information, view the full webinar at this link: <u>https://www.monolithicpower.com/en/support/webinars.html</u>.

To enable FSS modulation, the following components on the board must be modified:

- Mount a 0Ω 0603 resistor on R18
- Mount a 10kΩ 0603 resistor on R20
- Mount a 100nF 0603 capacitor (with a voltage rating of at least 6.3V) on C26
- Remove R22 and replace it with a $1k\Omega$ 0603 resistor

To disable FSS, revert these changes.



7 Disclaimer

Monolithic Power Systems (MPS) reserves the right to make changes to its products and to discontinue products without notice. The applications information, schematic diagrams, and other reference information included herein is provided as a design aid only and are therefore provided as-is. MPS makes no warranties with respect to this information and disclaims any implied warranties of merchantability or non-infringement of third-party intellectual property rights.

MPS cannot assume responsibility for use of any circuitry other than circuitry entirely embodied in an MPS product. No circuit patent licenses are implied.

Certain applications using semiconductor products may involve potential risks of death, personal injury, or severe property or environmental damage ("Critical Applications").

MPS PRODUCTS ARE NOT DESIGNED, INTENDED, AUTHORIZED, OR WARRANTED TO BE SUITABLE FOR USE IN LIFE SUPPORT APPLICATIONS, DEVICES OR SYSTEMS, OR OTHER CRITICAL APPLICATIONS.

Inclusion of MPS products in critical applications is understood to be fully at the risk of the customer.

Questions concerning potential risk applications should be directed to MPS.

MPS semiconductors are typically used in power supplies in which high voltages are present during operation. High-voltage safety precautions should be observed in design and operation to minimize the chance of injury.

Notice: The information in this document is subject to change without notice. Users should warrant and guarantee that thirdparty Intellectual Property rights are not infringed upon when integrating MPS products into any application. MPS will not assume any legal responsibility for any said applications.