



Using a Microcontroller to Adjust the MP2759's Charging Current

Application Note

Prepared by
MPS Battery Management Product Line

March 2020

TABLE OF CONTENTS

Table of Contents	1
Abstract.....	2
1. Introduction	3
2. Method Details	3
2.1 Method Overview	4
2.2 Parameters-Related Design Guide	5
3. Design Example.....	5
3.1 Design Process	5
3.2 Design Results	5
4. Conclusion	7
5. Additional Reading.....	7

ABSTRACT

To fine-tune their performance, many battery-powered devices must adjust the charging current in real time under different operating modes. For example, many battery manufacturers require specific charging current levels for different temperatures to guarantee battery safety. Although the MP2759 has JEITA to adjust the charging current, an microcontroller (MCU) provides enhanced user configuration.

The MP2759 can regulate its charging current with a resistor (R_{ISET}) connected between the ISET pin and AGND. This application note details how to adjust the MP2759's charging current in real time with an MCU, based on the charging current regulation. This application note describes the MP2759, and addresses the relationship between R_{ISET} and the charging current. Next, this note recommends a design guide for charging current real-time adjustment, and lastly provides a design example.

1. INTRODUCTION

The MP2759 is a highly integrated switching charger designed for applications with 1-cell to 6-cell series Li-ion or Li-polymer battery packs. It supports several battery chemistries with different battery regulation voltages. The charging current can be regulated by connecting a corresponding resistor (R_{ISET}) between the ISET pin and AGND. The relationship between R_{ISET} and the charging current can be calculated with Equation (1):

$$I_{CHG} = \frac{96(k\Omega)}{R_{ISET} (k\Omega)} \quad (1)$$

Although the charging current can be adjusted with R_{ISET} , this method is unreliable for real-time regulation. By using the PWM of an MCU, the charging current can be adjusted in real time with greater reliability. Figure 1 shows the standard schematic for the MP2759.

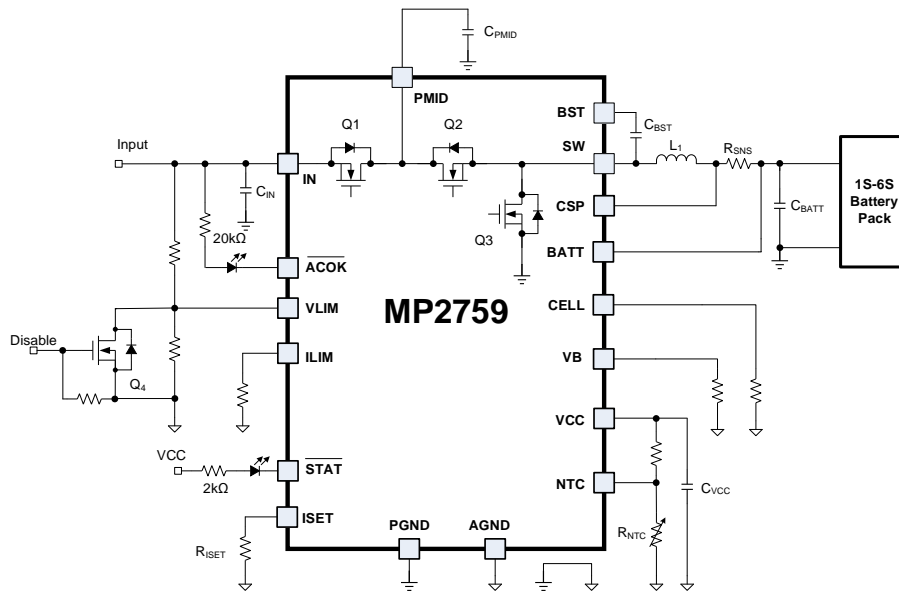


Figure 1: MP2759 Application Schematic

2. METHOD DETAILS

The MP2759 regulates the charging current with different resistor values read by the ISET pin. The ISET pin maintains a constant voltage of 1.2V, meaning the charging current can be adjusted by changing the equivalent resistor between the ISET pin and AGND. This change can be initiated by modifying the MCU's PWM duty cycle.

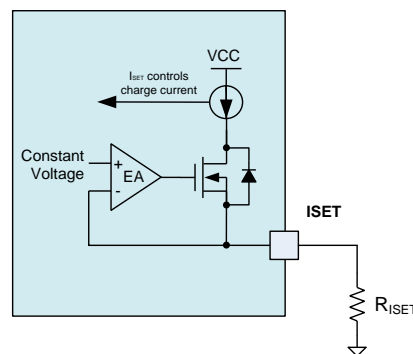


Figure 2: Equivalent Circuit of the ISET Pin

2.1 Method Overview

Figure 3 shows how to build a design when the equivalent resistor is connected to the MP2759's ISET pin.

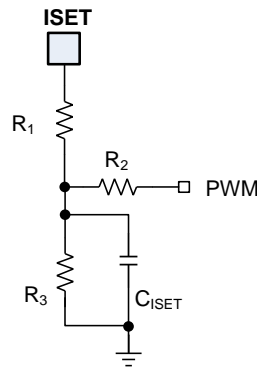


Figure 3: Equivalent Resistor Design Circuit

The PWM signal has a controllable duty cycle. This signal is generated by an MCU. The RC filter (consisting of R_2 , R_3 , and C_{ISET}) filters the PWM signal to the DC signal. The equivalent resistance (R_{EQ}) between the ISET pin and AGND can be calculated with Equation (2):

$$R_{EQ} = \frac{1.2R_1G_{123}}{1.2G_{123} - \left(\frac{DUTY \times V_{M_PWM}}{R_2} + \frac{1.2}{R_1} \right)} \quad (2)$$

Where DUTY is the PWM duty cycle, and V_{M_PWM} is the PWM amplitude (the same as the MCU supply voltage, which is about 3.3V). G_{123} can be estimated with Equation (3):

$$G_{123} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \quad (3)$$

For Equations 1, 2, and 3, R_{EQ} must exceed 0Ω . When R_{EQ} falls below 0Ω , $I_{CHG} = 0A$. Table 1 lists the charging current based on the PWM input.

Table 1: Charging Current vs. PWM Input

PWM Input	PWM Duty	Charging Current
GND	0%	Max charging current
Logic high	100%	0A
PWM duty cycle	0% to MAX_DUTY ⁽¹⁾	Linearly adjust charging current
Float	N/A	$96(k\Omega)/(R_1+R_3)$

Note:

1) MAX_DUTY is the maximum PWM duty when the charging current falls to 0A. It is recommended to be about 80%.

2.2 Parameters-Related Design Guide

Based on the analysis above, the parameters (R_1 , R_2 , R_3 , C_{ISET}) can be designed with the following guidelines:

- The equivalent resistor that corresponds to the max charging current is R_{MAX_ICHG} , which can be calculated with Equation (4):

$$R_{\text{MAX_ICHG}} = R_1 + R_2 // R_3 \quad (4)$$

- Choose an appropriate R_1 , estimated with Equation (5):

$$R_1 = 0.5 R_{\text{MAX_ICHG}} \quad (5)$$

- Solve the equations, then calculate R_2 and R_3 with Equation (6):

$$\begin{cases} R_2 // R_3 = R_{\text{MAX_ICHG}} - R_1 \\ \frac{\text{MAX_DUTY} \times V_{\text{M_PWM}} - 1.2}{R_2} = \frac{1.2}{R_3} \end{cases} \quad (6)$$

- Choose an appropriate C_{ISET} to filter the PWM signal to DC signal, estimated with Equation (7):

$$\frac{1}{2\pi(R_2 // R_3)C_{\text{ISET}}} \ll f_{\text{PWM}} \quad (7)$$

Where f_{PWM} is the PWM frequency.

3. DESIGN EXAMPLE

This section demonstrates how to successfully design the parameters to adjust the charging current in real time when $\text{MAX_ICHG} = 2.7\text{A}$, $\text{MAX_DUTY} = 80\%$, $V_{\text{M_PWM}} = 3.3\text{V}$, and $f_{\text{PWM}} = 2\text{kHz}$.

3.1 Design Process

- Calculate $R_{\text{MAX_ICHG}}$ using Equation (8):

$$R_{\text{MAX_ICHG}} = \frac{96(\text{k}\Omega)}{\text{MAX_ICHG}} = 35\text{k}\Omega \quad (8)$$

- Choose $R_1 = 20\text{k}\Omega$.
- Use Equation (6) to calculate $R_2 = 33\text{k}\Omega$, and $R_3 = 27\text{k}\Omega$.
- Set $C_{\text{ISET}} = 1\mu\text{F}$ to filter the PWM signal to the DC signal.

3.2 Design Results

Build a demo board with the parameters determined above to verify the effectiveness of the method proposed in this application note. Figure 4 shows the demo board schematic.

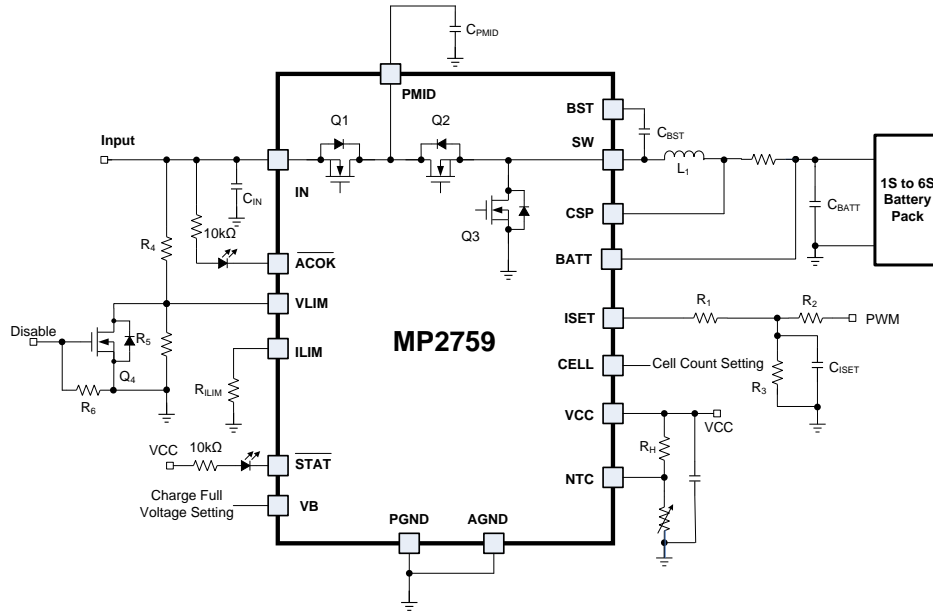


Figure 4: MP2759 Charging Current Adjustment Application Demo Board Schematic

According to the results obtained after testing the demo board (under the test conditions: $V_{IN} = 16V$, $V_{BATT} = 12V$, $V_{M_PWM} = 3.3V$, and $f_{PWM} = 2kHz$), there is a linear relationship between the charging current and the PWM duty cycle, and the duty cycle offers a wide range of 0% to 82%. (see Figure 5).

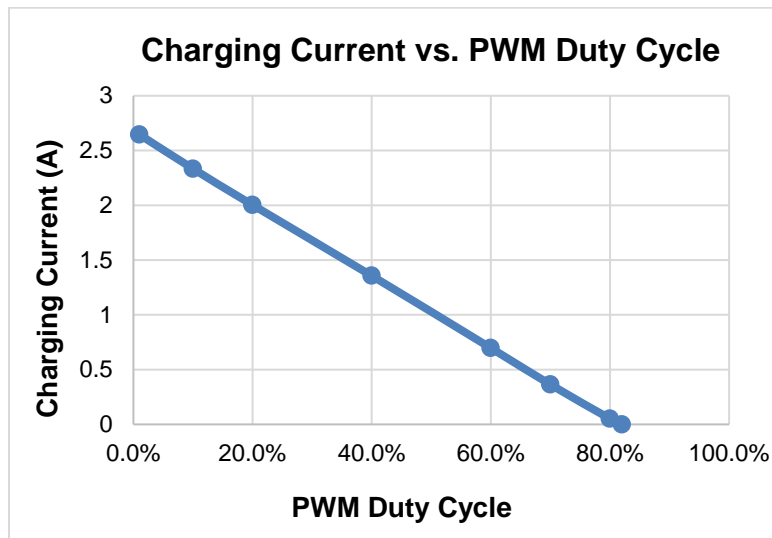


Figure 5: Charging Current vs. PWM Duty Cycle

The MP2759 does not experience overshoot or undershoot when the charging current changes (see Figure 6). In addition, the device demonstrates normal start-up and shutdown (see Figure 7).

All the test results offer evidence supporting the effectiveness of the design method introduced in this application note.



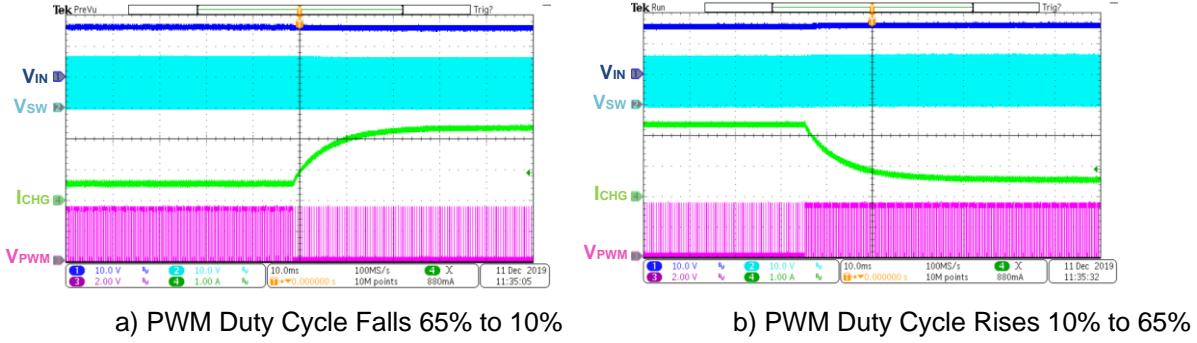


Figure 6: Charging Current Transition between 0.5A and 2.4A

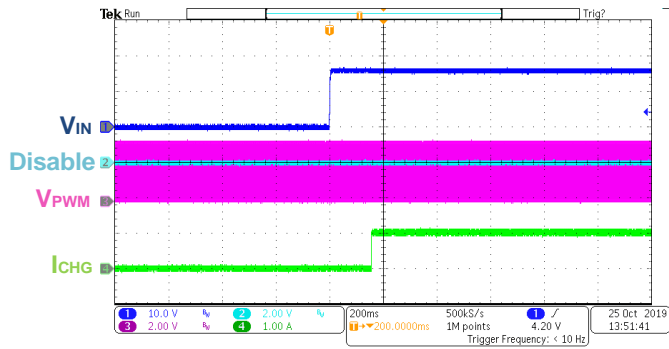

VIN Start-Up

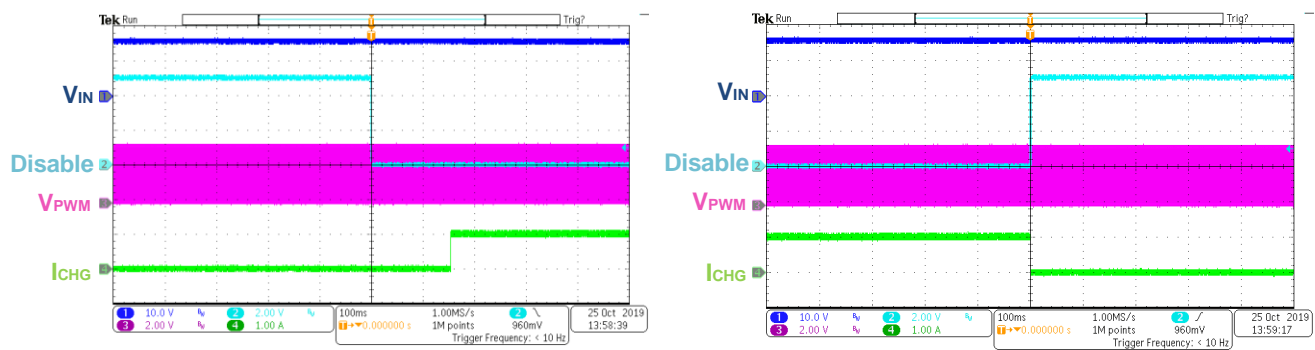

Charge Enable

Charge Disable

Figure 7: Waveforms of MP2759 On/Off Application (Duty = 50%)

4. CONCLUSION

Charging performance can be optimized with an adjustable charging current. The application note proposed a method to adjust the MP2759’s charging current in real time with an MCU. A design example was provided, as well as test results to prove the validity of this current-charging method.

5. ADDITIONAL READING

For more information about MPS battery management products, please visit the following link:

<https://www.monolithicpower.com/en/products/battery-management.html>

NOTICE: The information in this document is subject to change without notice. Users should warrant and guarantee that third party Intellectual Property rights are not infringed upon when integrating MPS products into any application. MPS will not assume any legal responsibility for any said applications.