



AN183

**Designing an Isolated Gate Driver Power
Supply with LLC Topology**

Designing an Isolated Gate Driver Power Supply with LLC Topology

Application Note

Prepared by Ao Sun

March 2022

ABSTRACT

Unregulated flyback converters and push-pull converters are typically used for isolated gate driver power supply applications, which require a tightly coupled transformer to reduce power loss caused by the inductance leakage. Modern high-power systems often have a higher bus voltage (V_{BUS}) and dV/dt at the switching nodes. A higher isolation voltage ($V_{ISOLATION}$) rating and lower interwinding capacitance are required for transformer design; however, these cannot be achieved on a tightly coupled transformer.

Resonant topology is an ideal solution for this issue. It utilizes the inductance leakage, which allows for a loosely coupled transformer. The advantages of resonant topology include reduced interwinding capacitance and transformer size, as well as high efficiency and improved load regulation.

AN183 provides a step-by-step design guide for a low-cost LLC converter. This converter is designed for isolated gate drivers in IGBT and Si/SiC MOSFET devices. The design is ideal for automotive and industrial applications, including electric vehicle motor drivers, onboard chargers, and grid-tied inverters.

ISOLATED GATE DRIVER POWER SUPPLY DESIGN WITH LLC TOPOLOGY

A half-bridge primary-side MOSFET and half-bridge secondary-side rectifier are preferred for low-power applications, as they require fewer switches and diodes. The LLC converter design employs a transformer (T_1), magnetizing inductance (L_m), and inductance leakage (L_{l1} , L_{l2}). The resonant capacitor (C_r) and the inductance leakage form an LC resonant tank. Selecting a switching frequency (f_{sw}) similar to the resonant tank's frequency (f_r) keeps the resonant tank impedance at about 0Ω . If the LLC converter has a conversion ratio equal to the transformer turns ratio ($1:N$ of T_1), then the LLC converter can operate as a DC transformer. Empirically, this statement holds true so long as $L_m > 10 \times L_{l1}$. In cases where L_m is comparable to L_{l1} , the conversion ratio exceeds the transformer turns ratio (N) and becomes $N(1 + \frac{L_{l1}}{L_m})$.

Figure 1 shows an LLC topology scheme.

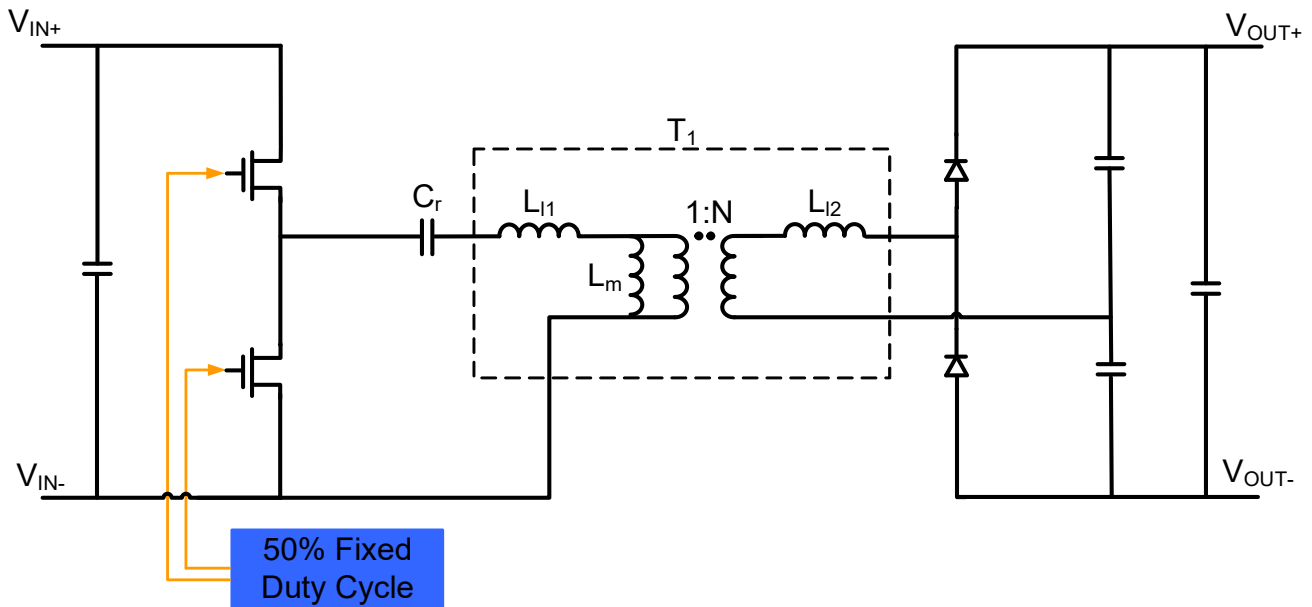


Figure 1: LLC Topology Scheme

1. MPS Gate Drive Power Supply Solution Using LLC Topology

The LLC converter design employs the MPQ18913 as a half-bridge transformer driver. It features a high f_{sw} and a wide input voltage (V_{IN}) range for system design flexibility. Figure 2 shows the gate driver power supply design schematic for a SiC device.

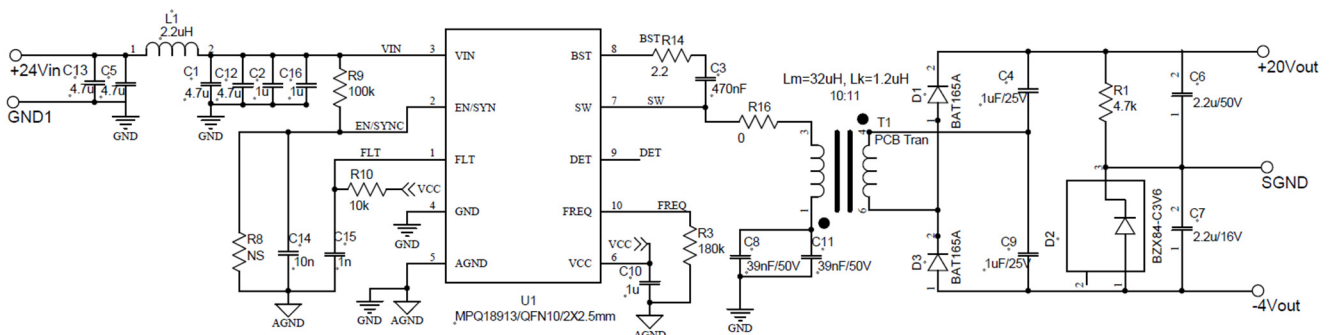


Figure 2: Gate Driver Power Supply Design Schematic for a SiC Device

A Zener diode splits the output voltage (V_{OUT}) into two rails, which can be used for suitable for a IGBT or SiC driver.

Table 1 shows the component selection and equations for the LLC converter using the MPQ18913.

Table 1: Design Equations and Component Selection for the LLC Converter

Parameter	Equation and Description	Notes
Switching frequency (f_{sw})	$f_{sw} = \begin{cases} 0.5\text{MHz} - 0.75\text{MHz}, P_{out} < 6\text{W} \\ 0.75\text{MHz} - 2\text{MHz}, P_{out} < 3\text{W} \\ 1.5\text{MHz} - 5\text{MHz}, P_{out} < 2\text{W} \end{cases} \quad (1)$ <p>A higher f_{sw} has larger transformer winding AC resistance, which limits the output power.</p>	MPQ18913 $f_{sw} = 5\text{MHz}$
Transformer magnifying inductance (L_m)	$L_m \leq \frac{\text{Dead Time}}{8 \times C_{oss} \times f_{sw}} = \frac{25\text{ns}}{8 \times 0.15\text{nF} \times f_{sw}} \quad (2)$ <p>This L_m guarantees the zero-voltage switching (ZVS) of the primary switches.</p>	See the Transformer Design section for more details on the design of T_1 .
Rectification diodes (D1 and D3)	$I_{PEAK} = \pi \times I_{OUT} \quad (3)$ <p>Use Schottky diodes to minimize switching losses and achieve ZVS.</p>	The recommendation of D1 and D3 will be shown in section 3
Output capacitors (C6 and C7)	$C_6 = C_7 \geq \frac{Q_g}{V_{RIPPLE}} \quad (4)$ <p>Where Q_g is the gate charger of the powered device (e.g. SiC or IGBT), and V_{RIPPLE} is the maximum voltage ripple.</p>	If C6 and C7 should be $>22\mu\text{F}$, then choose the MPQ18913A for the design in place of the MPQ18913.
Frequency-setting resistor (R3)	$R_3 = \frac{100\text{k}\Omega}{f_{sw}(\text{MHz})} \quad (5)$	
Resonant Capacitor (C_r)	$C_r = \frac{1}{4 \times \pi^2 \times (2 \times L_{l1}) \times f_{sw}^2} \quad (6)$	The inductance leakage (L_{l1}) is determined after designing the transformer.

2. Transformer Design

The key specifications of the transformer are magnetizing inductance, power loss, isolation voltage ($V_{ISOLATION}$) rating, and coupling capacitance. There are two types of transformers (toroid and planar) that are recommended due to their ease of design and low coupling capacitance.

2.1. Core Material Selection

To take advantage of the MPQ18913's high f_{sw} , the core should be able to operate at high frequencies. The core material should have a low relative permeability (between 100 and 1000). Some core material options include P9L (0.5MHz to 1.5MHz, manufactured by Encore), PC50 (1MHz to 2MHz, manufactured by TDK), and 61 material ($\geq 2\text{MHz}$, manufactured by Fair-Rite).

2.2. Toroid Transformer

To set up the toroid transformer, follow the guidelines below:

- Select the toroid transformer turns ratio.

At the resonant frequency (f_r), the LLC converter voltage gain is equal to the transformer turns ratio (N), which can be calculated with Equation (7):

$$N = \frac{V_{OUT_MIN} + 2V_f + V_{RESISTIVE_DROP} + V_{HEADROOM}}{V_{IN_MIN}} \quad (7)$$

Where V_F is the voltage drop of the rectification diodes (D1 and D3), $V_{RESISTIVE_DROP}$ is the voltage drop across primary-side MOSFETs and the resistance of transformer windings, V_{OUT_MIN} is the lower limit for V_{OUT} , V_{IN_MIN} is the lowest V_{IN} , and $V_{HEADROOM}$ is the V_{OUT} drop caused by the dummy load (e.g. an R1 power loss or an extra resistive load connected between $+20V_{OUT}$ and $-4V_{OUT}$).

Note that $V_{RESISTIVE_DROP}$ is proportional to the load current (I_{LOAD}), and is critical to the load regulation of the gate driver's power supply. For load regulation, a minimum number of turns (N) are recommended to reduce the resistance of the transformer windings.

$(2V_F + V_{RESISTIVE_DROP})$ can be estimated with Equation (8):

$$2V_F + V_{RESISTIVE_DROP} = (4N + 4) \times I_{LOAD} \tag{8}$$

Figure 3 shows a toroid transformer.

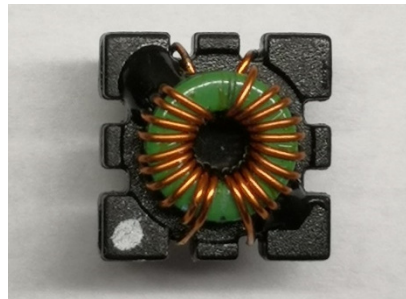


Figure 3: Toroid Transformer

2. Select the window size.

The window size of the toroid transformer requires careful selection to fit the windings. Given number of turns, the diameter of the magnet wire can be calculated with Equation (9):

$$D_{TOTAL} = D_{CONDUCTOR} + 2 \times T_{INSULATION} \tag{9}$$

Where D_{TOTAL} is the diameter of the winding wire, $D_{CONDUCTOR}$ is the diameter of conductor, and $T_{INSULATION}$ is the thickness of the insulation layer.

$D_{CONDUCTOR}$ can be four times the skin depth at f_{SW} . $T_{INSULATION}$ is related to the $V_{ISOLATION}$ rating. If the required $V_{ISOLATION}$ is below 2kV, then choose an enameled wire with a breakdown voltage (V_{BREAK}) that exceeds the transformer's $V_{ISOLATION}$ rating. If the required $V_{ISOLATION}$ exceeds 2kV, then double- or triple-insulated wires are recommended. If the turns ratio (N) does not equal 1, then use a thicker insulation layer for the low-voltage side of the windings. The two sides should have a V_{BREAK} equal to double the $V_{ISOLATION}$ rating.

Figure 4 shows the geometric structure of a toroid core.

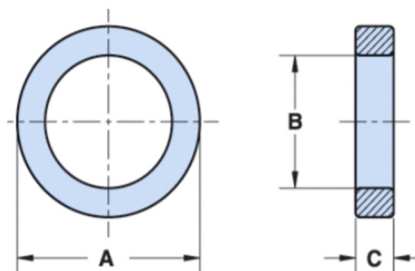


Figure 4: Toroid Core Geometric Structure

The toroid core's inside diameter (B) must be able to fit the windings. B can be calculated with Equation (10):

$$N_1 \sin^{-1} \frac{D_1}{B-D_1} + N_2 \sin^{-1} \frac{D_2}{B-D_2} < \frac{2}{3} \pi \quad (10)$$

Where N_1 and N_2 are the number for turns, and D_1 and D_2 are the wire diameters.

3. Select the core size based on the inductance per square turn (A_L) and the core loss.

A_L can be calculated with Equation (11):

$$L_m = N_1^2 \times A_L \quad (11)$$

Where L_m is the transformer magnifying inductance, which can be calculated with Equation 2 (see Table 1 on page 4). The other two geometric parameters (A and C) can be selected accordingly with A_L .

The maximum flux density (B_{MAX}) can confirm whether the core loss is acceptable. B_{MAX} can be calculated with Equation (12):

$$B_{MAX} = \frac{V_{IN_MAX}}{4 \times f_{SW} \times N_1 \times (A-B) \times C} \quad (12)$$

Consider the core loss density (provided by the core material vendor) at f_{SW} and B_{MAX} . The core loss density should not exceed 150mW/cm³ for thermal performance. If the application requires the density to exceed 150mW/cm³, then select a core that has a larger effective area or more turn windings.

4. Select the transformer bobbin.

Select a transformer bobbin that fits the core and windings. The transformer bobbin size and creepage between the leads of the primary and secondary sides is critical. It is recommended to have a ≥ 3.5 mm creepage for a 3kV $V_{ISOLATION}$ rating, and ≥ 7 mm creepage for a 5kV $V_{ISOLATION}$ rating.

After the transformer is built, its leakage inductance can be measured by the primary side while the two terminals of the secondary side are shorted. Then the resonant capacitance can be calculated with Equation 6 (see Table 1 on page 4).

2.3. Planar Transformer

To set up the planar transformer, follow the guidelines below:

1. Select the planar transformer turns ratio.

The method to determine the planar transformer turns ratio is the same as the toroid transformer. Follow step 1 in the Toroid Transformer section on page 4 to determine the planar transformer turns ratio.

Figure 5 shows a planar transformer with an ER core.

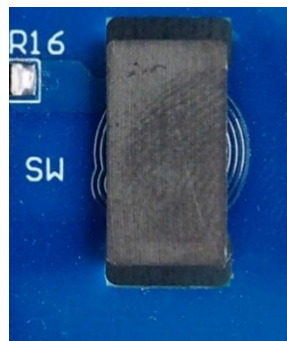


Figure 5: Planar Transformer with an ER Core

2. Select the window size.

If a 6-layer PCB layout is used, then use the middle layer to form the primary and secondary side as follows:

- Form the primary side by connecting mid-layer 1 and mid-layer 2 in series using coils.
- Form the secondary side by connecting mid-layer 3 and mid-layer 4 in series using coils.

Do not connect coils on the top and bottom layers to avoid masking the core by Hi-pot breakdown.

Figure 6 shows the geometric structure of an ER core.

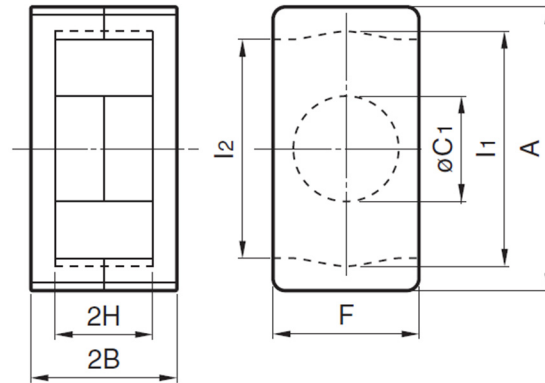


Figure 6: ER Core Geometric Structure

The window size ($I_1 - C_1$) can be calculated with Equation (13):

$$\frac{I_1 - C_1}{2} \geq \frac{N_x}{2} \times W_{\text{TRACE}} + \left(\frac{N_x}{2} - 1 \right) \times W_{\text{CLEARANCE}} + 2 \times L_{\text{INSULATION}} \quad (13)$$

Where N_x is the number of turns of the primary/secondary side, W_{TRACE} is the PCB trace width (10mil for a 0.25 load on 1oz PCB), $W_{\text{CLEARANCE}}$ is the clearance between the two PCB traces (1oz PCB requires a ≥ 4 mil clearance, typically), and $L_{\text{INSULATION}}$ is the clearance between the PCB trace and the core.

Then $L_{\text{INSULATION}}$ can be calculated with Equation (14):

$$L_{\text{INSULATION}} = \frac{V_{\text{ISOLATION}}}{2 \times E_b} \quad (14)$$

Where E_b is the dielectric strength of the pre-preg material.

The clearance between the primary and secondary sides in all directions can be calculated with Equation (15):

$$T_{\text{INSULATION}} = \frac{V_{\text{ISOLATION}}}{E_b} \quad (15)$$

For typical PCB layouts, the dielectric strength should be 250V/mil.

3. Determine the inductance per square turn (A_L).

The optimal A_L can be calculated with Equation 11 on page 6 or with Equation 2 (see Table 1 on page 4). If the permeability of the selected core material is high, then the air gap is required to reduce A_L . An air-gapped core is shown in Figure 7 shows an ER core with an air gap.



Figure 7: ER Core with an Air Gap

4. Select the core size.

Select the inner height ($2H$) according to the total PCB thickness . Then select a core that fits the PCB and coils.

B_{MAX} can confirm whether the core loss is acceptable. B_{MAX} can be calculated with Equation (16):

$$B_{MAX} = \frac{V_{IN_MAX}}{8 \times f_{SW} \times N_1 \times A_e} \quad (16)$$

Consider the core loss density (provided by the core material vendor) at f_{SW} and B_{MAX} . The core loss density should not exceed $200\text{mW}/\text{cm}^3$ for thermal performance. If the application requires the density to exceed $200\text{mW}/\text{cm}^3$, then select a core that has a larger effective area or more turn windings.

After the transformer is built, its leakage inductance can be measured by the primary side while the two terminals of the secondary side are shorted. Then the resonant capacitance can be calculated with Equation 6 (see Table 1 on page 4).

3. Selecting the Rectification Diodes

The diode capacitance (C_T) and reverse current (I_R) are two significant parameters of the rectification diodes. C_T and I_R can affect load regulation negatively.

C_T is part of the LLC resonant network, and raises the gain of the LLC converter at light loads. A small C_T is recommended for improved load regulation.

I_R increases as the diode temperature increases. At heavy loads, the temperature of the diodes rise, and I_R adds an extra load to the LLC converter. This increases load regulation.

Considering these parameters, it is recommended to use BAT165 (40V, 0.75A, AEC-Q101) or PMEG6010CEJ (60V, 1A, AEC-Q101) for the rectification diodes.

REVISION HISTORY

Revision #	Revision Date	Description	Pages Updated
1.0	8/26/2022	Initial Release	-

Notice: The information in this document is subject to change without notice. Please contact MPS for current specifications. Users should warrant and guarantee that third-party Intellectual Property rights are not infringed upon when integrating MPS products into any application. MPS will not assume any legal responsibility for any said applications.