

DC/DC Converter EMC Troubleshooting

November 2021

Agenda

- **General Guidelines for DC/DC EMC Troubleshooting**
- **Examples Cases with MPS DC/DC Evaluation Boards**
- **Conclusion**

Structured Troubleshooting

- Which EMC tests are failed by DUT? (radiated/conducted emissions)
- How about immunity?
- How does the test set-up look like?
- Housing: metal or plastic?
- Are cables connected to the system?
- At what frequency does the DUT exceed the limits?
- Is it possible to identify the source clock(s)?
- Where are the DC/DC converters placed in the system?



Structured Troubleshooting

- **Are filter elements placed at each cable?**
- **What is the distance from the DC/DC converter to the cable/connector?**
- **Identify and mark all high dV/dt and dI/dt circuit nodes**
- **Check the routing of those circuit nodes for potential coupling**
- **Use snap-on ferrites on cables, and try to distinguish CM and DM noise**
- **Place shielding over the DC/DC converter block**

Tool Set for Troubleshooting

Cu-Foil

Snap-On Ferrite

Shielding

Field Probes


Identify the Source

Are discrete frequency lines above the limit or “mountains”?
Try to identify the source.

Sometimes the source is obvious.


Scan: #2 [30 MHz - 108 MHz] Supply

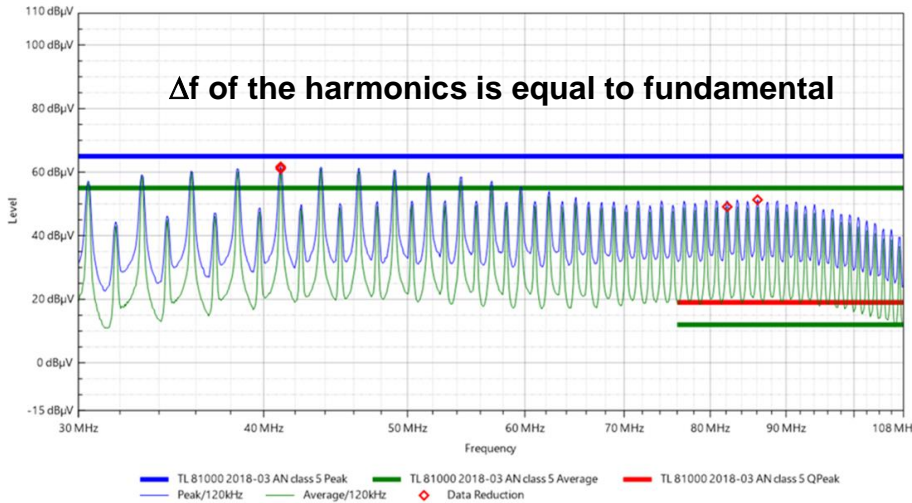Δf of the harmonics is equal to fundamental



But sometimes it is not.

Supply


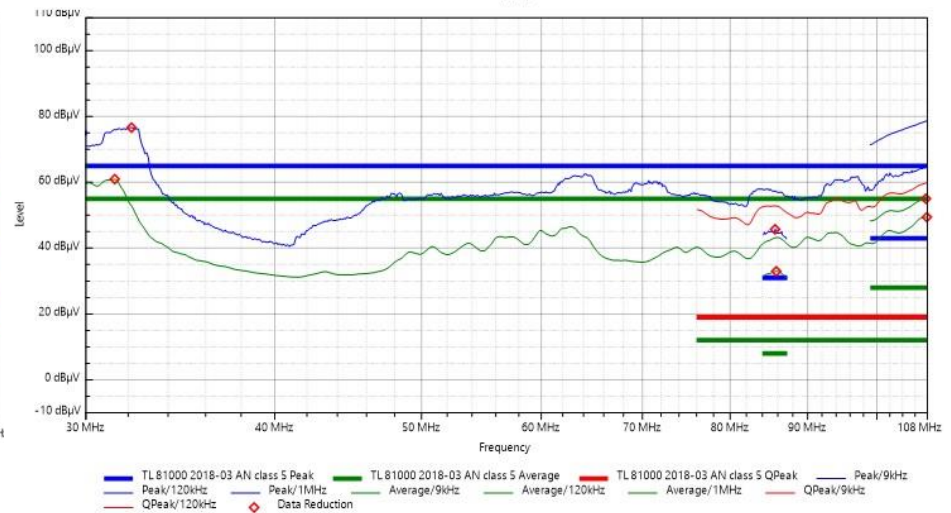


Identify the Source

Which clocks are used in the system? Measure the exact frequencies of all clocks. Then reate a table with the clocks, harmonics, and mixing products.

	f1 [MHz]	f2 [MHz]	f2 - f1 [MHz]	f1+f2 [MHz]	f3 [MHz]	f3 + f1 [MHz]	f3 - f1 [MHz]
Fsw	0.489	1.93	1.441	2.419	20.03	20.519	19.541
2x	0.978	3.86	2.882	4.838	40.06	41.038	39.082
3x	1.467	5.79	4.323	7.257	60.09	61.557	58.623
4x	1.956	7.72	5.764	9.676	80.12	82.076	78.164
5x	2.445	9.65	7.205	12.095	100.15	102.595	97.705
6x	2.934	11.58	8.646	14.514	120.18	123.114	117.246
7x	3.423	13.51	10.087	16.933	140.21	143.633	136.787
8x	3.912	15.44	11.528	19.352	160.24	164.152	156.328
9x	4.401	17.37	12.969	21.771	180.27	184.671	175.869
10x	4.89	19.3	14.41	24.19	200.3	205.19	195.41
11x	5.379	21.23	15.851	26.609	220.33	225.709	214.951
12x	5.868	23.16	17.292	29.028	240.36	246.228	234.492
13x	6.357	25.09	18.733	31.447	260.39	266.747	254.033

Use Snap-On Ferrite

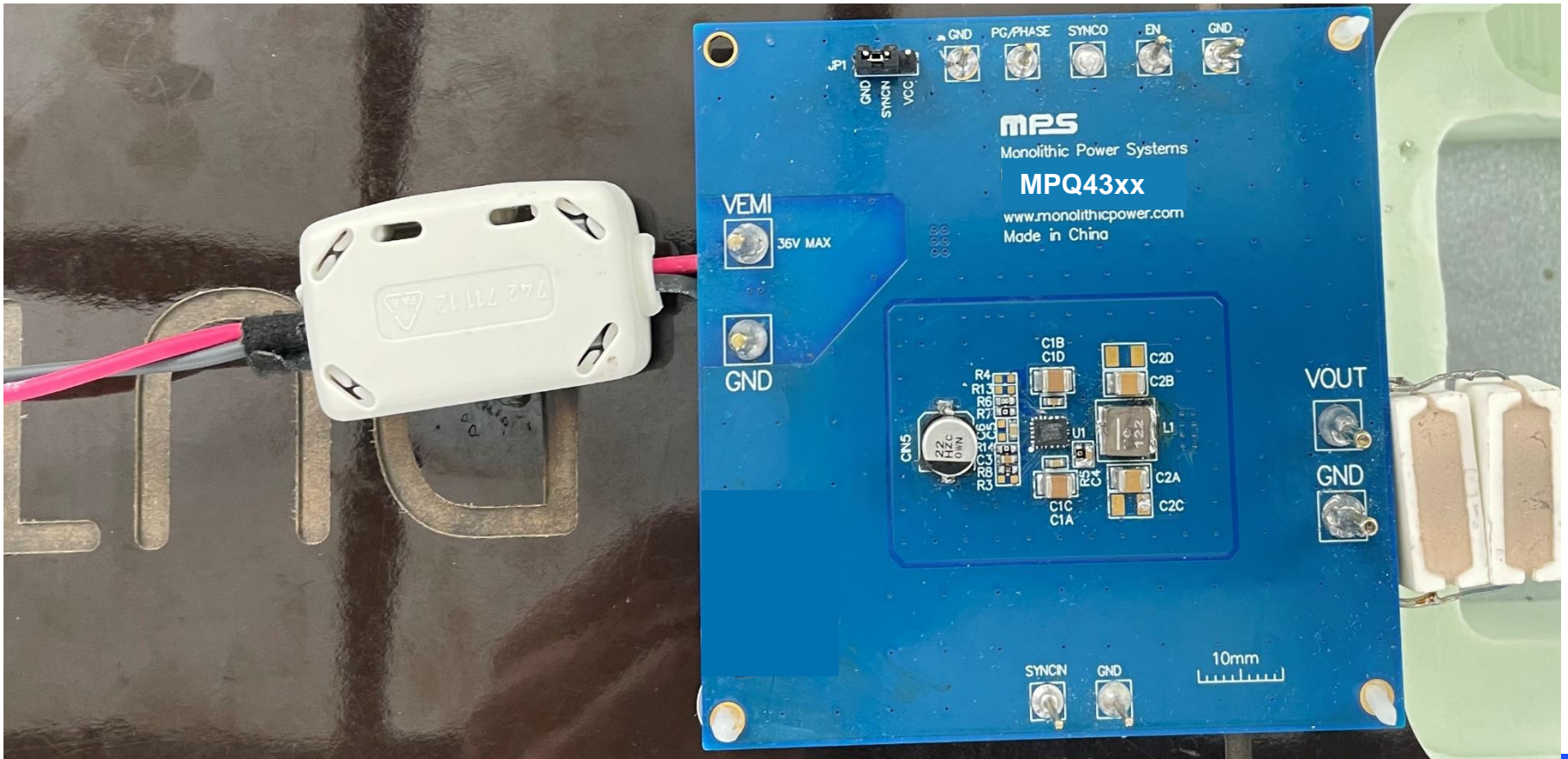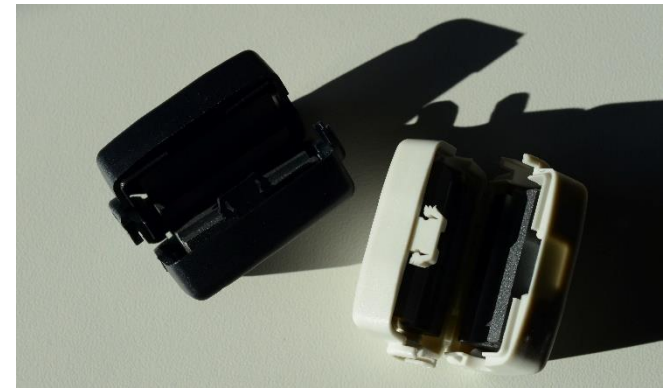

Try to Find the Path

- Increase the input filter capacitors by 2x
- Increase the input filter coil by 2x
- What is the distance between the buck C_{IN} and the filter?
- Is an off-board filter effective?



Field Probes

H- and E-Field Probes





They can be used with a scope, spectrum analyzer, or EMC receiver

Use Cu-Foil


Start with the DC/DC converter and coil...

.... to part of the PCB.

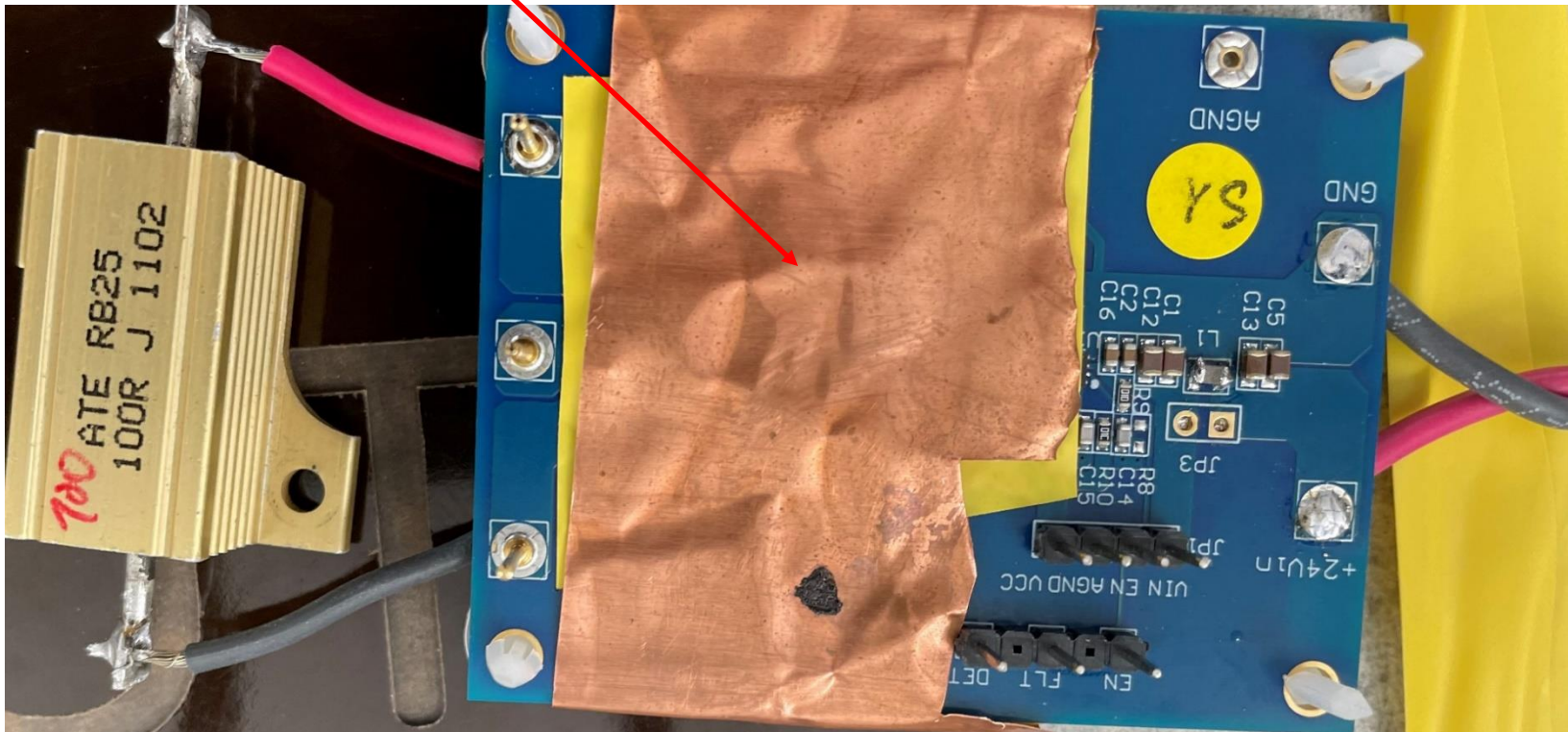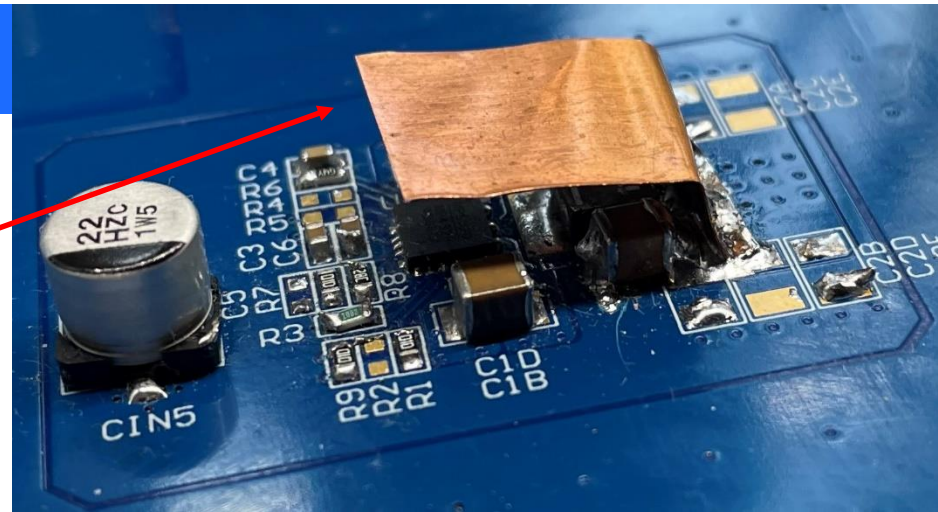

Refresh: Buck Converter Voltage & Current Waveforms

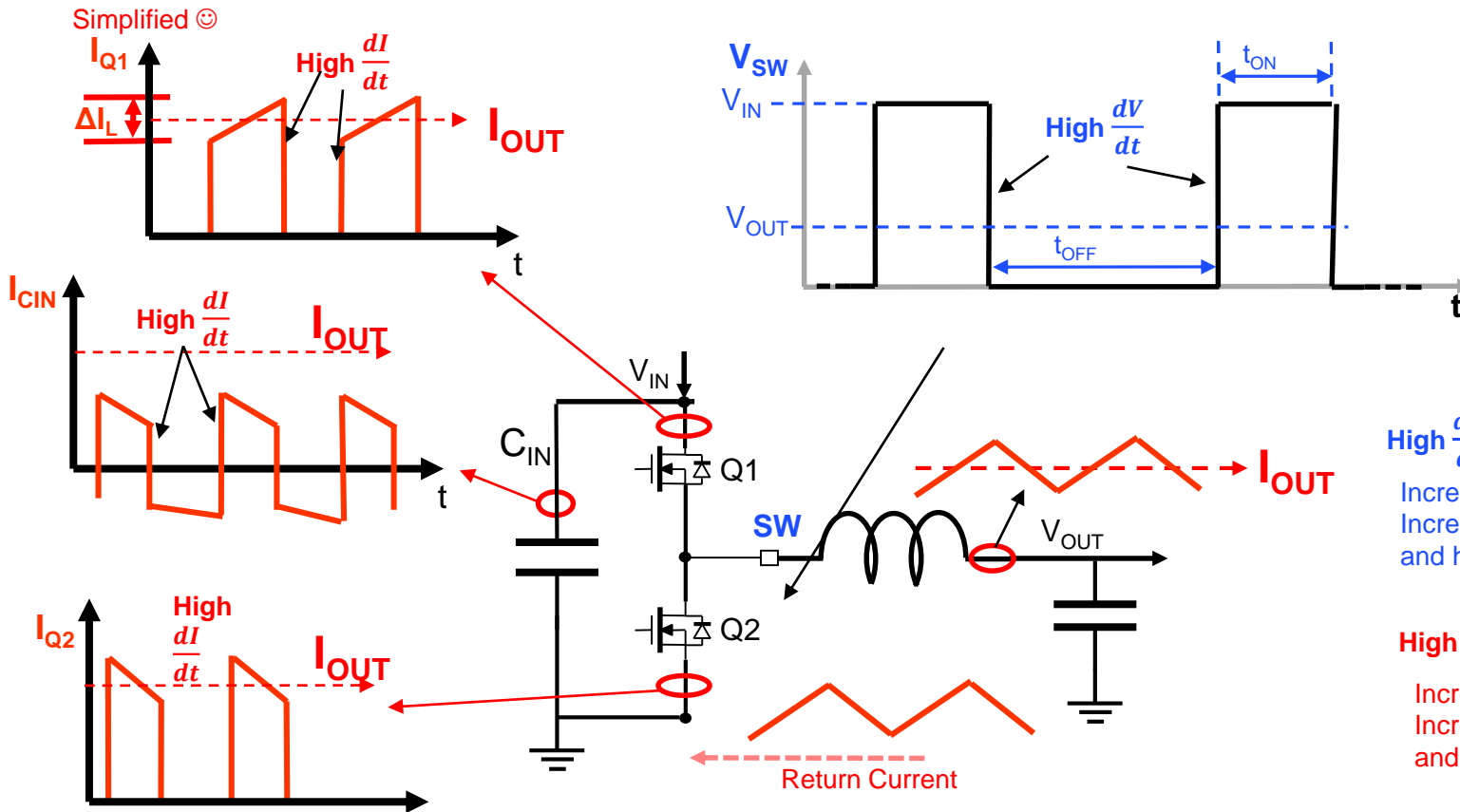A boost converter is just a mirror image.





High $\frac{dV}{dt} \Rightarrow E - Field$

Increases with voltage
Increases with antenna size
and height above PCB

High $\frac{dI}{dt} \Rightarrow H - Field$

Increases with current
Increases with loop size
and height above PCB

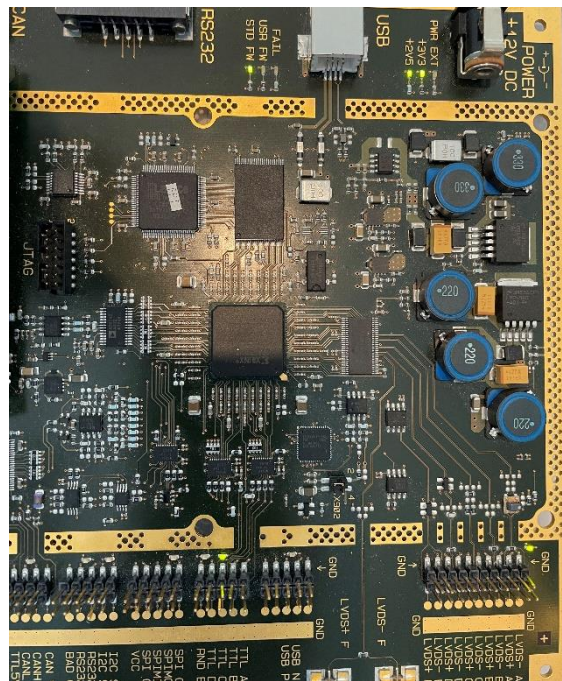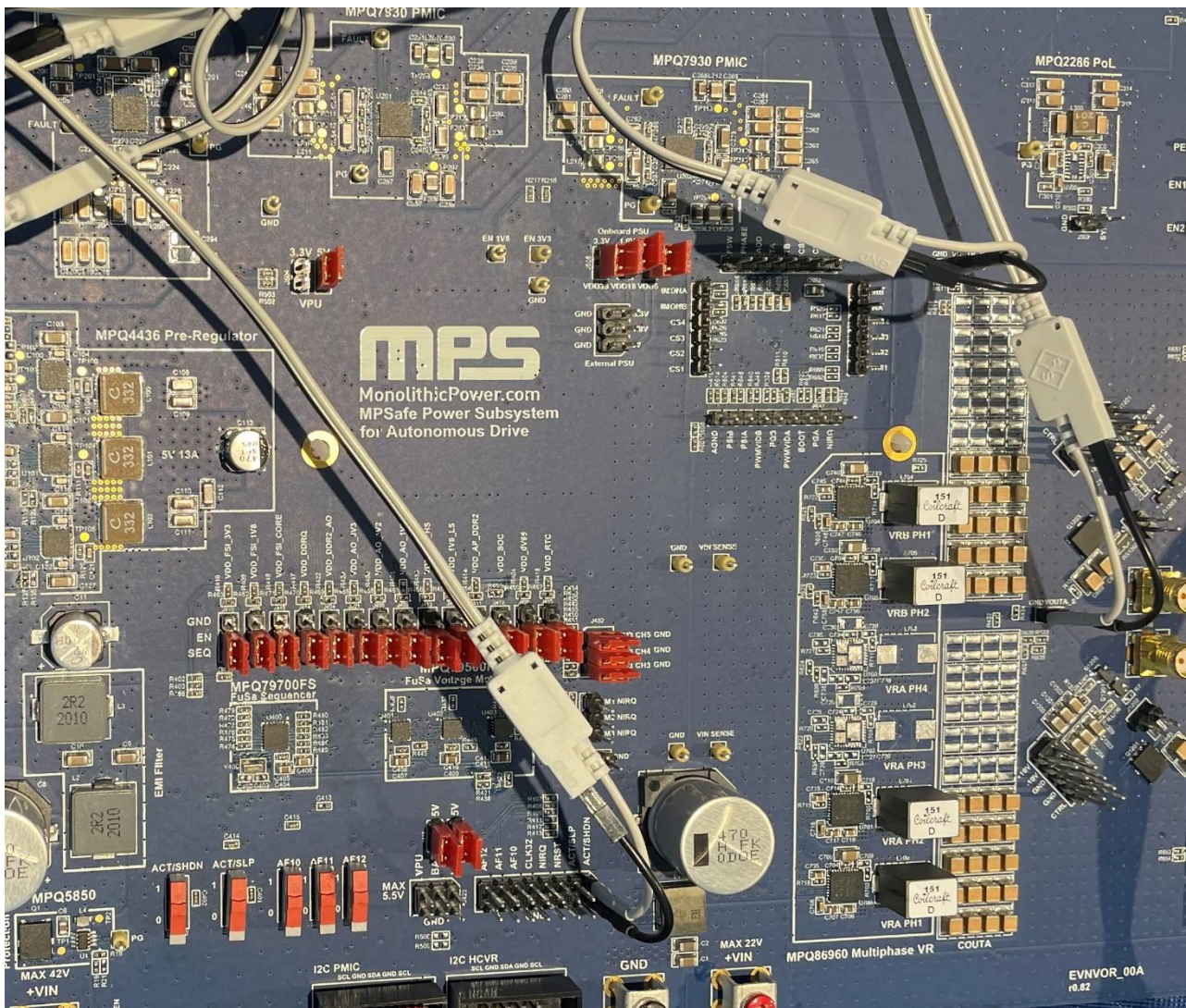Large Boards with Many DC/DC Buck Converters




Several DC/DC Bucks on One Large Power Rail

This can be the main system input (12V or 24V).

PCB traces have few mΩ and nH

System Connector

EMC Filter

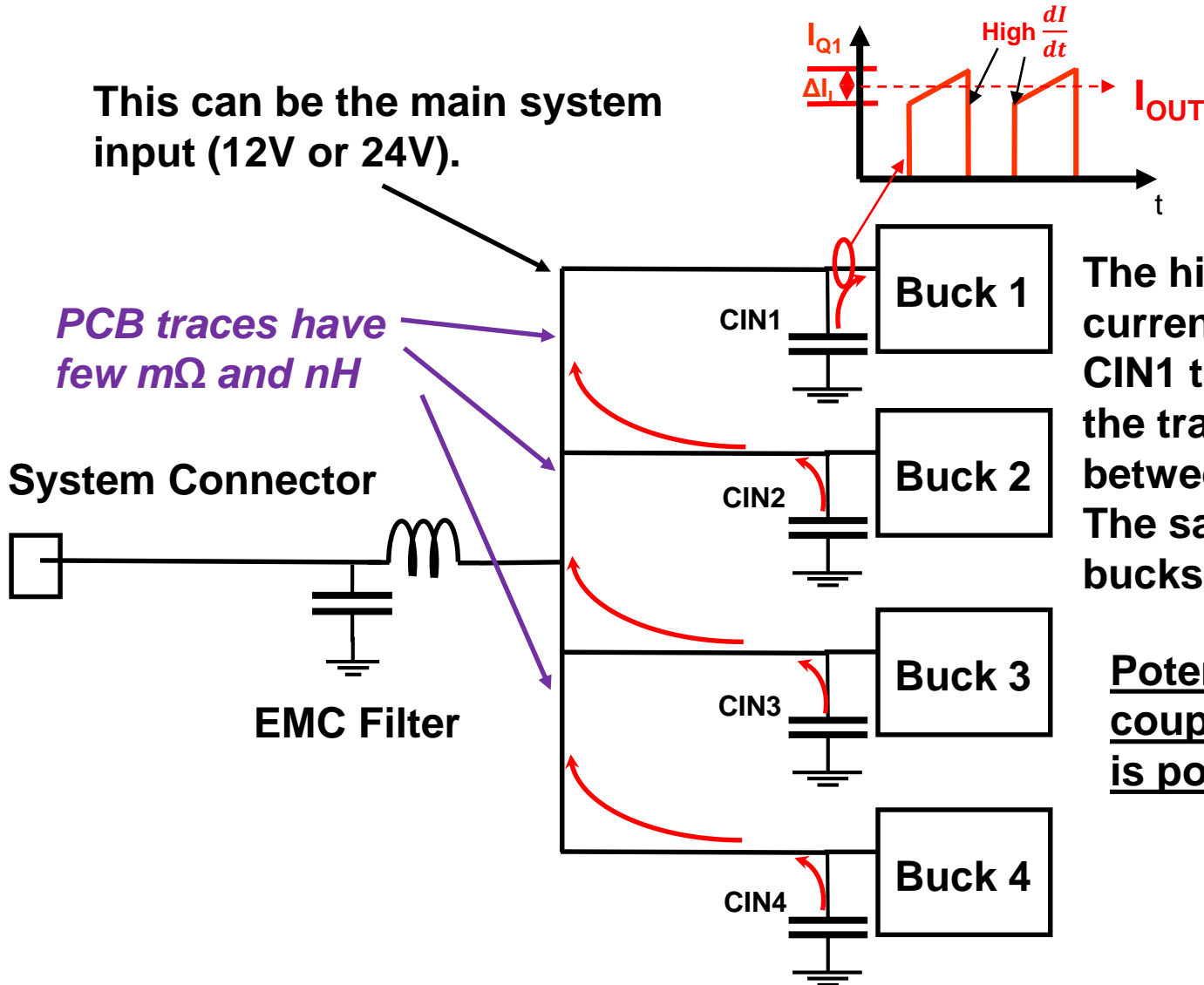


The high dI/dt input current of buck 1 splits to CIN1 to CIN4, according to the trace impedance between DC/DC and CINx. The same applies for bucks 2~4.

Potential radiation and coupling in other circuits is possible!

Several DC/DC Bucks on One Large Power Rail

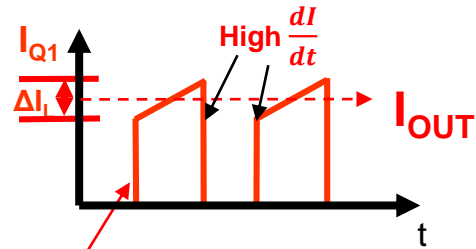Intermediate rail (5V or 3.3V POL on a large board)




PCB traces have few m Ω and nH


The high dI/dt input current of buck 1 splits to CIN1 to CIN4, according to the trace impedance between DC/DC and CINx. The same applies for bucks 2~4.

Potential radiation and coupling in other circuits is possible!


System Connector

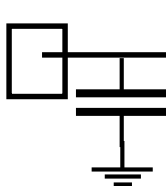

EMC Filter

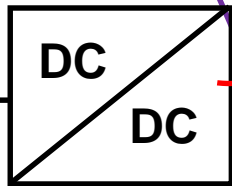

Primary Buck


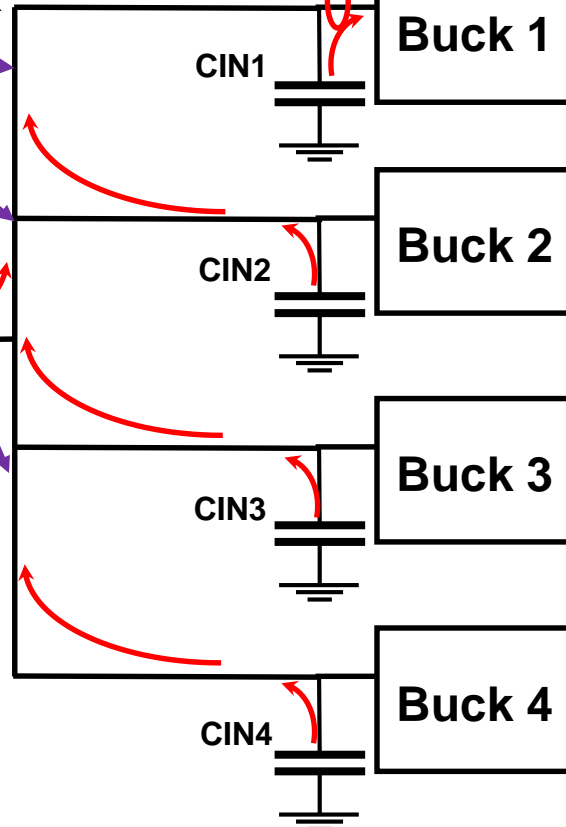


Several DC/DC Bucks on One Large Power Rail

Place a small coil (100nH to 1µH)
between individual DC/DC converters


The coil must have a
much higher L than
the PCB trace between
the DC/DC converters

System Connector

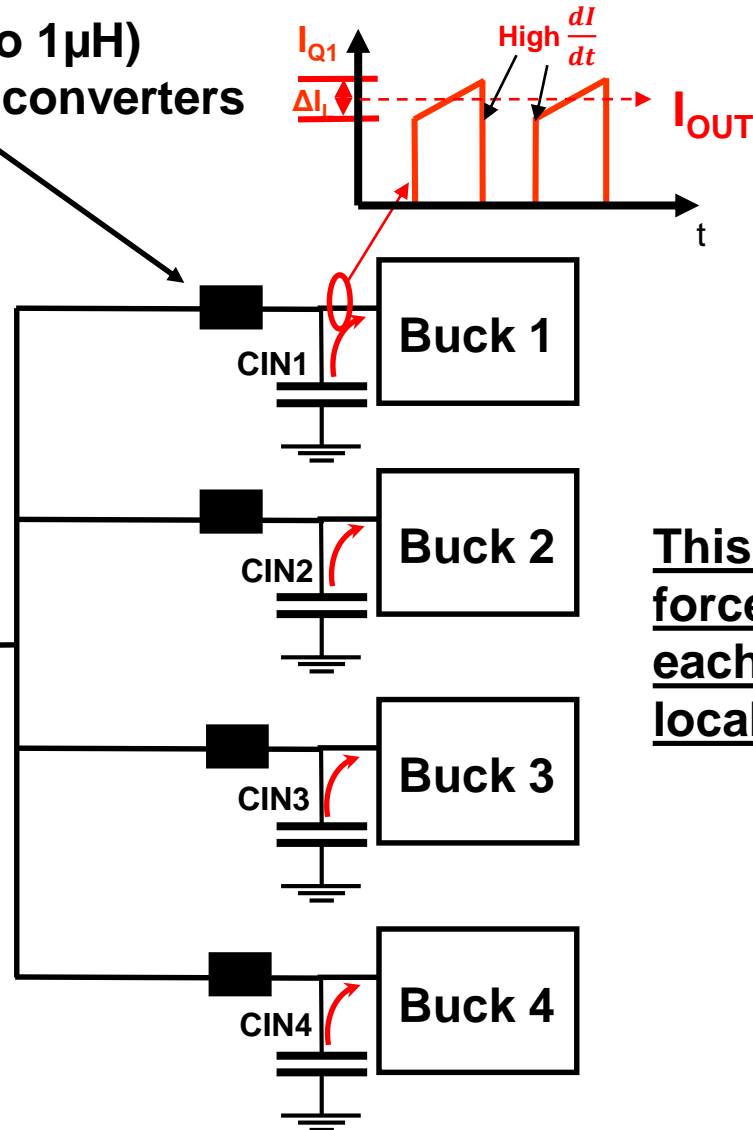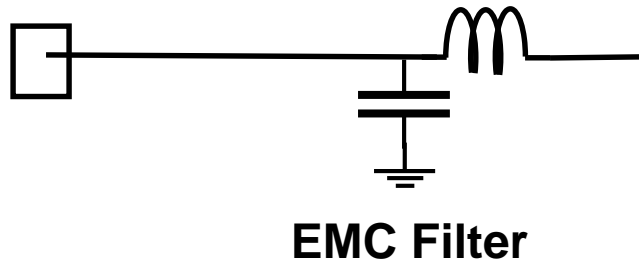


This configuration
forces the high dI/dt of
each buck to flow in its
local CIN!

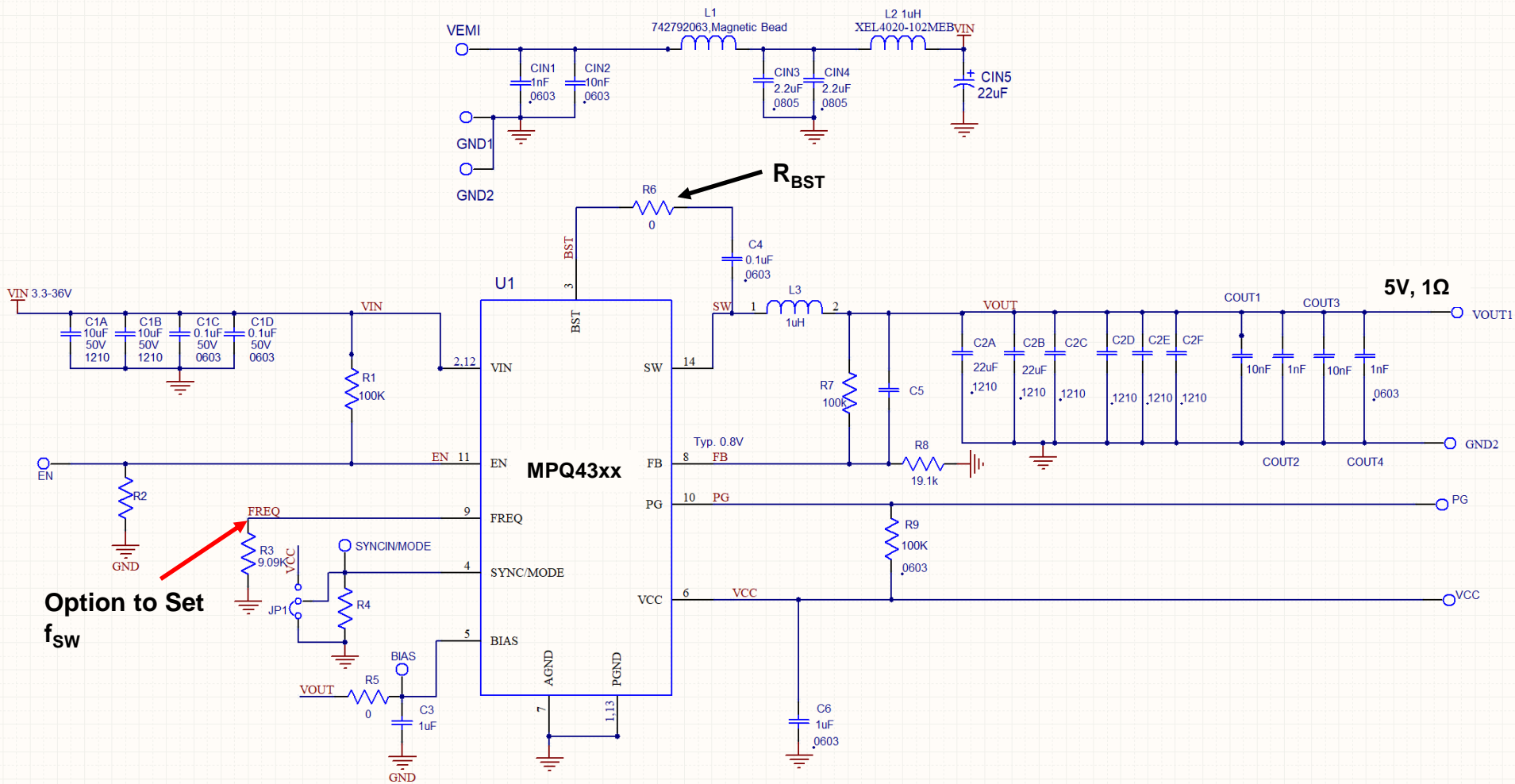MPS Example #1: 5A Buck $f_{sw} = 2\text{MHz}$




Top Layer

Input Filter Placed on the Bottom Side

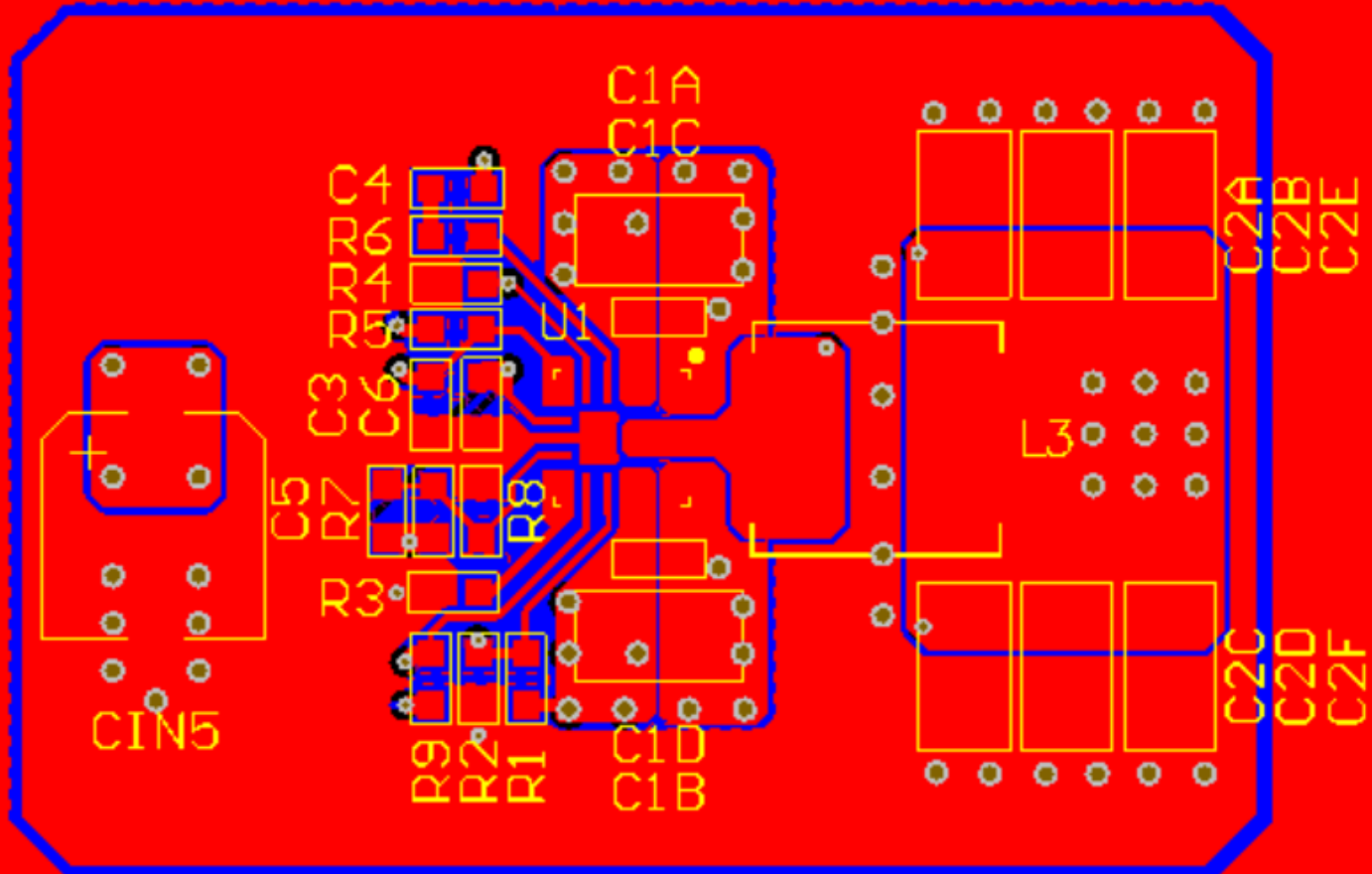


MPQ43xx 5V 5A Buck 2.2MHz with SSFM

Input Filter on the Bottom

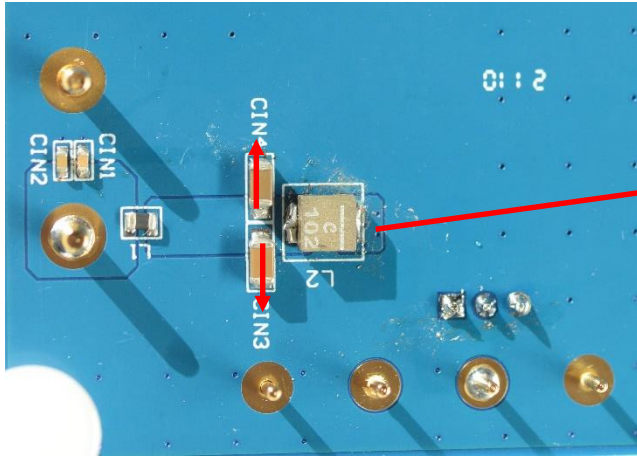

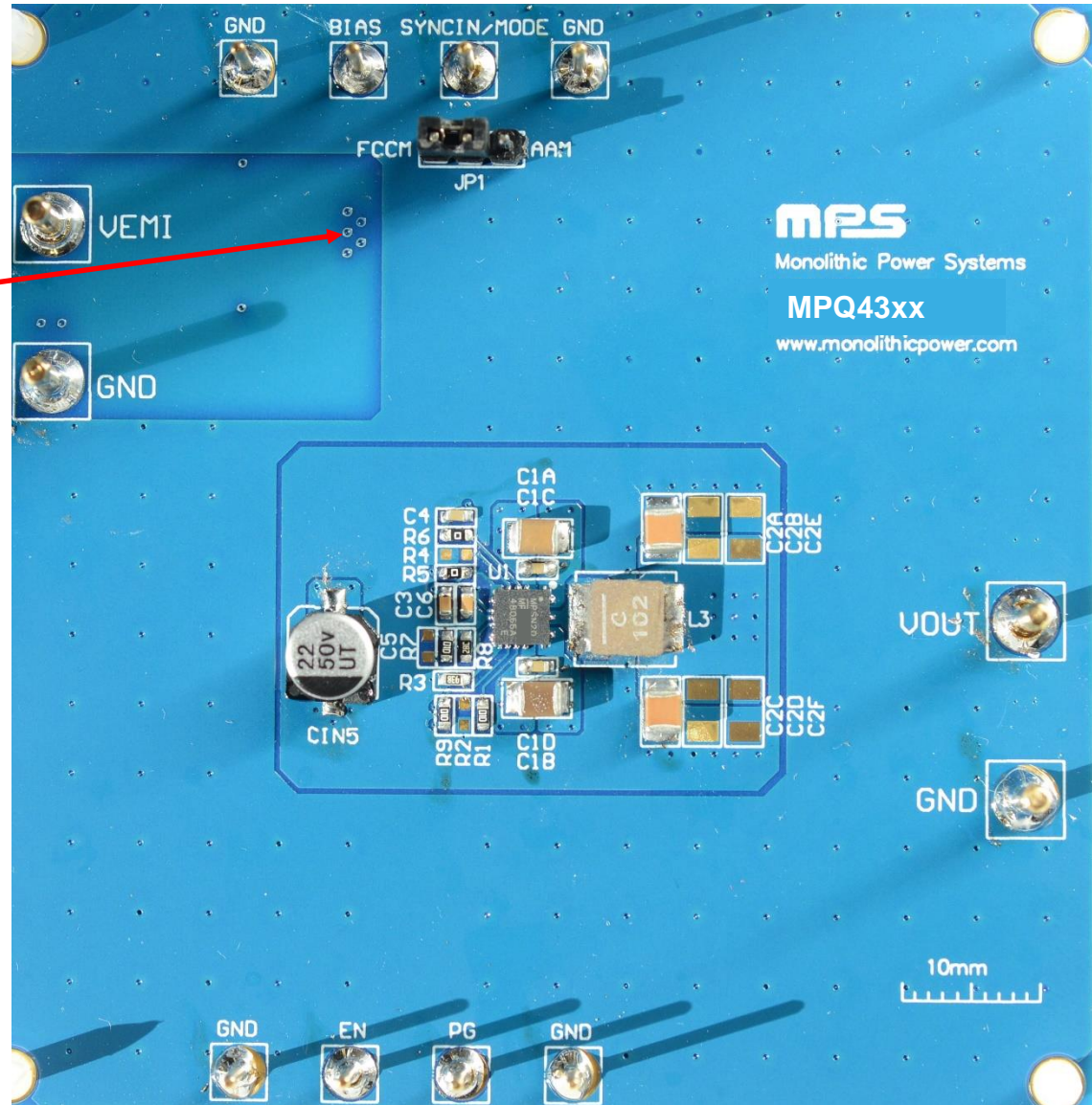The input filter has about 50dB damping at 2.2MHz.



Input L, C Filter – Simplified 1-Stage vs. 2-Stage

Input EMC Filter: Single-Stage vs. Two-Stage

=Enter your parameter

Single-Stage	Fundamental	1st Harm	2nd Harm	3rd Harm	4th Harm	5th Harm
f_{sw} :	2.20 MHz	4.40	6.60	8.80	11.00	13.20
Omega f_{sw}	13.821/ μ s	27.65	41.47	55.29	69.11	82.94
L_single:	0.33 μ H					
XL:	4.56 Ω	9.12	13.68	18.25	22.81	27.37
C-effective:	0.70 μ F					
XC:	0.10 Ω	0.052	0.034	0.026	0.021	0.017
Damping	-33.09 dB	-44.99	-52.00	-56.99	-60.86	-64.03
Two-Stage Filter Design:						
1st L:	0.10 μ H					
XL:	1.38 Ω	2.76	4.15	5.53	6.91	8.29
1st C:	0.60 μ F					
XC:	0.121 Ω	0.060	0.040	0.030	0.024	0.020
Damping 1	-21.91 dB	-33.42	-40.36	-45.32	-49.18	-52.33
2nd L:	0.10 μ H					
XL:	1.38 Ω	2.76	4.15	5.53	6.91	8.29
2nd C:	0.40 μ F					
XC:	0.181 Ω	0.090	0.060	0.045	0.036	0.030
Damping 2:	-18.73 dB	-29.99	-36.88	-41.82	-45.67	-48.82
Total Damping:	-40.65 dB	-63.40	-77.23	-87.13	-94.84	-101.16


Simplified calculation: $20 \log (X_c / (X_c + X_L))$ at f_{sw} , $2 \times f_{sw}$, etc.



Reduced Input Filter for 2MHz with SSFM


This filter has ~33dB damping at 2.2MHz.

CIN3/4 = 470nF, 0603

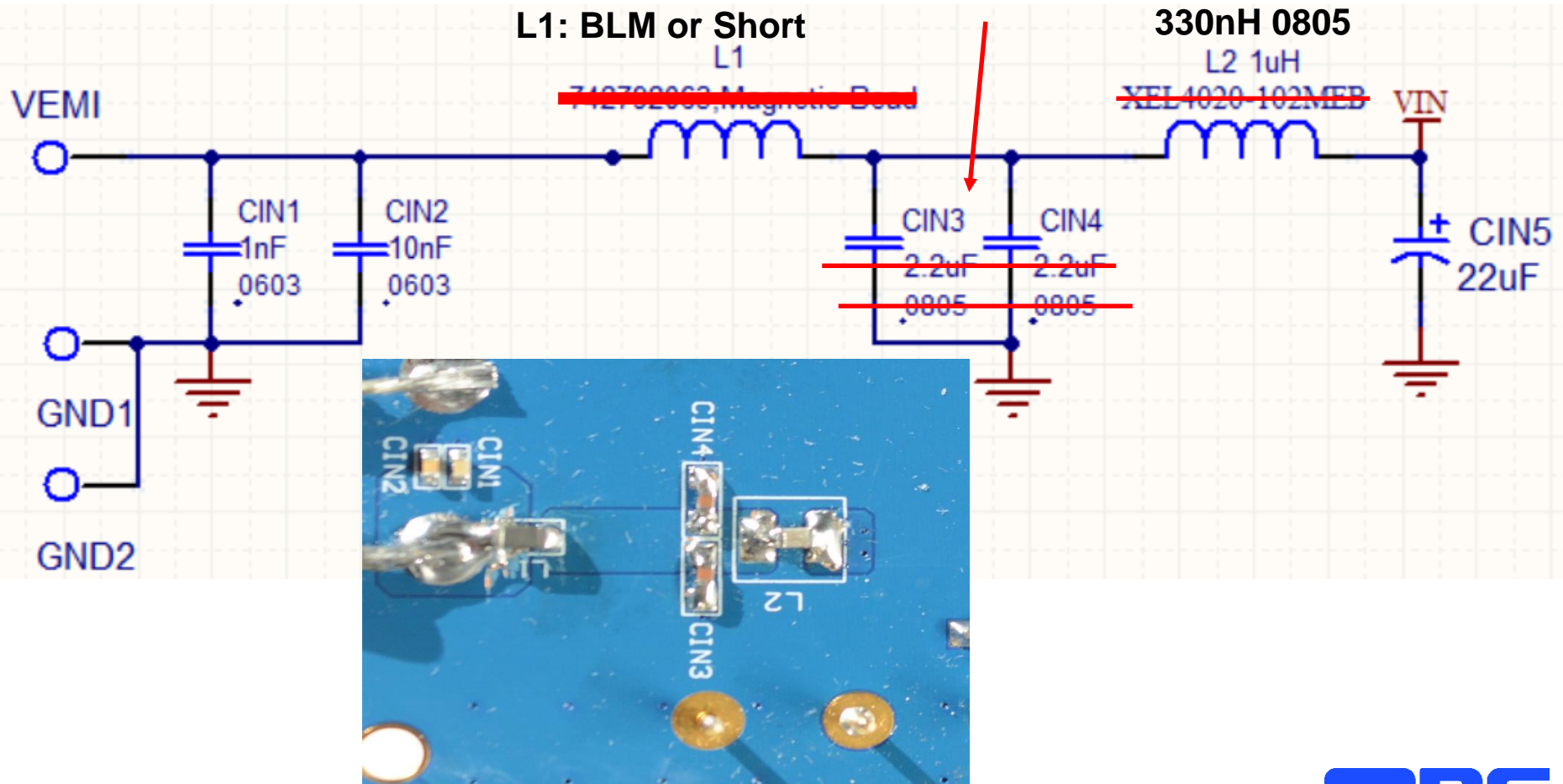

CE Test without and with Reduced Input Filter

Supply

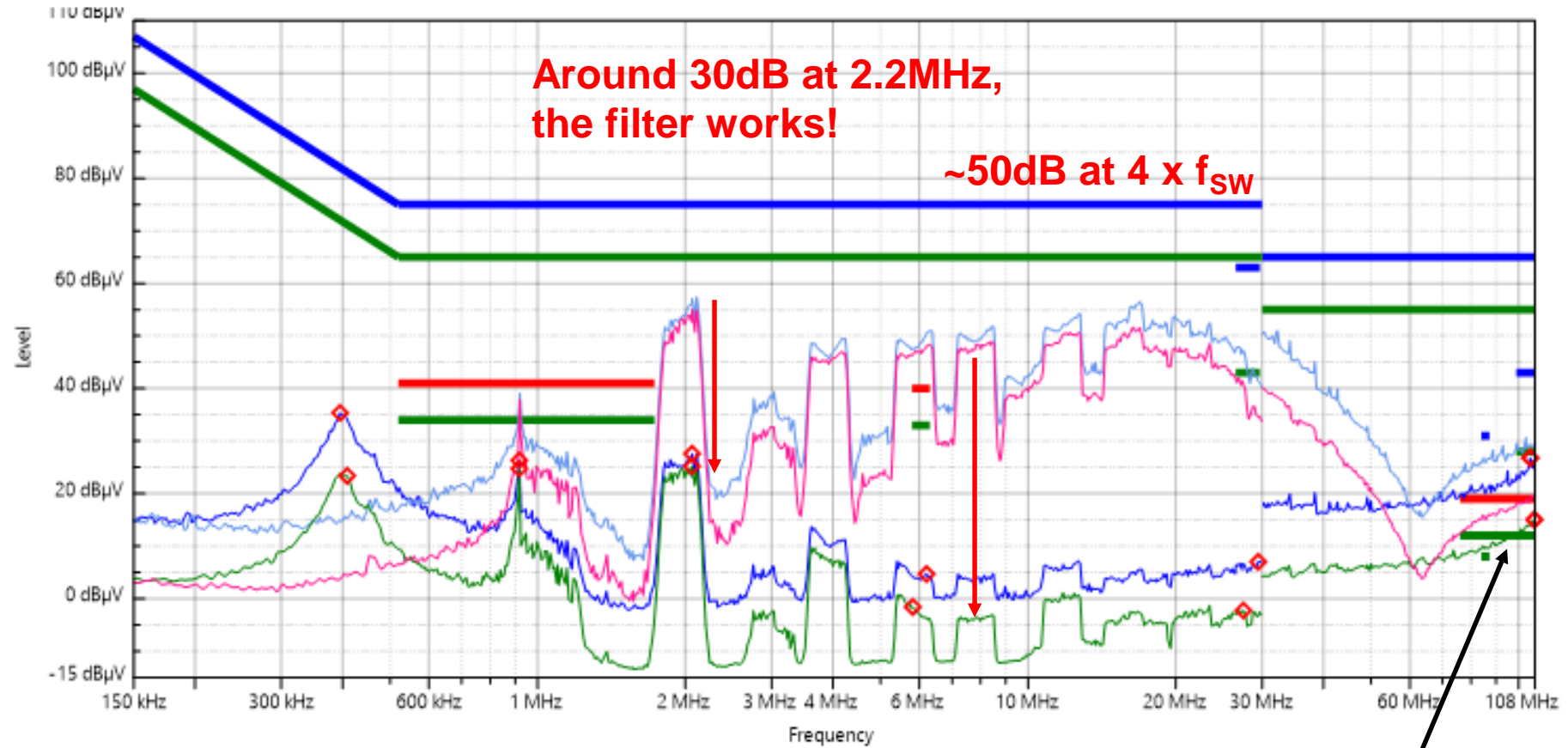


- TL 81000 2018-03 AN class 5 Peak
- TL 81000 2018-03 AN class 5 Average
- TL 81000 2018-03 AN class 5 QPeak
- Peak/9kHz
- Peak/120kHz
- Peak/9kHz (#1)
- Peak/120kHz (#1)
- Average/9kHz
- Average/120kHz
- Average/9kHz (#1)
- Average/120kHz (#1)
- ◇ Data Reduction

Not good enough in the FM band



Top Layer – Modification


Rotate the coil to verify SoW!

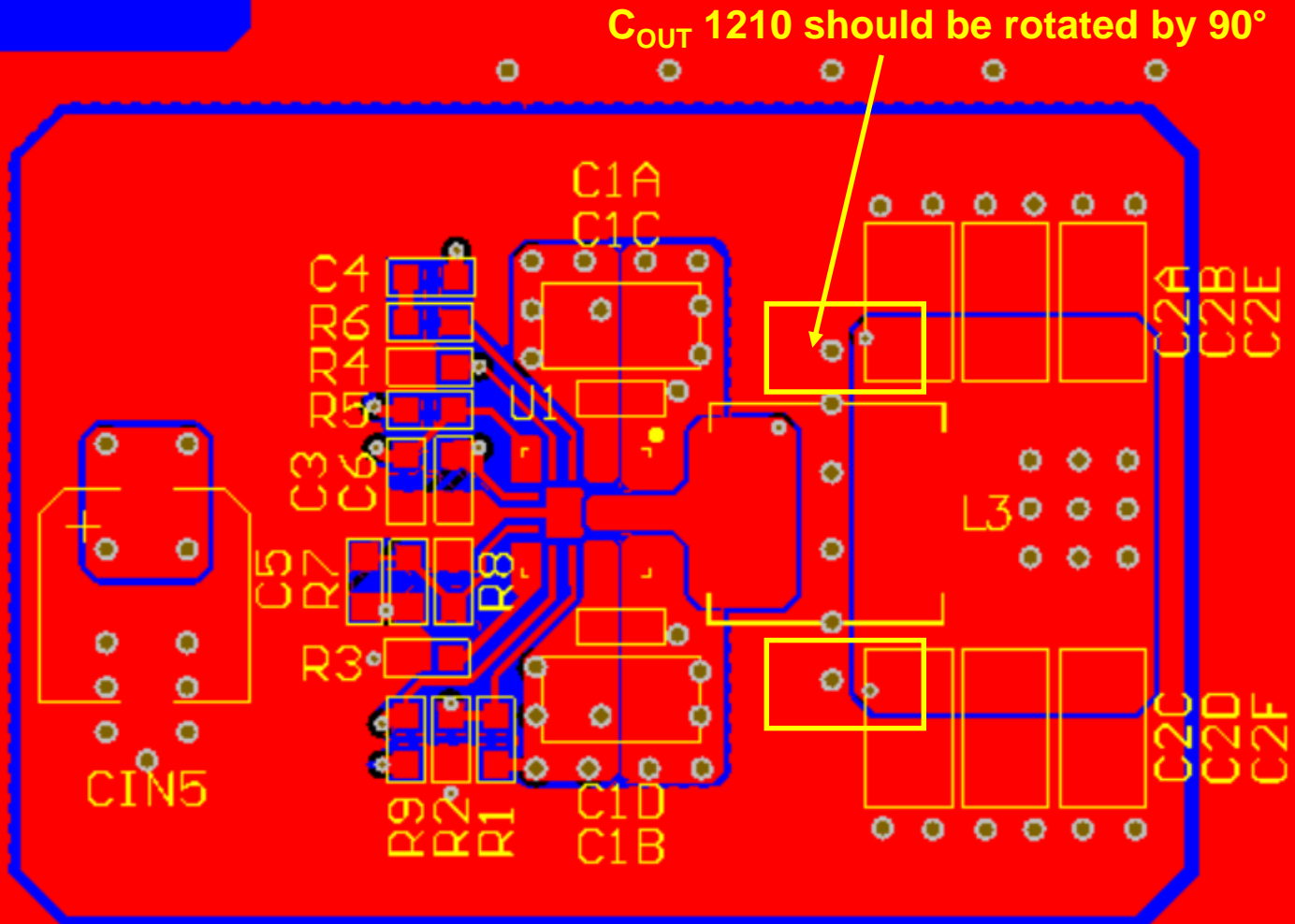

XAL5030 1 μ H in Both Directions


Start of winding at SW is 2dB to 3dB better

B3

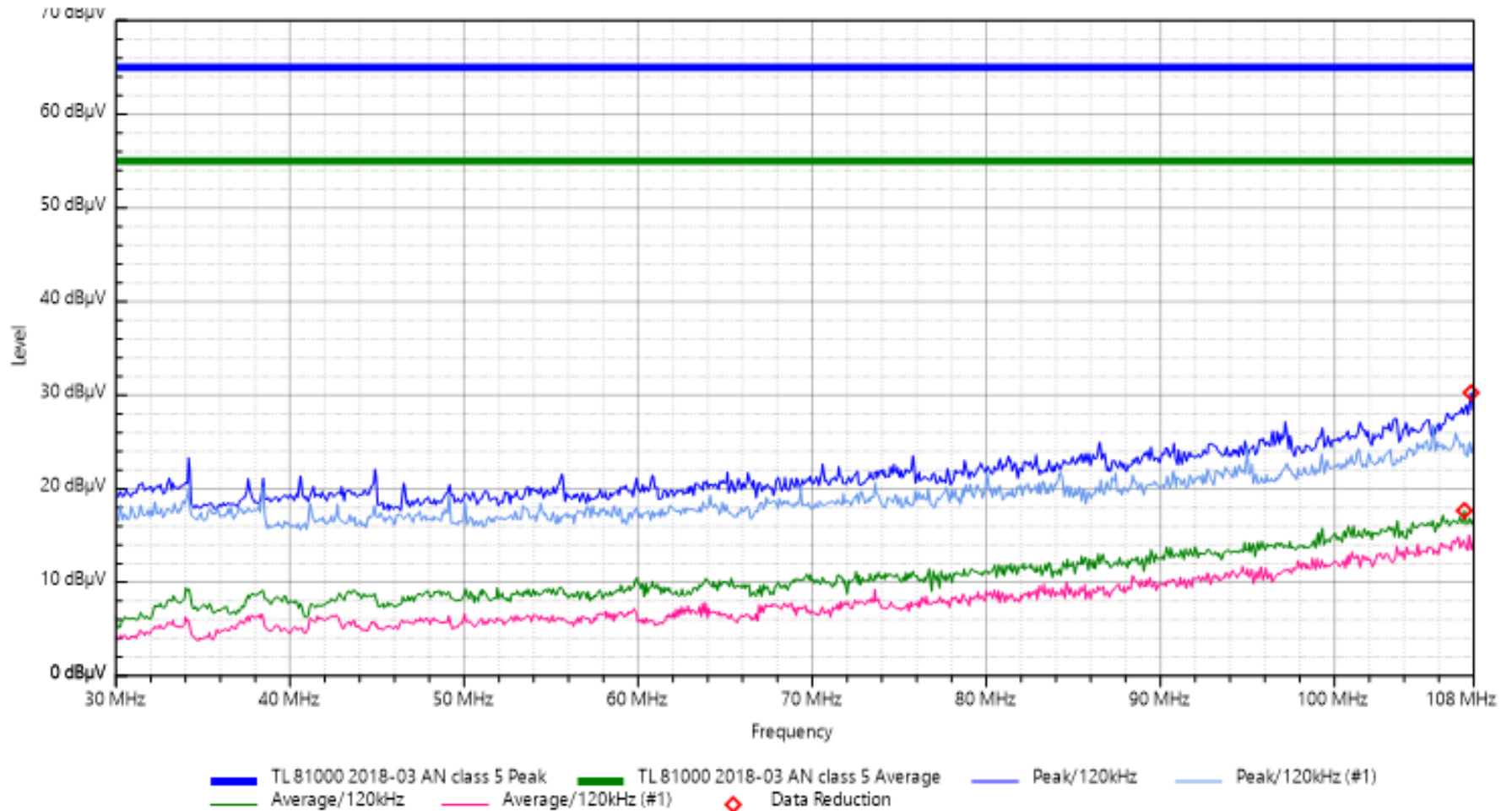

Replace XAL5030-1 μ H by XAL4020-1 μ H



B3

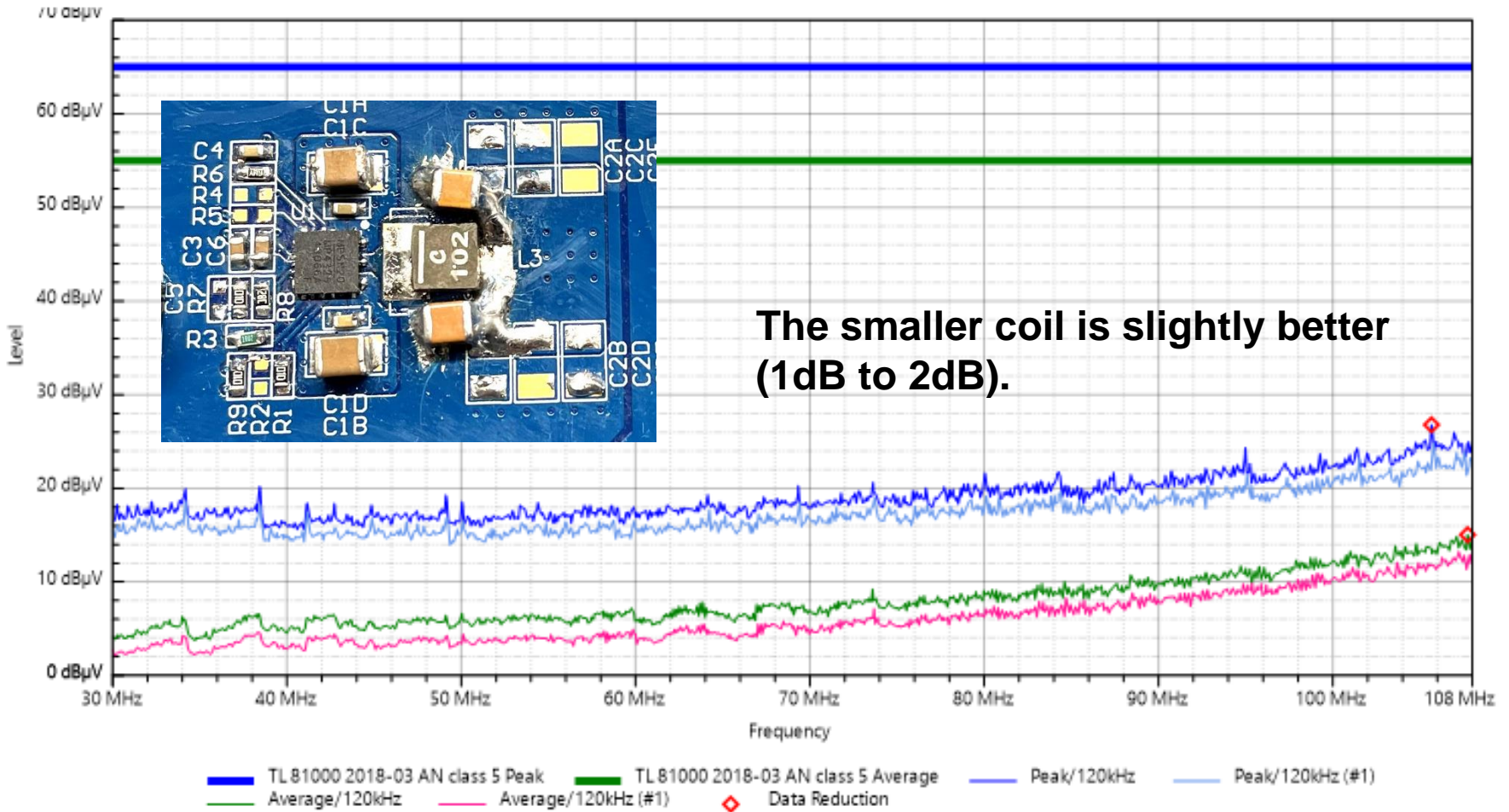

Add 4.7Ω Into BST Circuit

Effective above 90MHz

B3

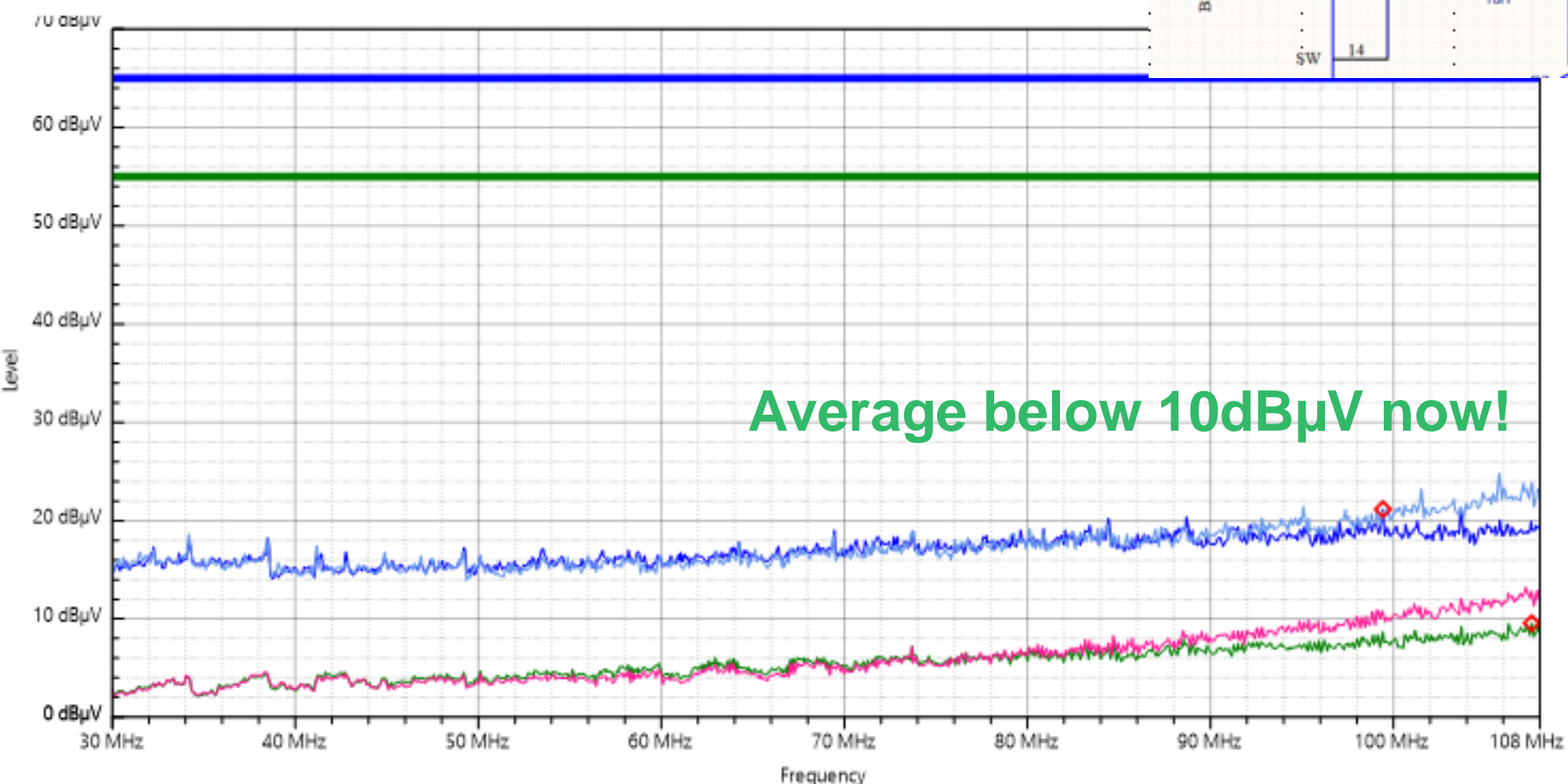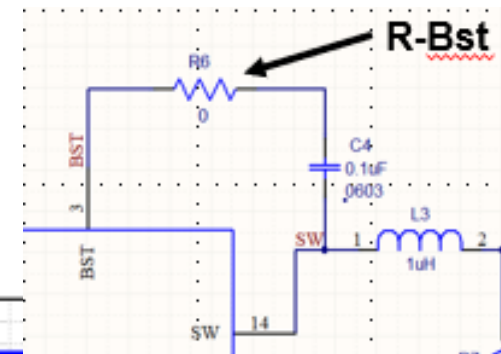


Average below 10dBµV now!

- TL 81000 2018-03 AN class 5 Peak
- TL 81000 2018-03 AN class 5 Average
- Peak/120kHz
- Peak/120kHz (#1)
- Average/120kHz
- Average/120kHz (#1)
- ◇ Data Reduction


MPS Example #2

13V to 3.3V System Buck, 4A

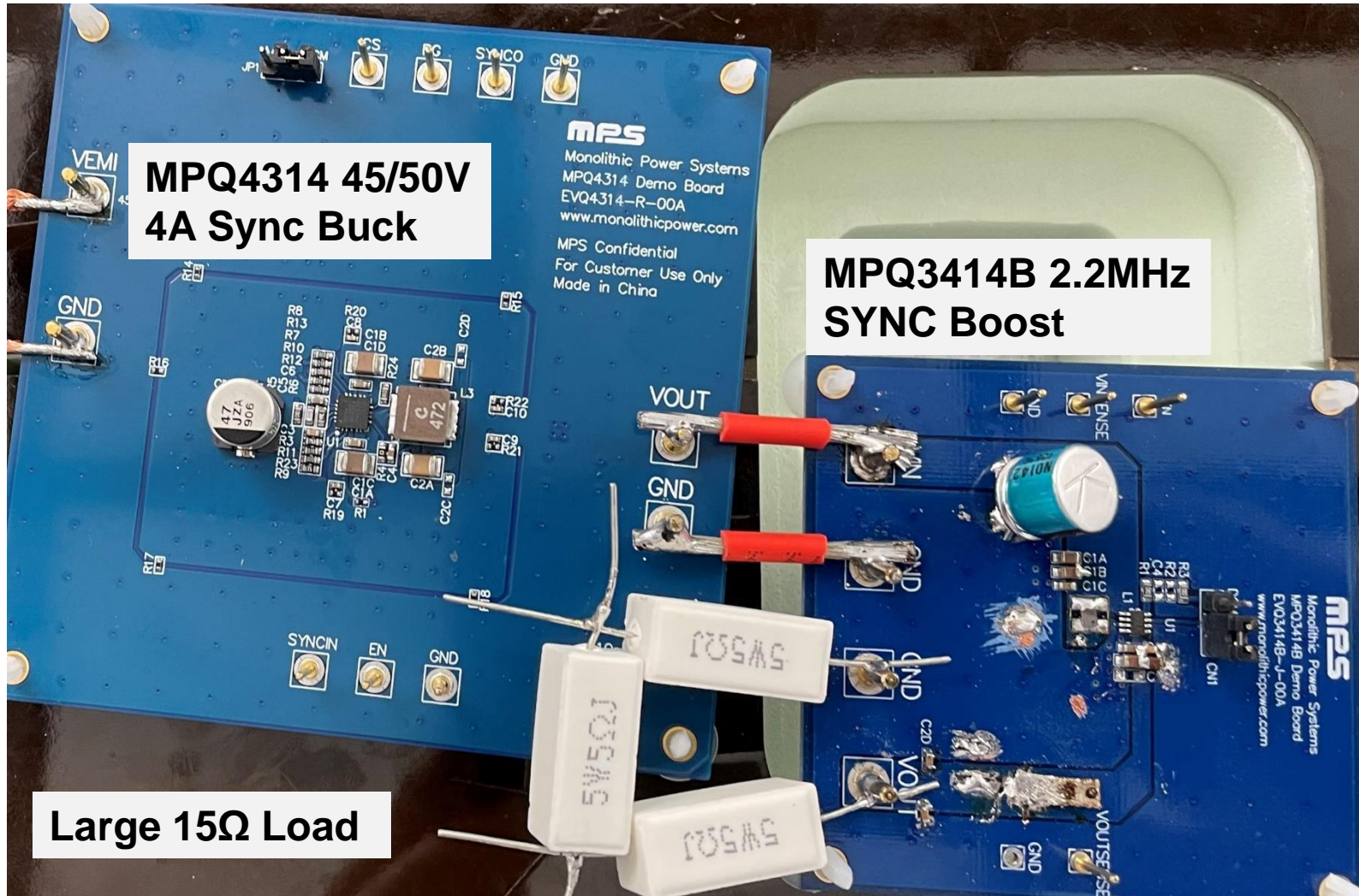3.3V to 5V Local Boost
for CAN (330mA, 1.66W)




MPQ314B Boost Schematic

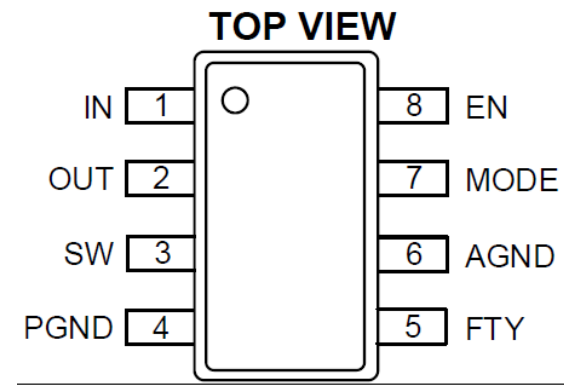


SW has 5V_{PKPK} with fast dV/dt

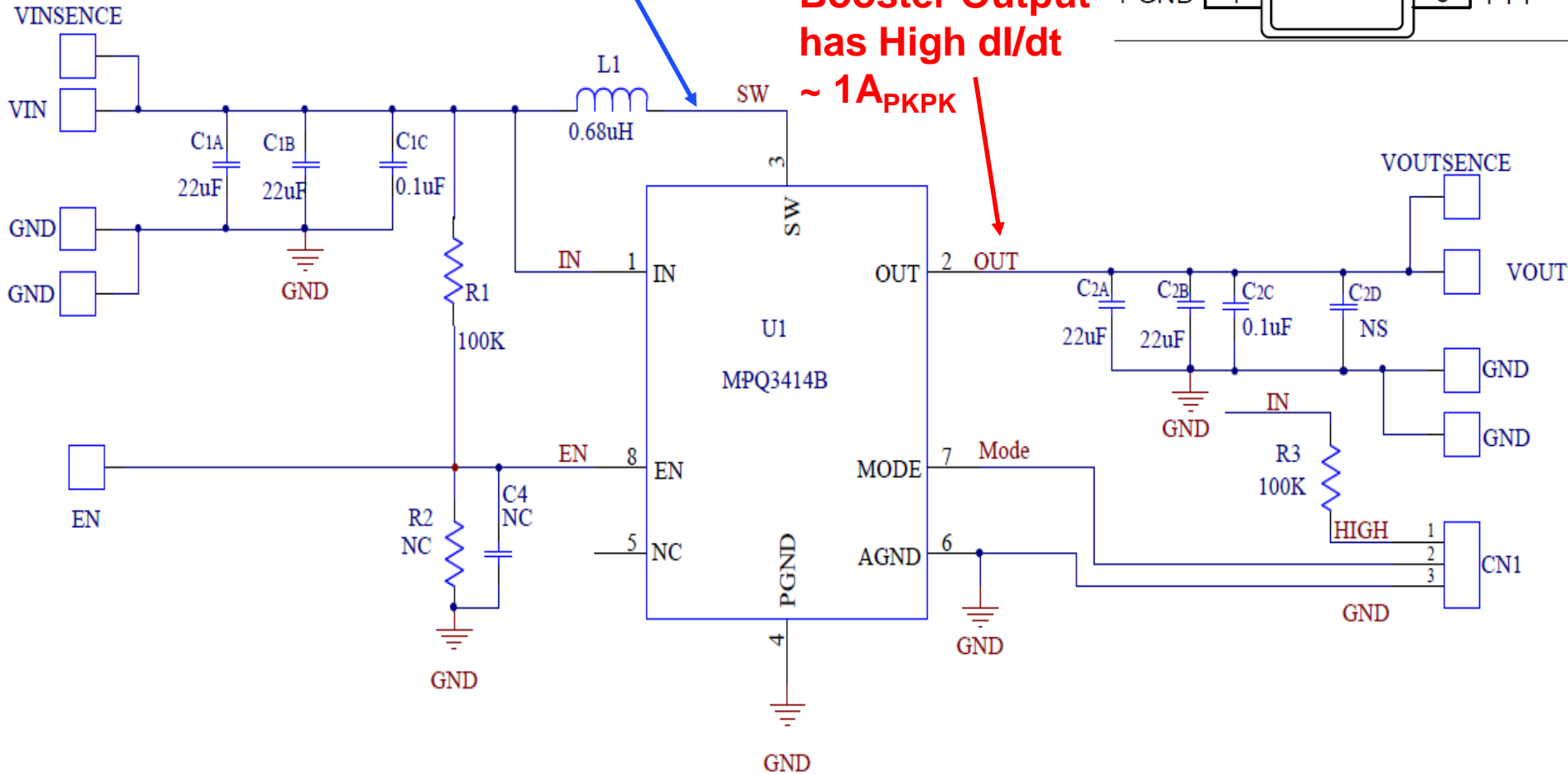Booster Output has High dI/dt ~ 1A_{PKPK}



Circuit Modification

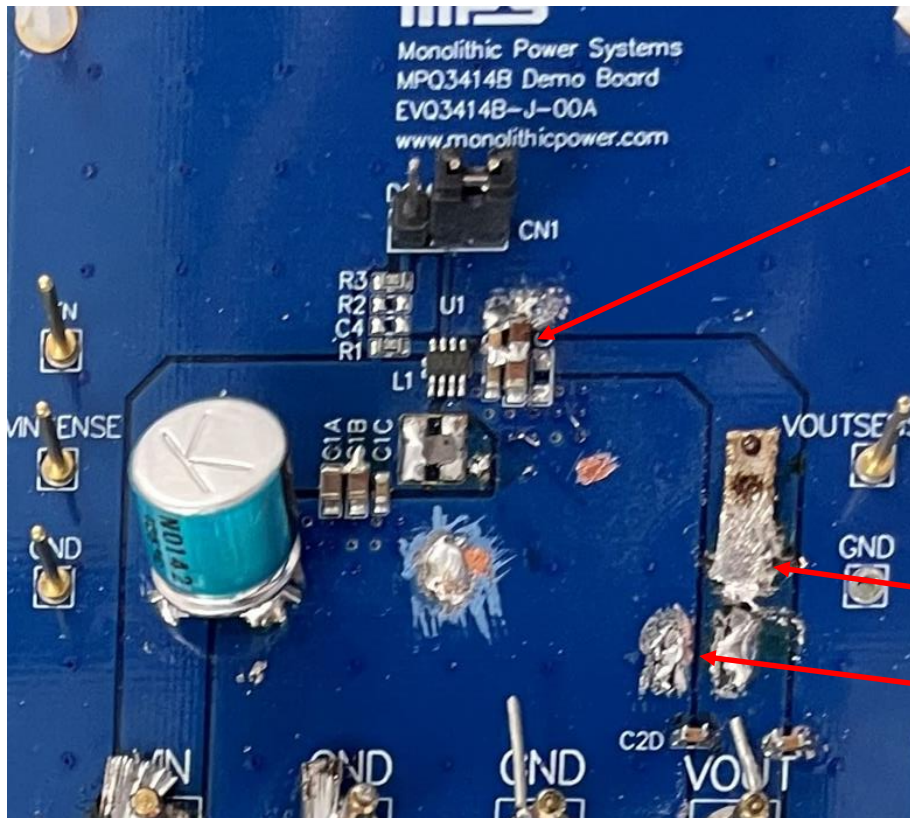As large load resistor (antenna!) is connected directly to the booster output, the first modification was an LC output filter.



Second modification:
 C_{OUT} with semi-symmetric
placement


A small 330nH coil
was placed here.
1 μ F MLCC here.

NO EFFECT! ☹️

Original MPS EV Board and Modified Board

Initial MAPI4020 $I_{RMS} = 8A$ and $8m\Omega$
4mmx4mmx2mm size

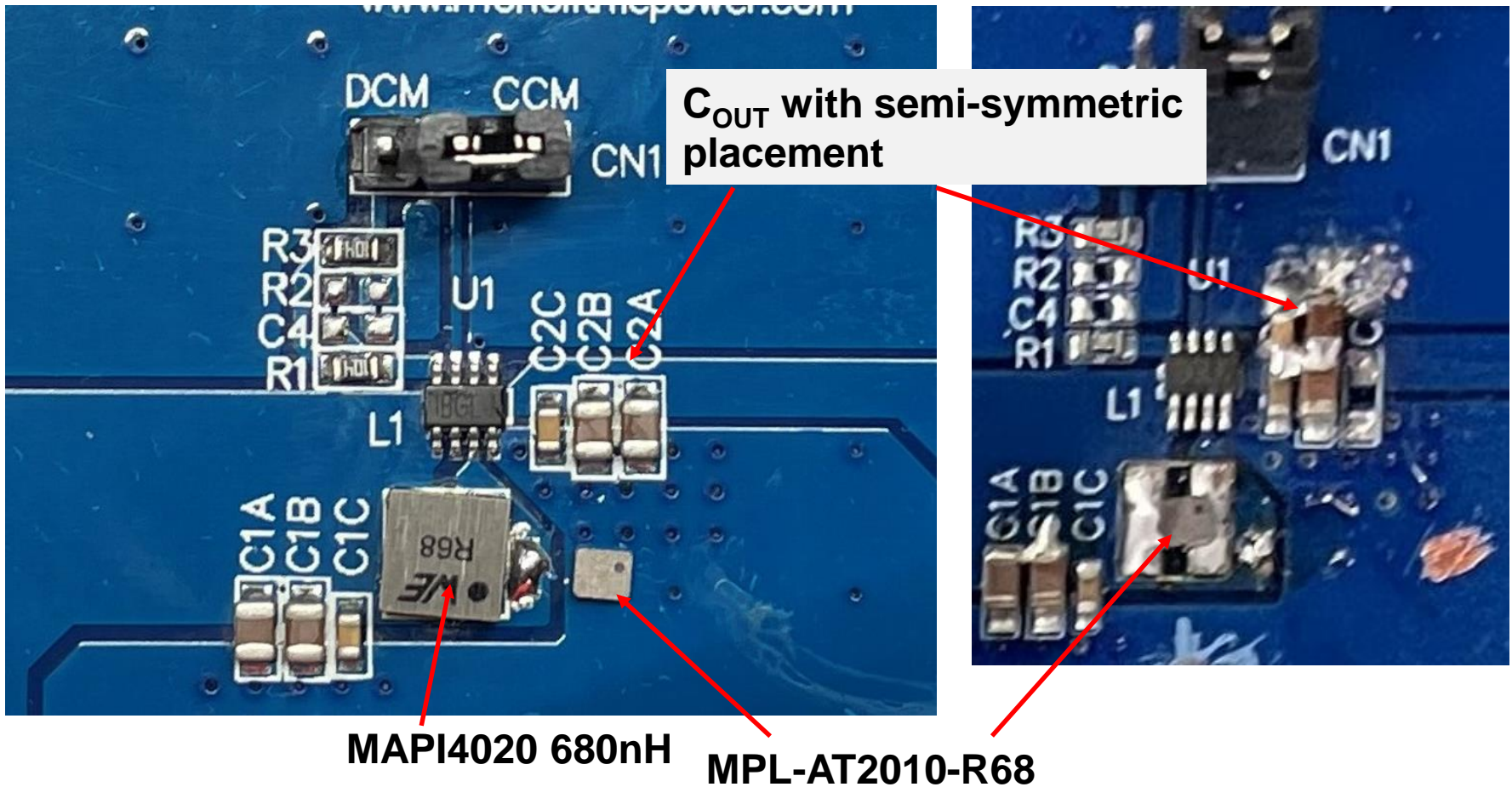
AT2010-R68 2mmx1.6mmx1mm
 $41m\Omega$, $I_{RMS} = 3.5A$, $I_{SAT} = 4.9A$




CE Average Test with OEM Limit

76MHz to 108MHz, BW = 120kHz

3 - VHF

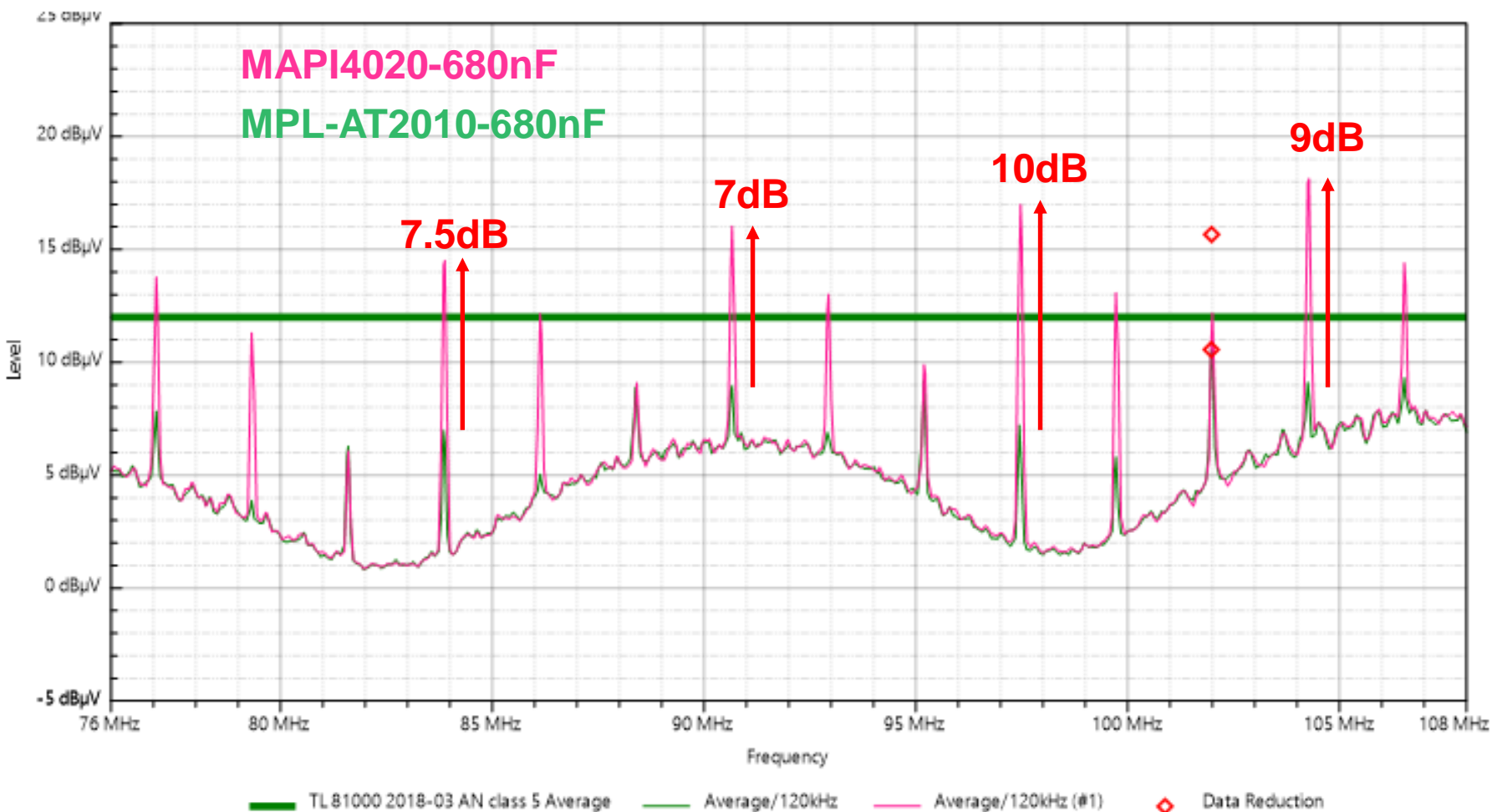

Power Inductors

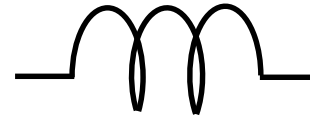

Power inductors share the same schematic symbol...



...but the construction is very different!




The EMC performance also differs a lot!

MPS Case #3: More about Power Inductors & EMC

EMC tests with MPS's 5A buck and a different 10 μ H coil.

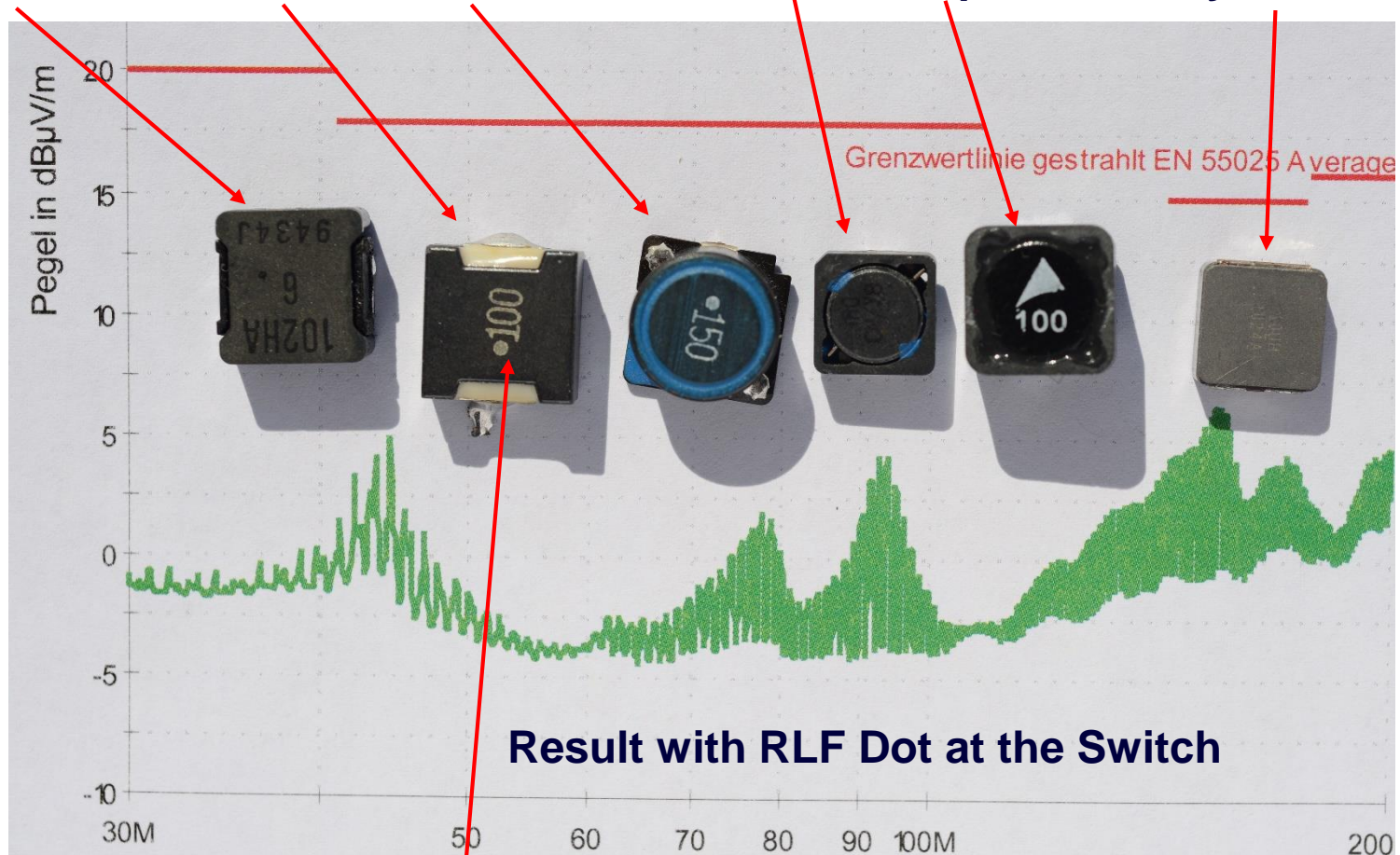
Panasonic, TDK RLF and SLF, Toko D104/124, Epcos, Vishay IHLP4040



The dot on the coil indicates the start of winding (SoW).


More about Power Inductors & EMC

Molded Inductor: WE LHMI 10mmx10mm

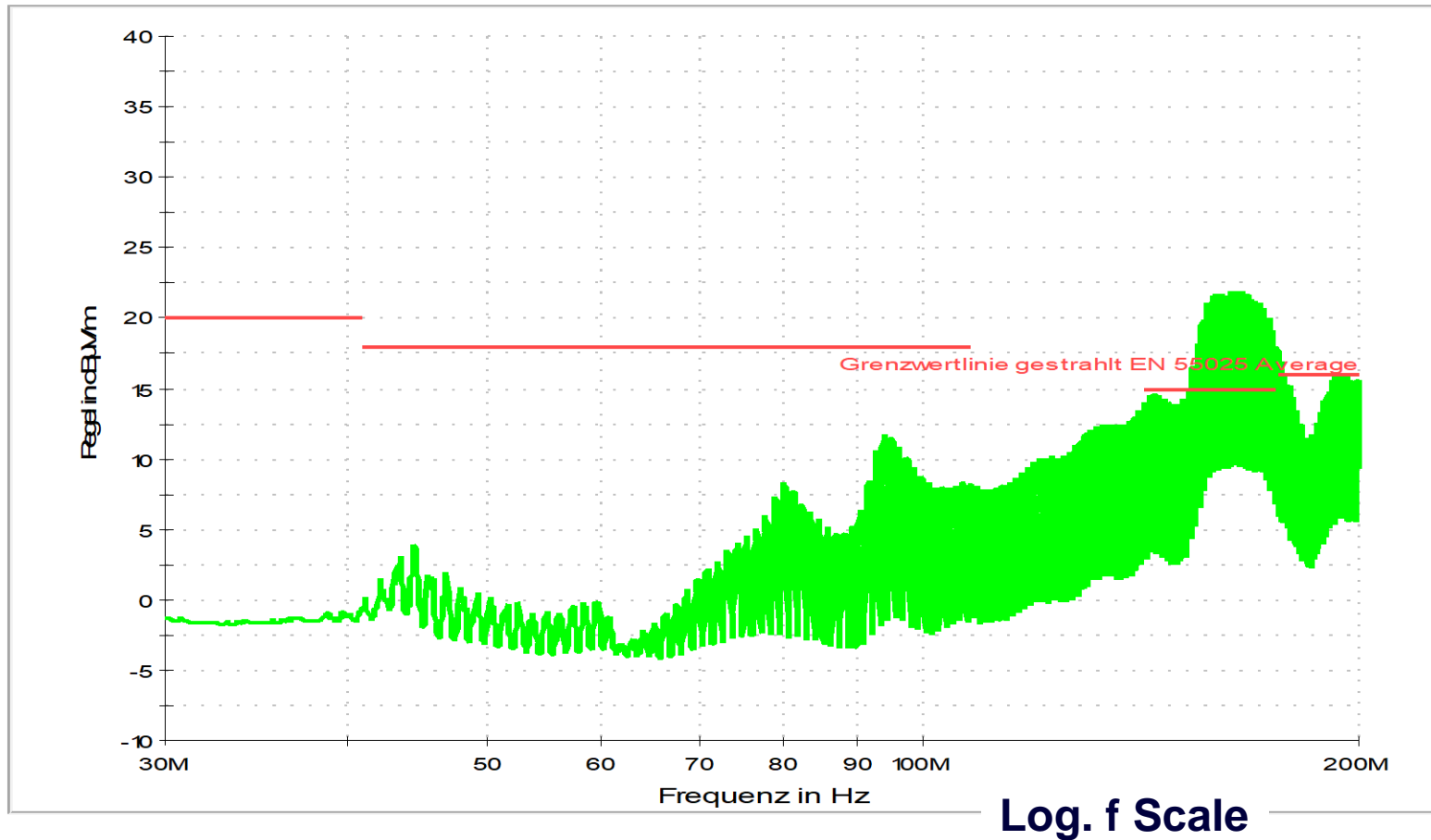

More about Power Inductors & EMC


TDK SLF12575 SoW at the Switch

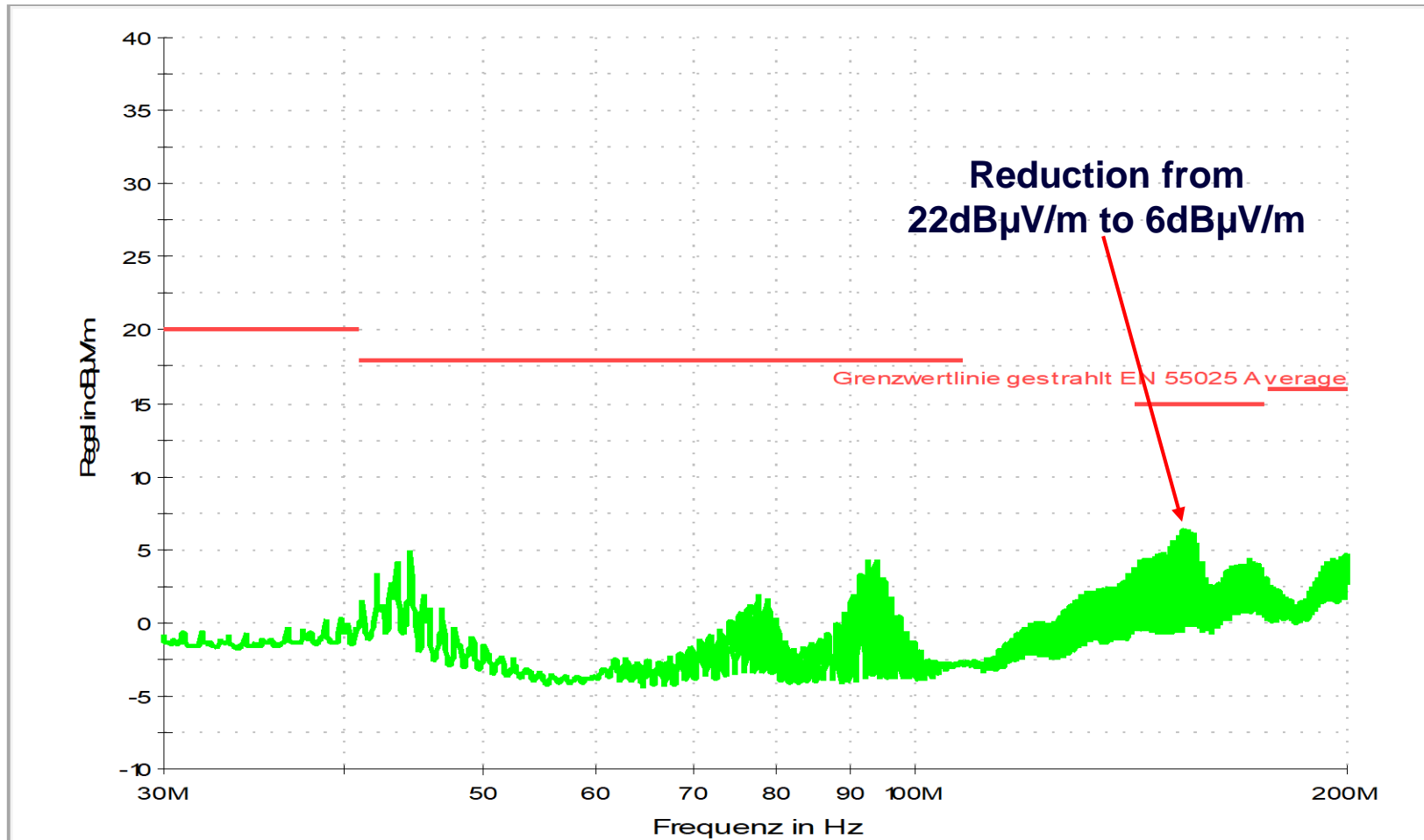

More about Power Inductors & EMC


Epcos coil with an MnZn core **SoW at SW (pink)** and **SoW at V_{OUT} (green)**

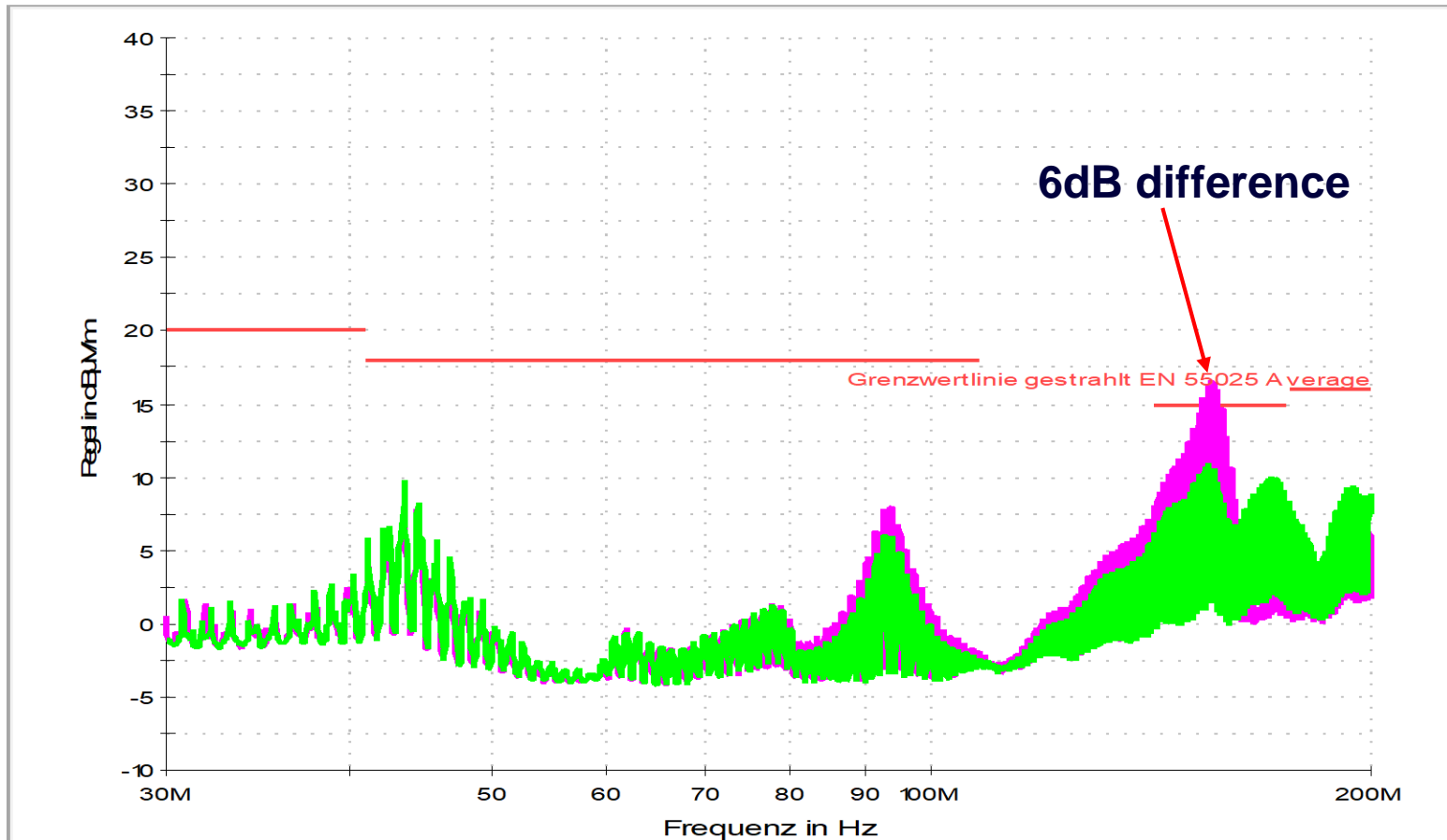The core of this MnZn coil is conductive, this might be the reason for better results with SoW at V_{OUT} .




MPS Case #4: More about Power Inductors & EMC

4.5mm Height

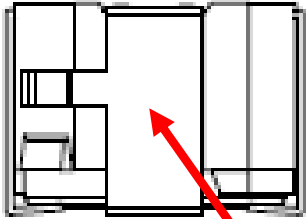

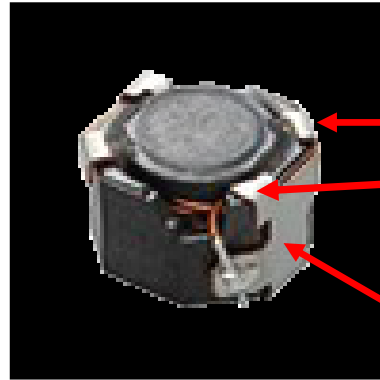
Contact metal acts as an antenna for the E-field from the SW node dV/dt



End-of-winding side contact metal with two clips into airgap for mechanical robustness

Even if the SoW is at SW, the plate will cause trouble

SHAPES AND DIMENSIONS

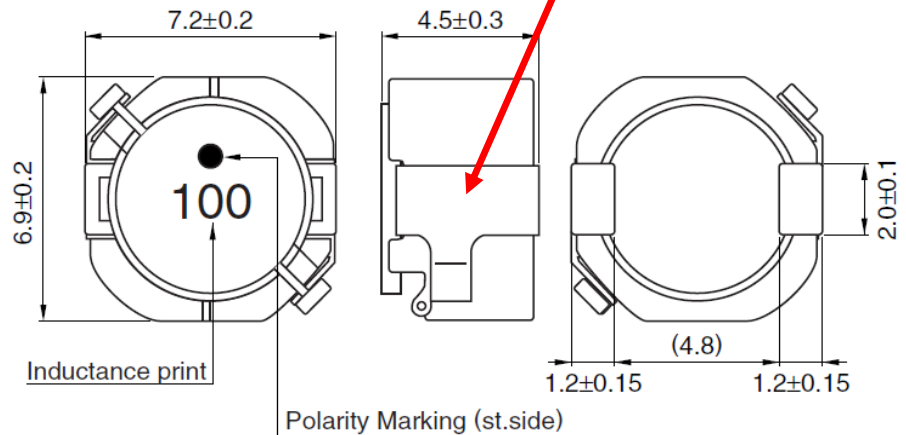


Weight: 0.72g

Dimensions in mm


Example Drawings from Murata, TDK and ABC

More about Power Inductors & EMC

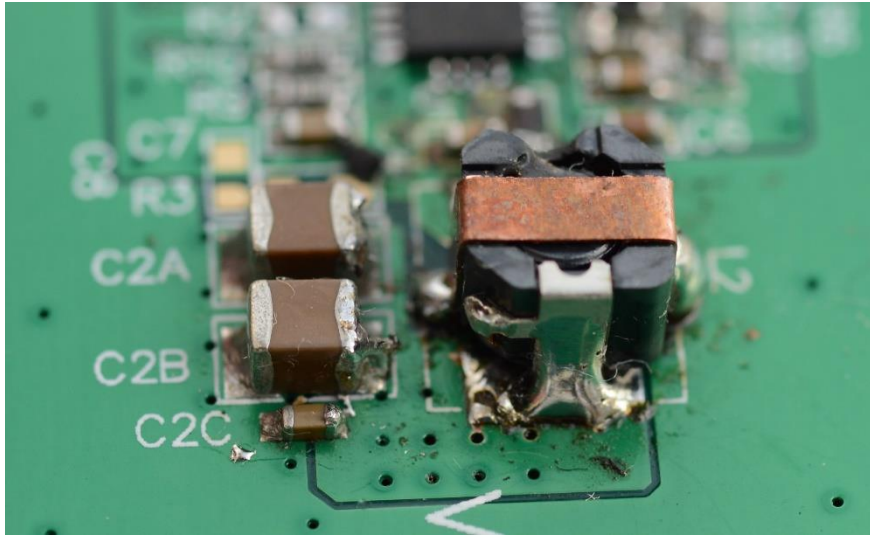


The SW node contact plate has been removed, and the winding is soldered directly to the PCB.

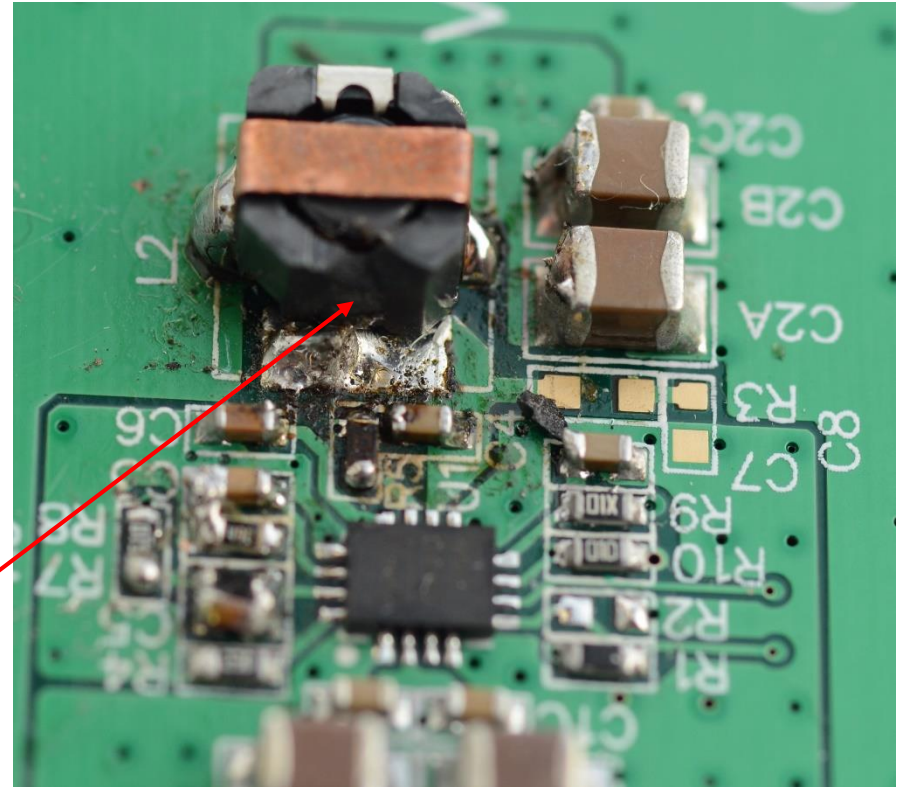6dB lower emissions at 1MHz
in monopole antenna testing




A 4.5mm height contact plate acts as an E-field antenna for the SW node's high dV/dt . The optimum coil should have an SW contact at the bottom.

RE Monopole Test 0.1MHz to 30MHz

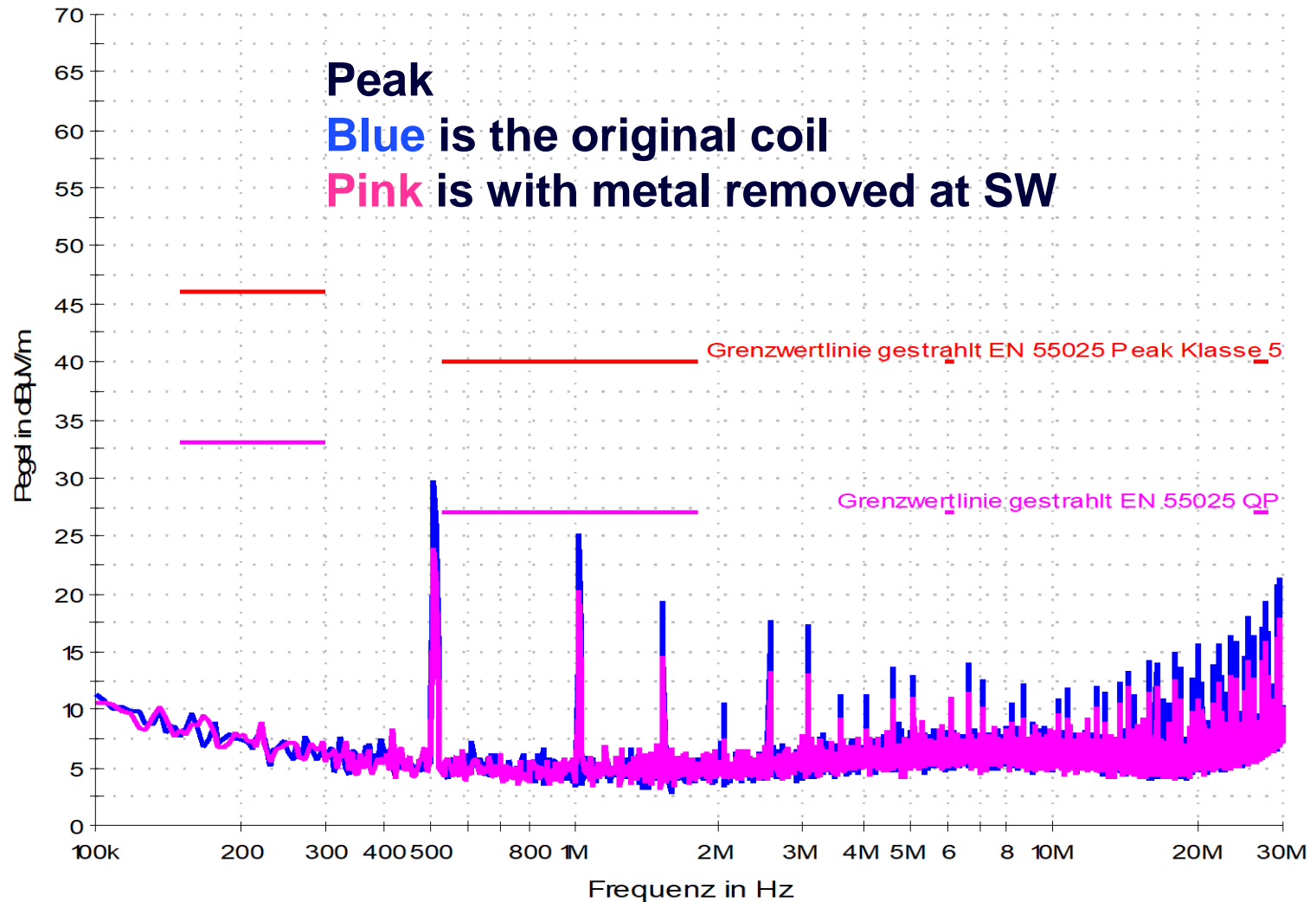


RE Monopole Test 0.1MHz to 30MHz

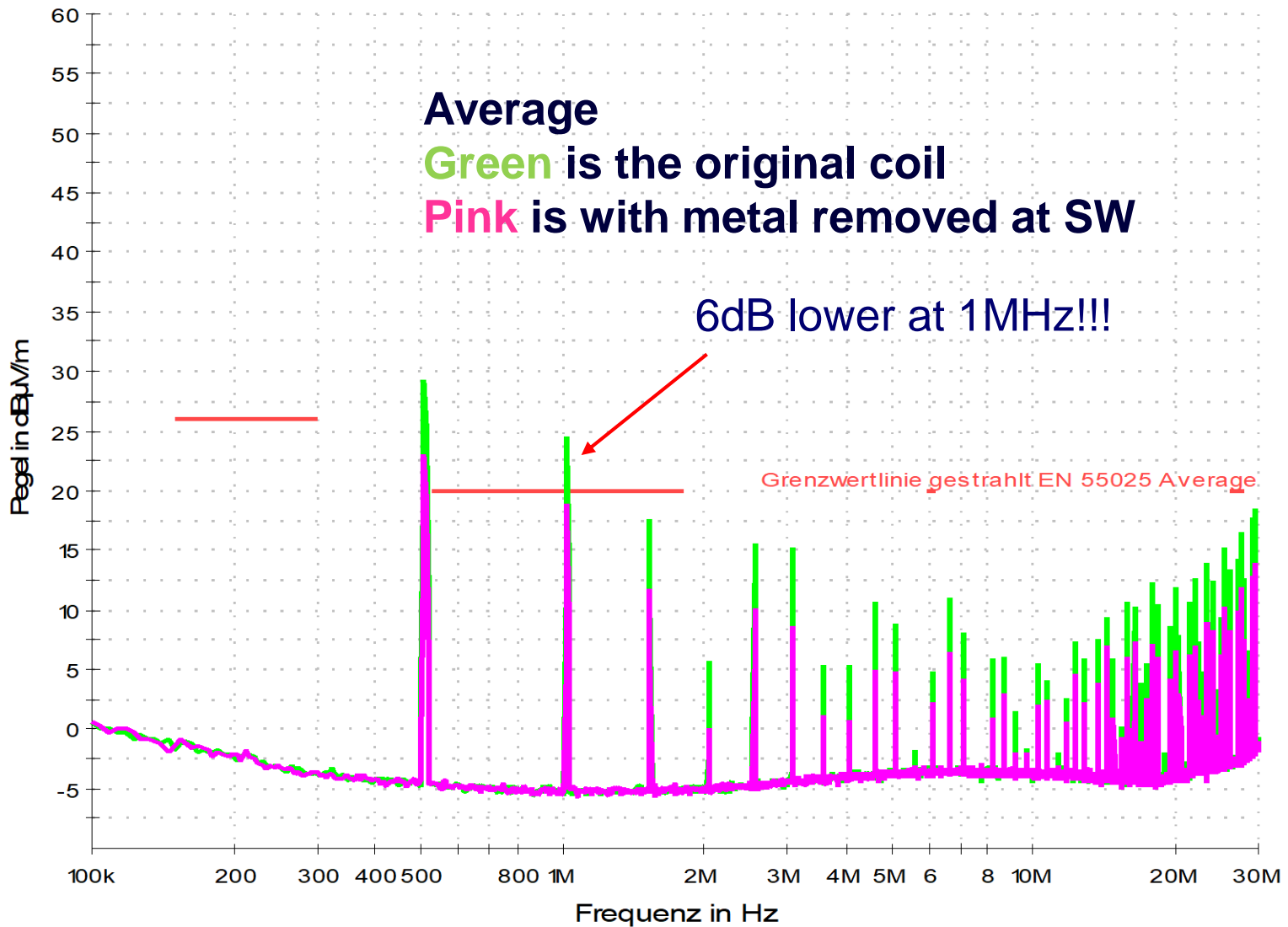

MPS Example #5

Isolated DC/DC, 5W, only average CE is shown

Supply

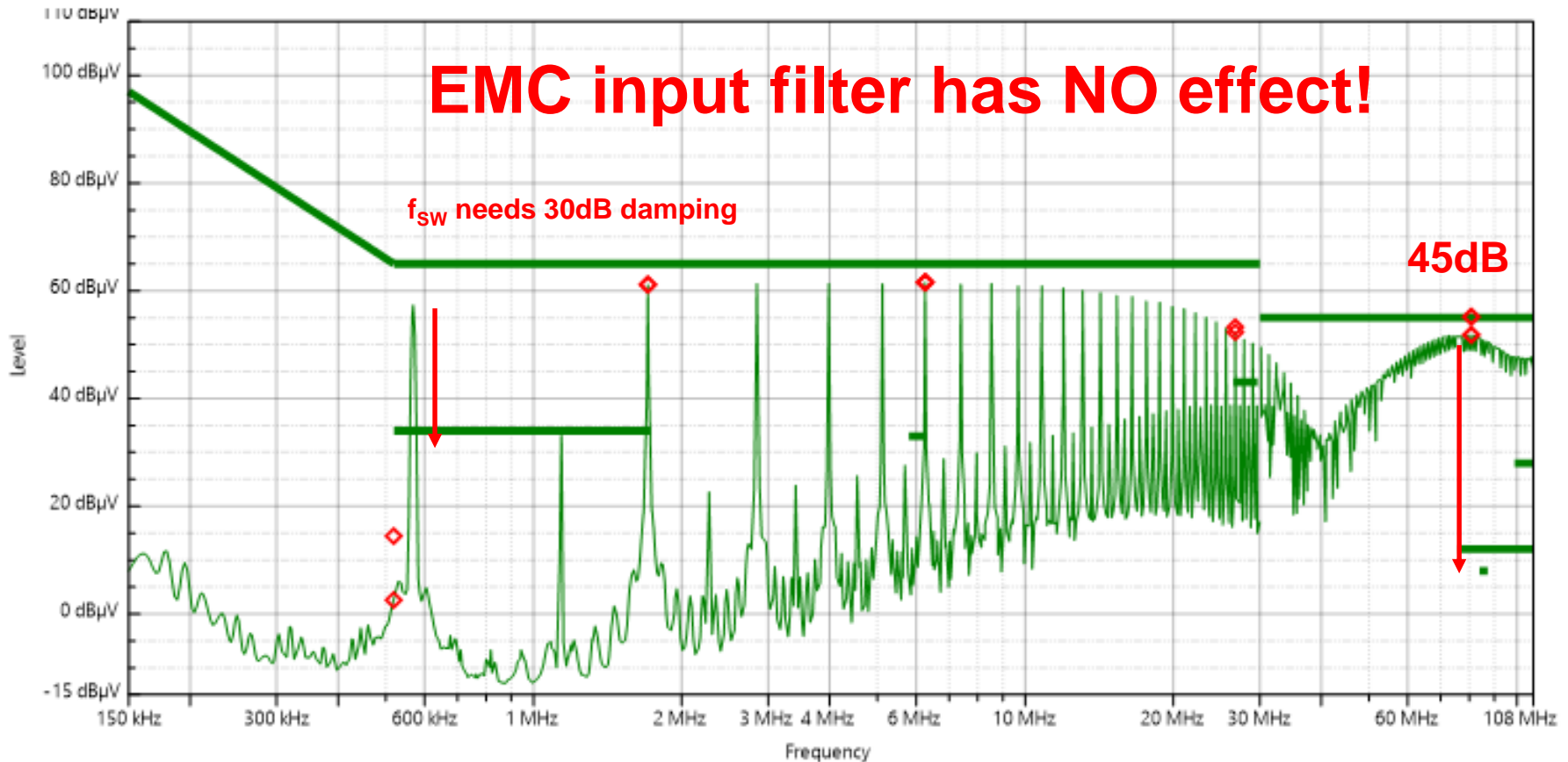

TL 81000 2018-03 AN class 5 Peak
Peak/120kHz

TL 81000 2018-03 AN class 5 Average
Average/9kHz

TL 81000 2018-03 AN class 5 QPeak
Average/120kHz

Peak/9kHz

◇ Data Reduction

MPS Example #5

- Additional tests with snap-on ferrite: no improvement!
- Test with an off-board EMC filter: no improvement!
- Copper foil around the circuit: some improvement!
- Add a Y-capacitor 2.2nF between the primary and secondary GND shows strong improvement
- Additional circuit and layout changes (mainly on the secondary) are needed



Conclusion

- Check the EMC filter structure for effectiveness .
- Review the PCB layout for high di/dt circuit nodes: Loops must be minimized.
- Review the layout and components connected to high dV/dt nodes: High dV/dt area should be small and low-profile.
- Try different inductors. Usually smaller, lower-profile types radiate less.
- If the distance between the DC/DC converter and the cable/connector is too small, use a local shield on top of the DC/DC circuit.