

# Driving Power MOSFETs

Pete Millett

Senior Technical Marketing Engineer

September 2020



# Pete Millett – Senior Technical Marketing Engineer



## 2014–Present

- MPS Senior Technical Marketing Engineer for motor driver ICs
- Responsible for new product definitions as well as application engineering

## 2005–2013

- Systems Engineer and Systems Manager at Texas Instruments
- Product definition and systems engineering for motor driver ICs (DRV8XXX)

## 1982–2005

- Board-level hardware design engineer at various computer and consumer electronics companies

MOSFET Basics




Driving Loads: H-Bridges and Half-H-Bridges

Driving the Gate


Effects of MOSFET Switching Speed

Conclusion


# Power MOSFETs

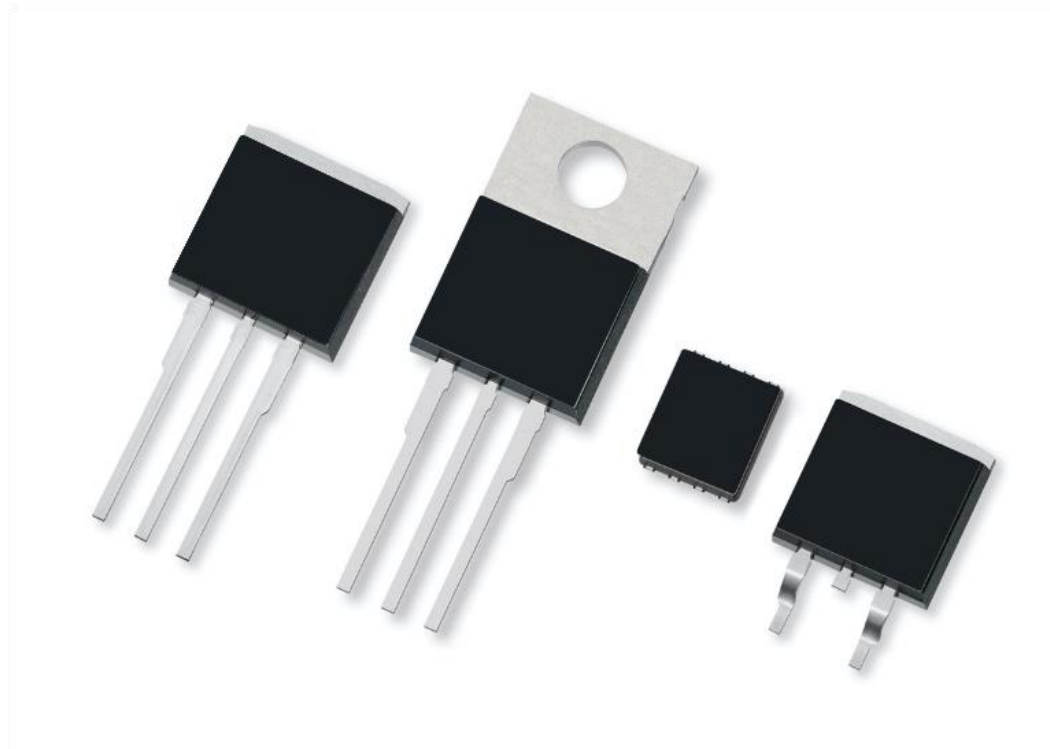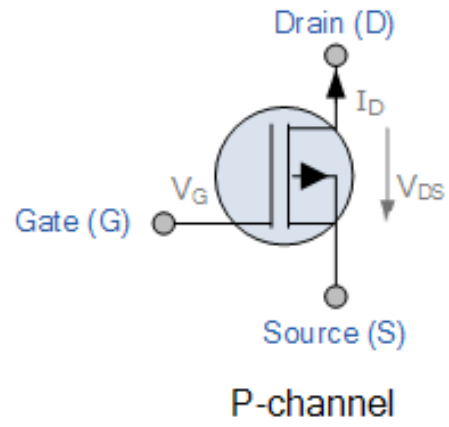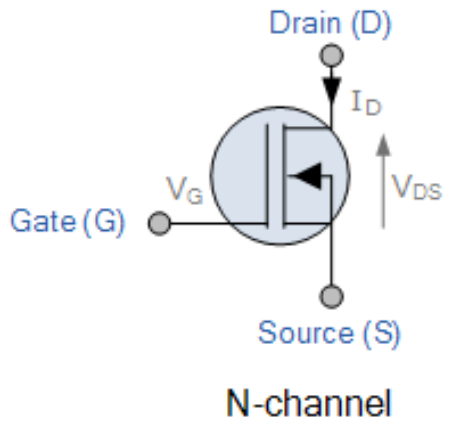


# Power Drive Circuits

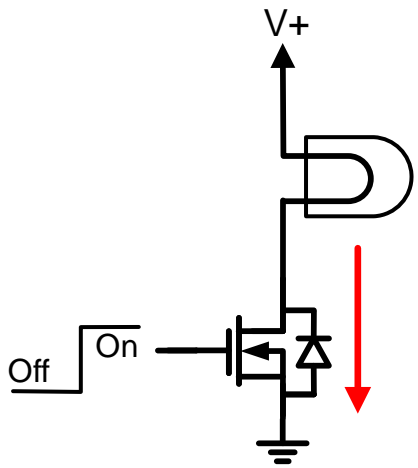

Low side

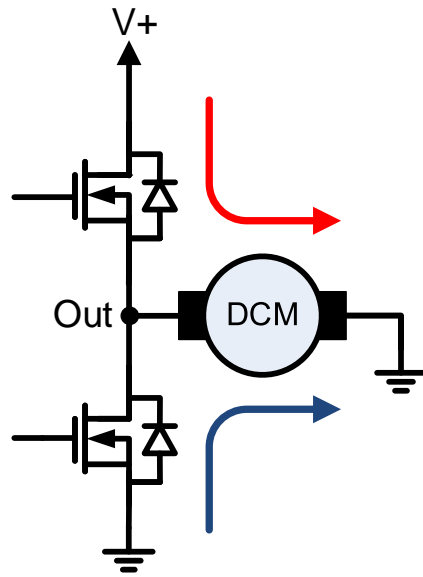



Half Bridge

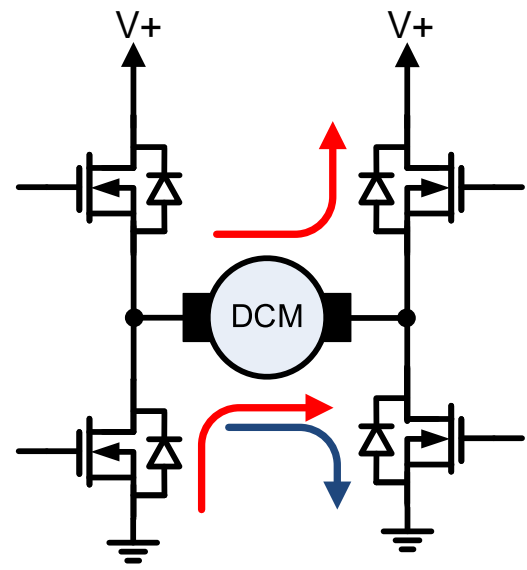

H-Bridge




Red: PWM On  
Blue: PWM Off

# Half Bridges: N and P

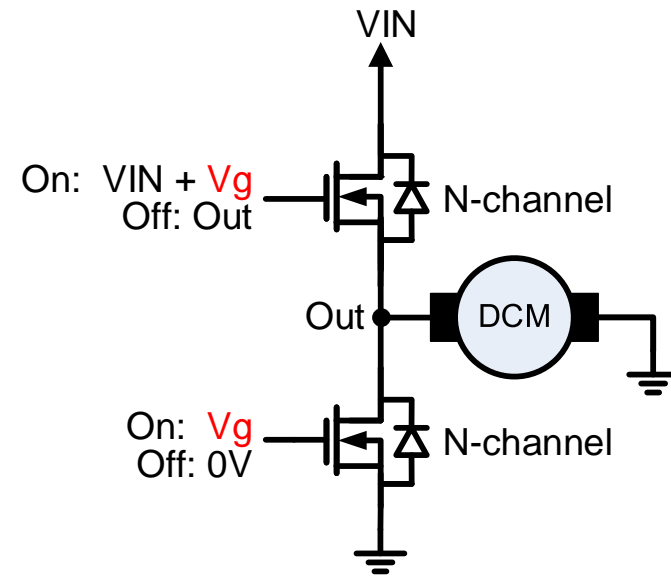
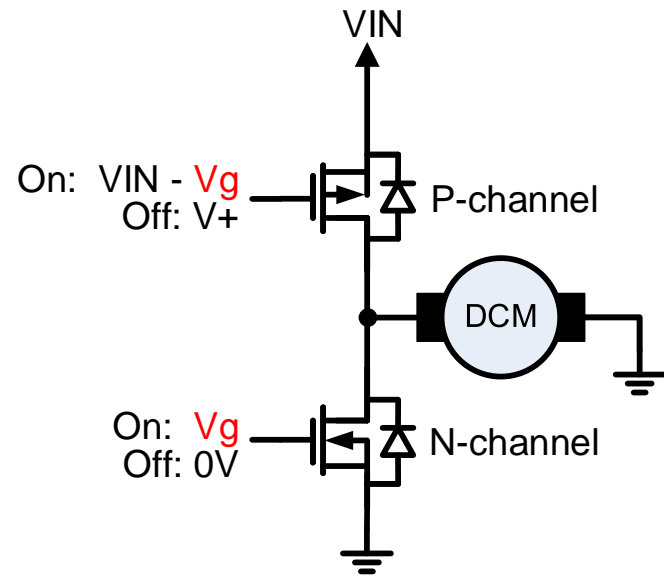


$V_{IN}$  – Load Supply Voltage  
 $V_g$  – Gate Drive Voltage

# MOSFET Structure

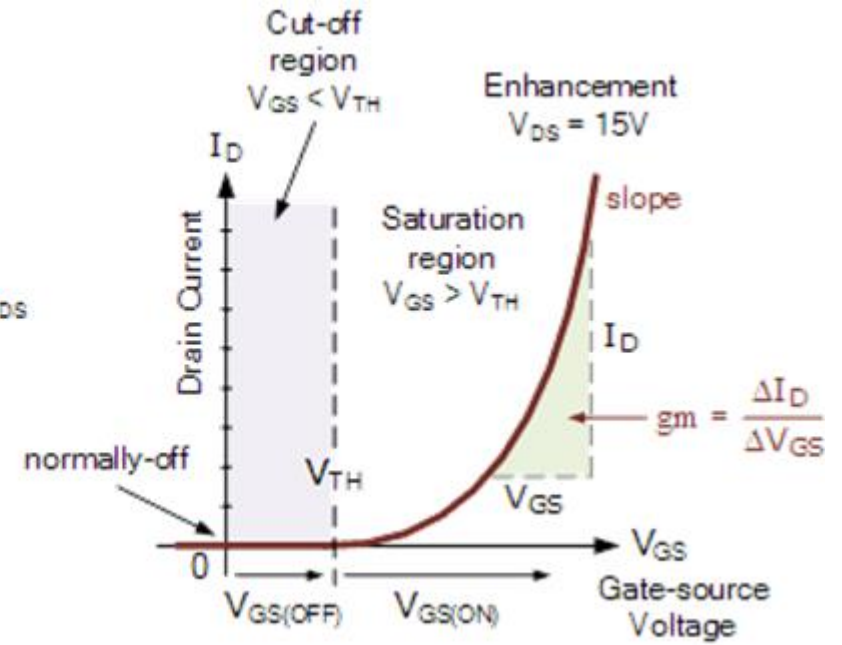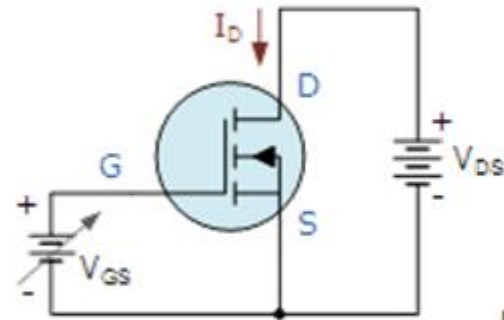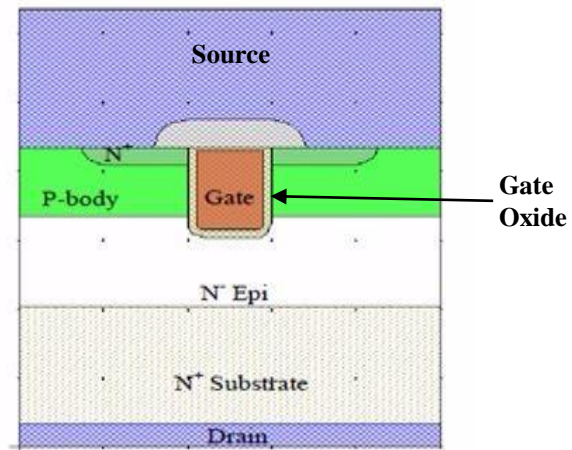
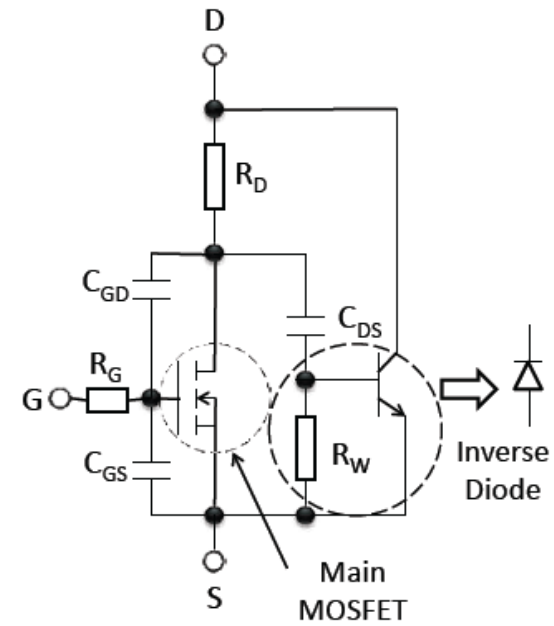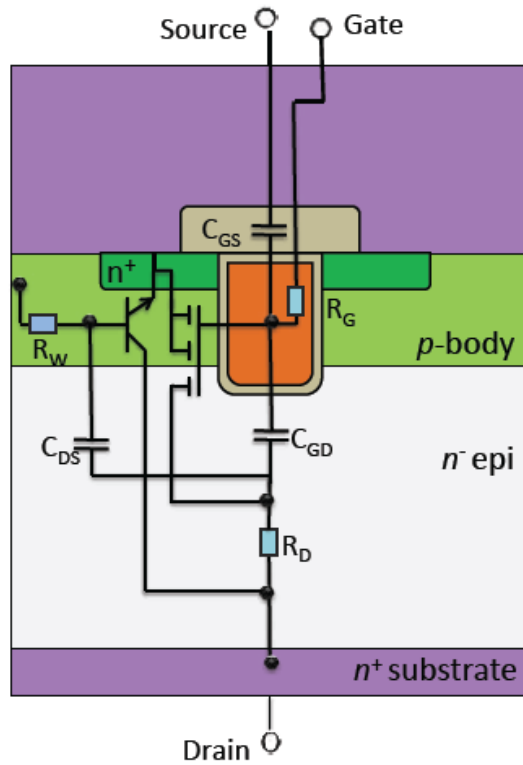
# Simplified Model of an N-channel Power MOSFET





# Datasheet Specs and Total Gate Charge

1 Coulomb =  $6.28 \times 10^{18}$  Electrons

that is:

**6,280,000,000,000,000,000**  
ELECTRONS

$Q = CV$  (Charge = Capacitance x Voltage)

$I = Q/t$  (Current = Charge / Time)


## IPP015N04N

VDS max	40.0 V
RDS (on) (@10V)	max 1.5 mΩ
ID (@25°C) max	120.0 A
Ptot max	250.0 W
Ciss	15000.0 pF
Coss	4000.0 pF
QG (typ @10V)	188.0 nC
VGS(th) min / max	2.0 V / 4.0 V

$C_{ISS}$  – Input capacitance  
(gate-to-source + gate-to-drain)

$Q_G$  – Total gate charge



# Driving the Gate

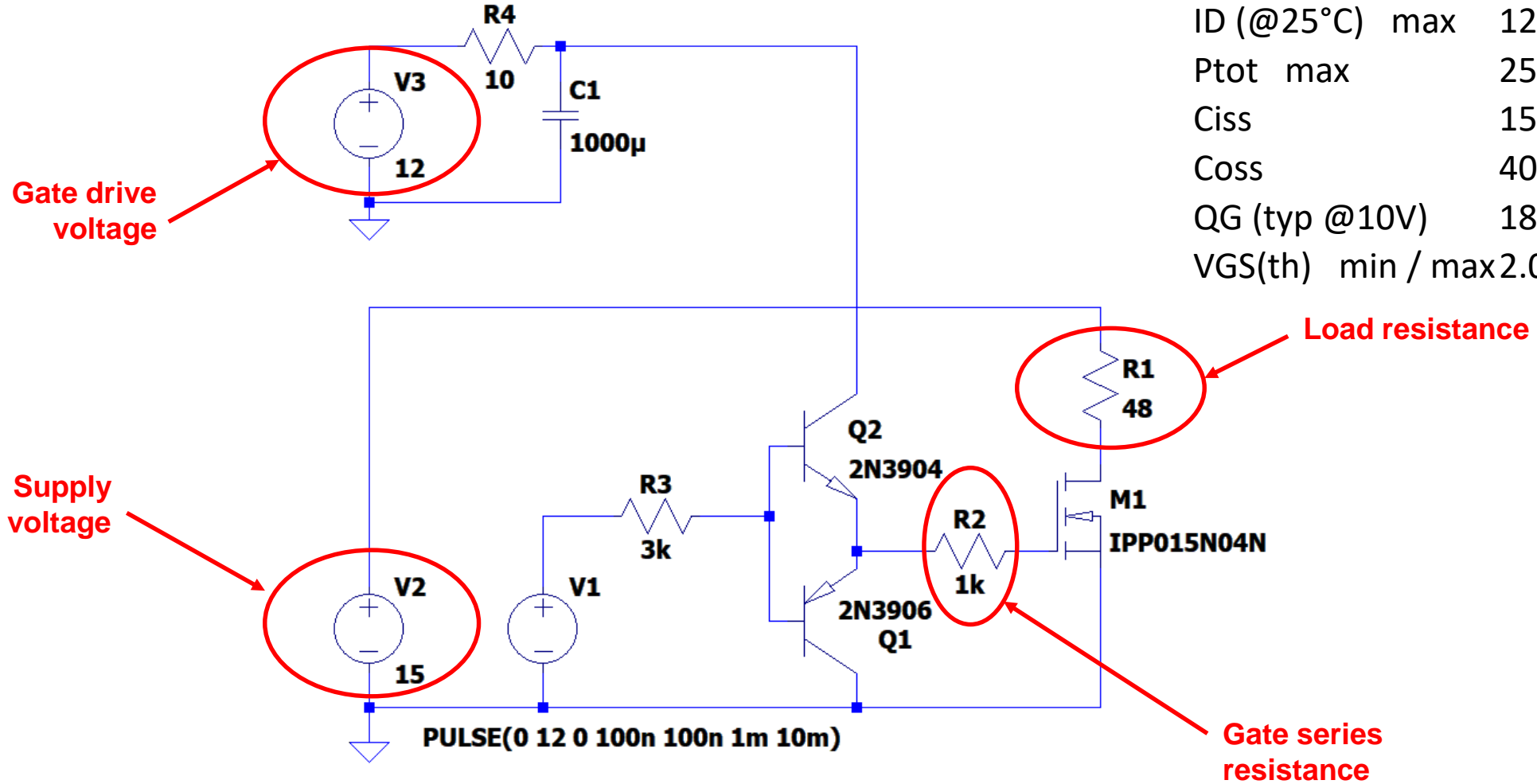

## IPP015N04N



VDS max	40.0 V
RDS (on) (@10V)	max 1.5 mΩ
ID (@25°C) max	120.0 A
Ptot max	250.0 W
Ciss	15000.0 pF
Coss	4000.0 pF
QG (typ @10V)	188.0 nC
VGS(th) min / max	2.0 V / 4.0 V

# Low Resistance Gate Drive

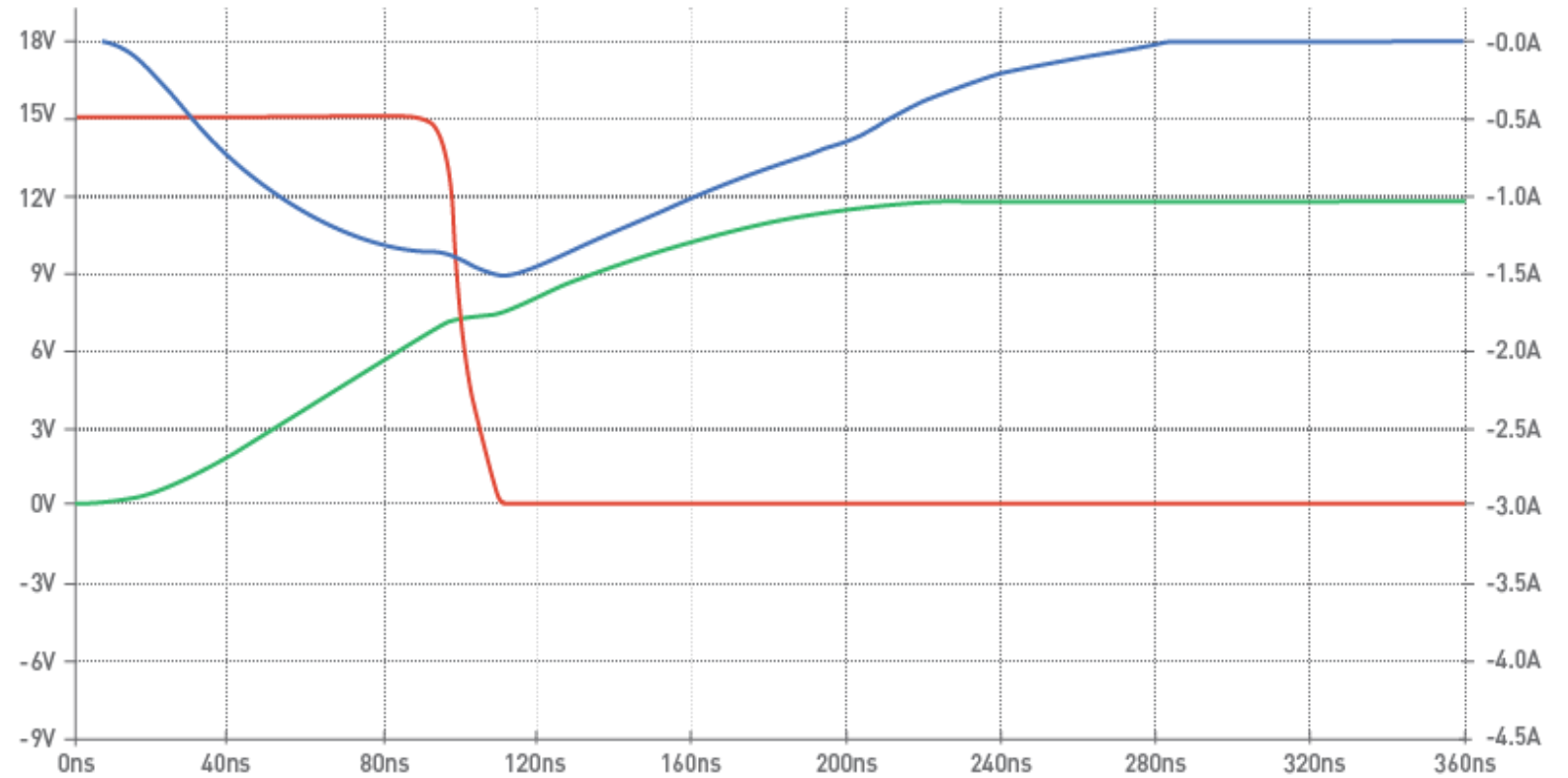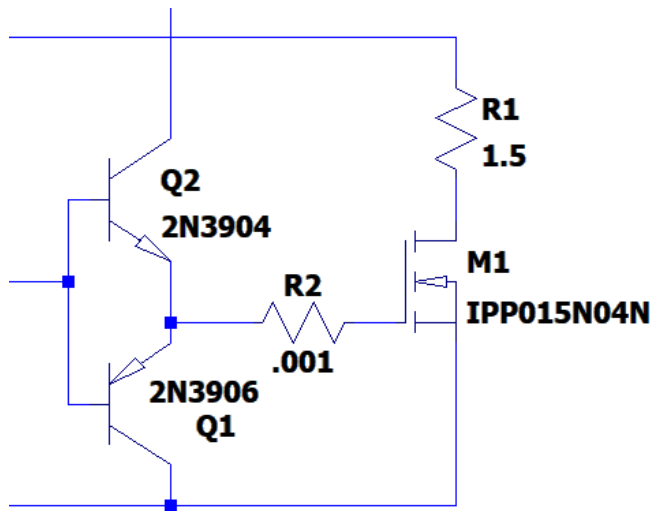



Red: Drain Voltage  
Green: Gate Voltage  
Blue: Gate Current

# Low Resistance Gate Drive

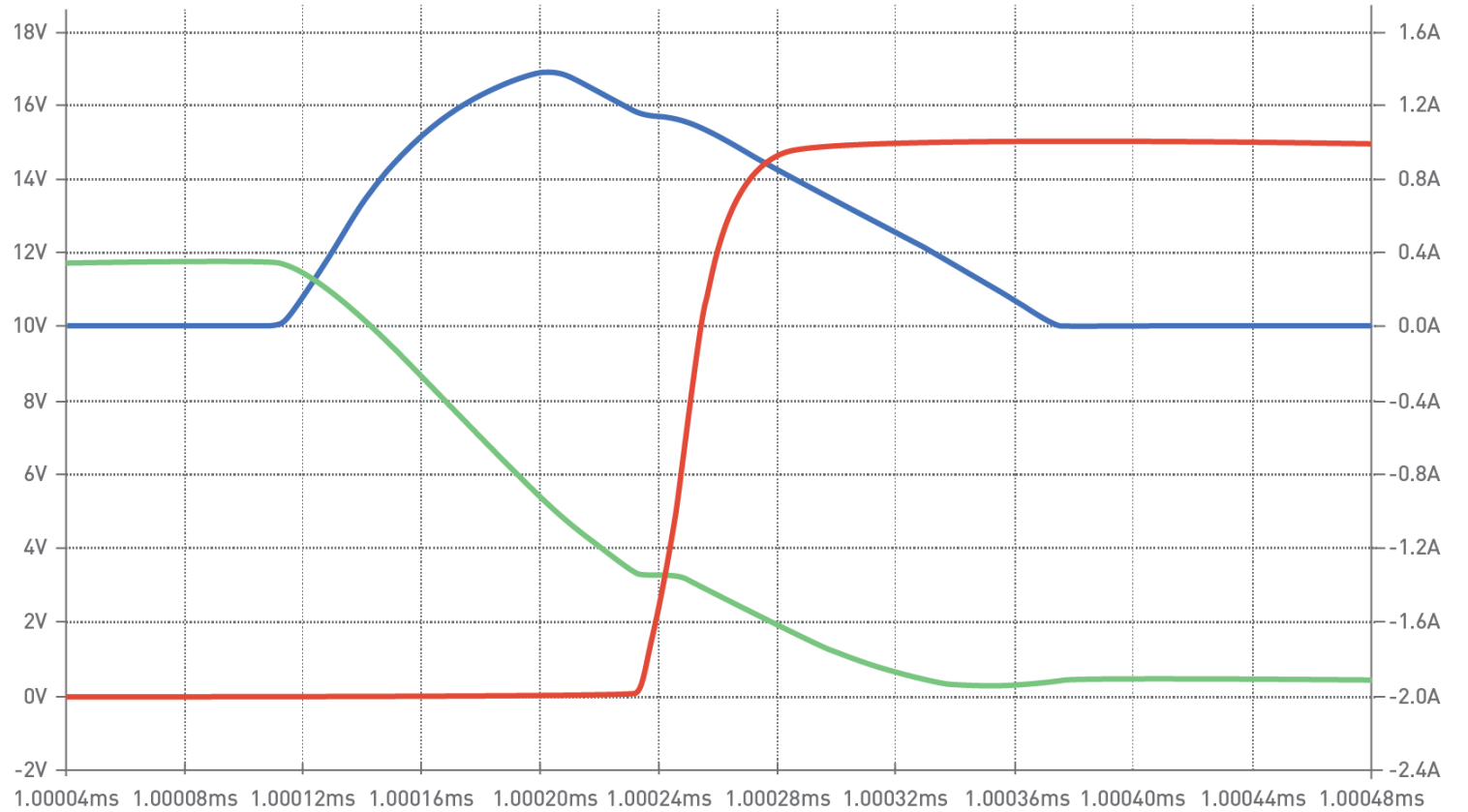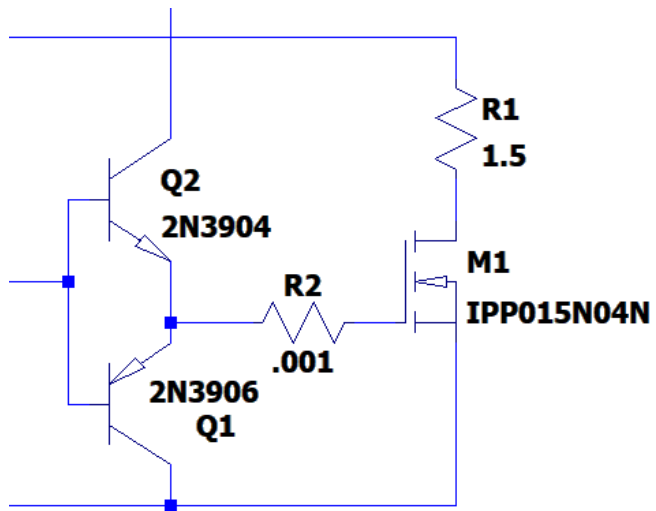



**Red: Drain Voltage**  
**Green: Gate Voltage**  
**Blue: Gate Current**

# Adding Series Resistance

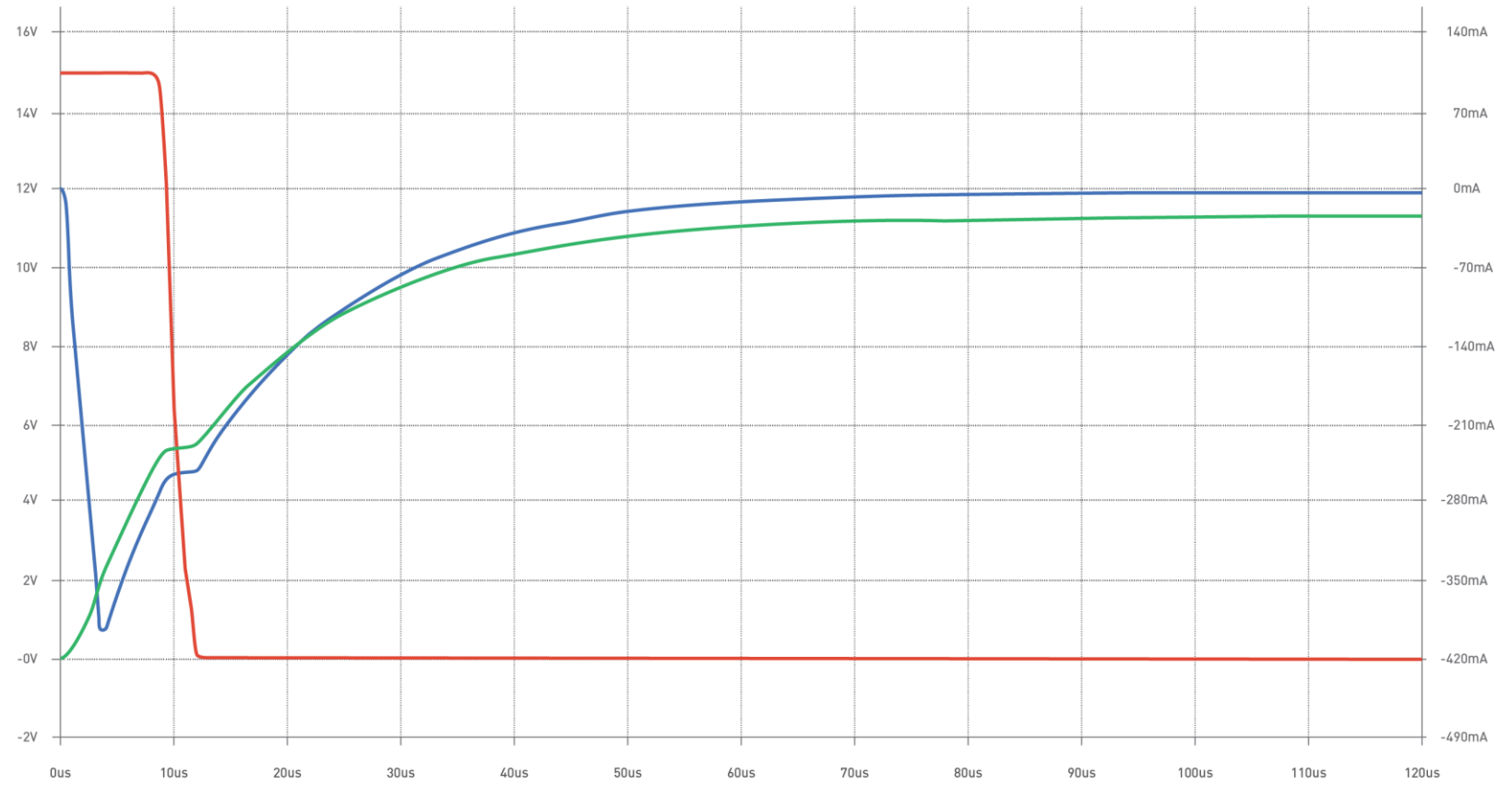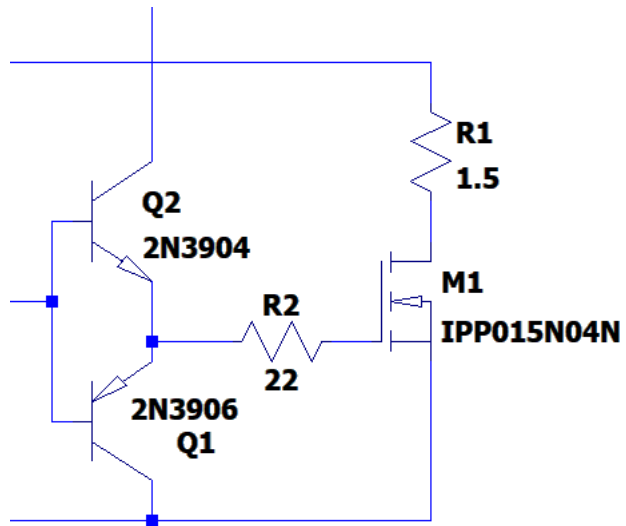



Red: Drain Voltage  
Green: Gate Voltage  
Blue: Gate Current

# Adding Series Resistance

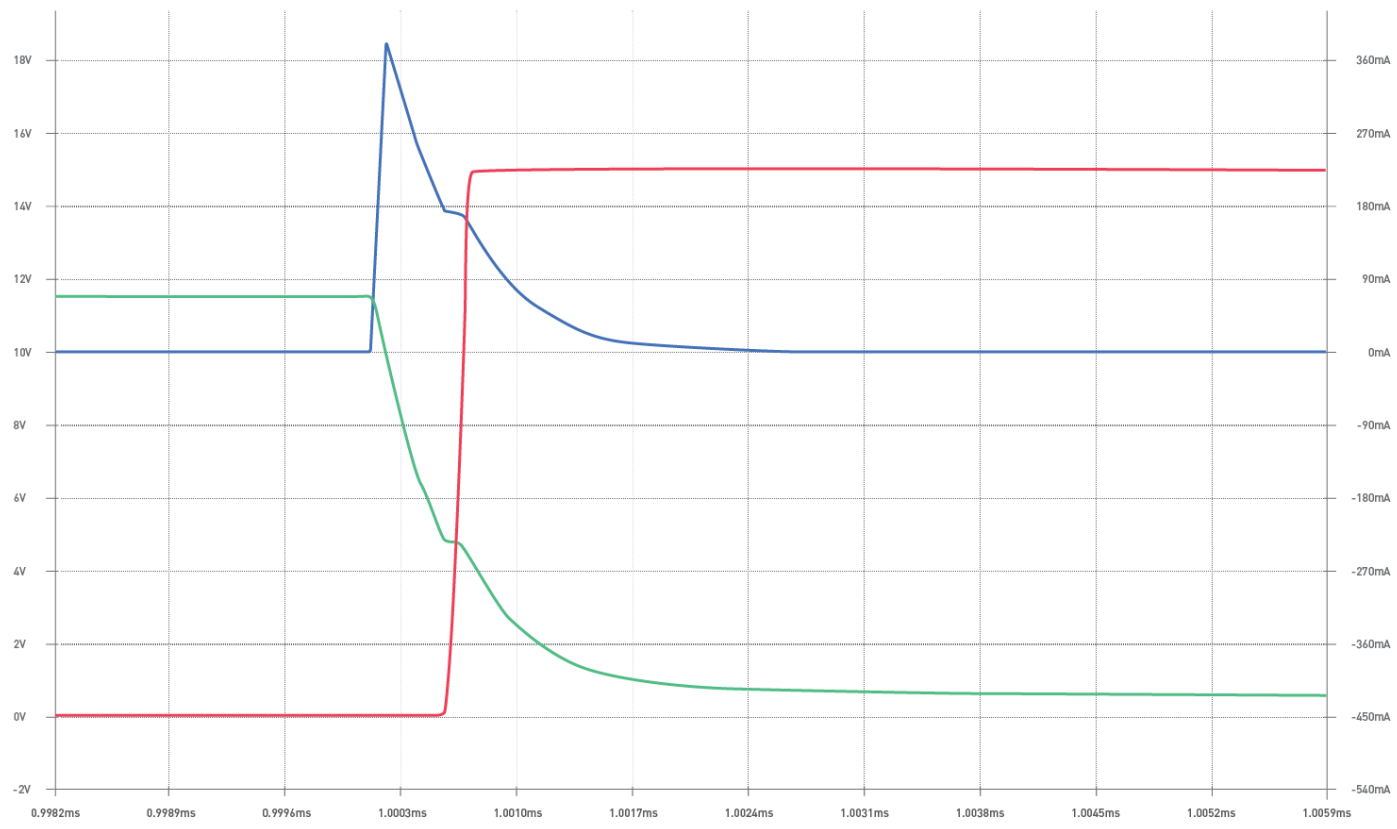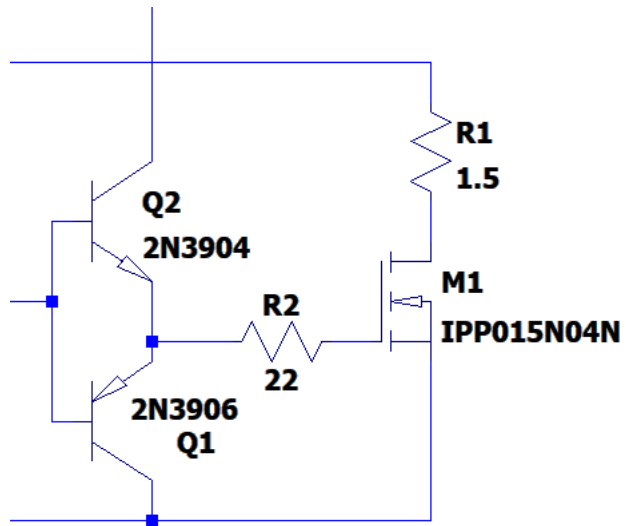



**Red: Drain Voltage**  
**Green: Gate Voltage**  
**Blue: Gate Current**

# Too Much Series Resistance?

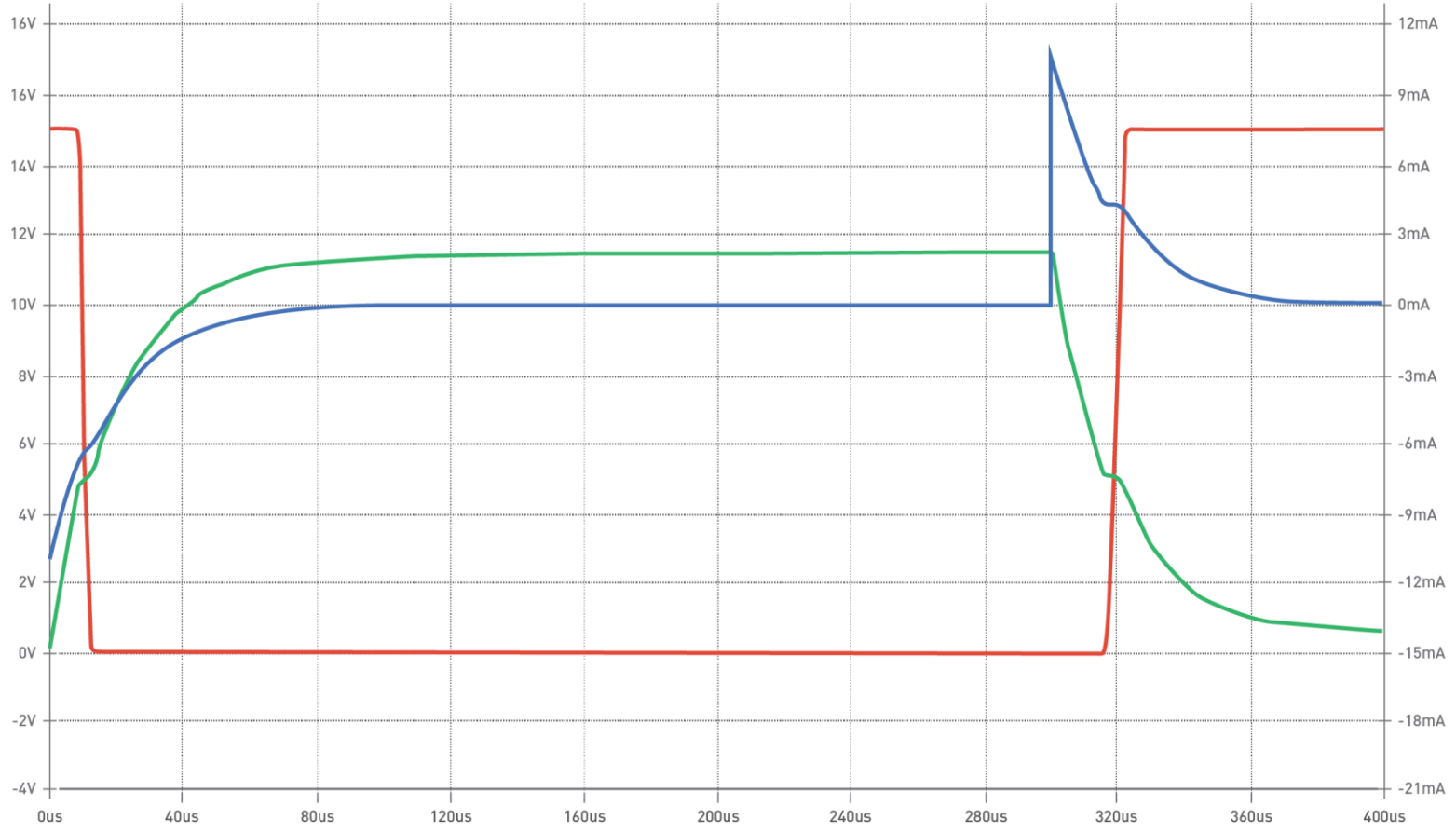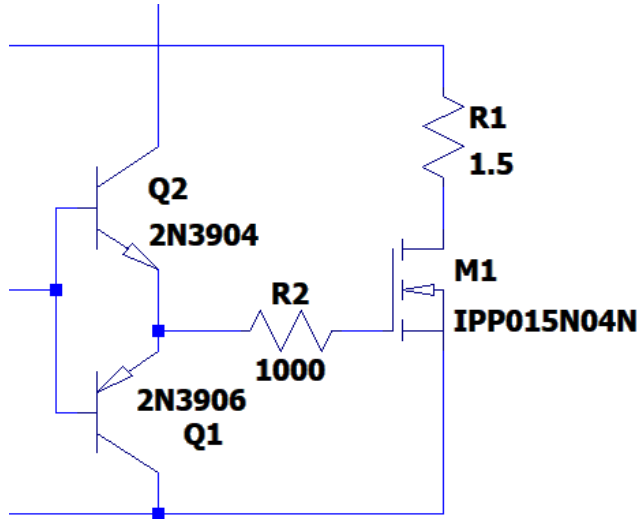

Red: Drain Voltage  
Green: Gate Voltage  
Blue: Gate Current



# Too Much Series Resistance?

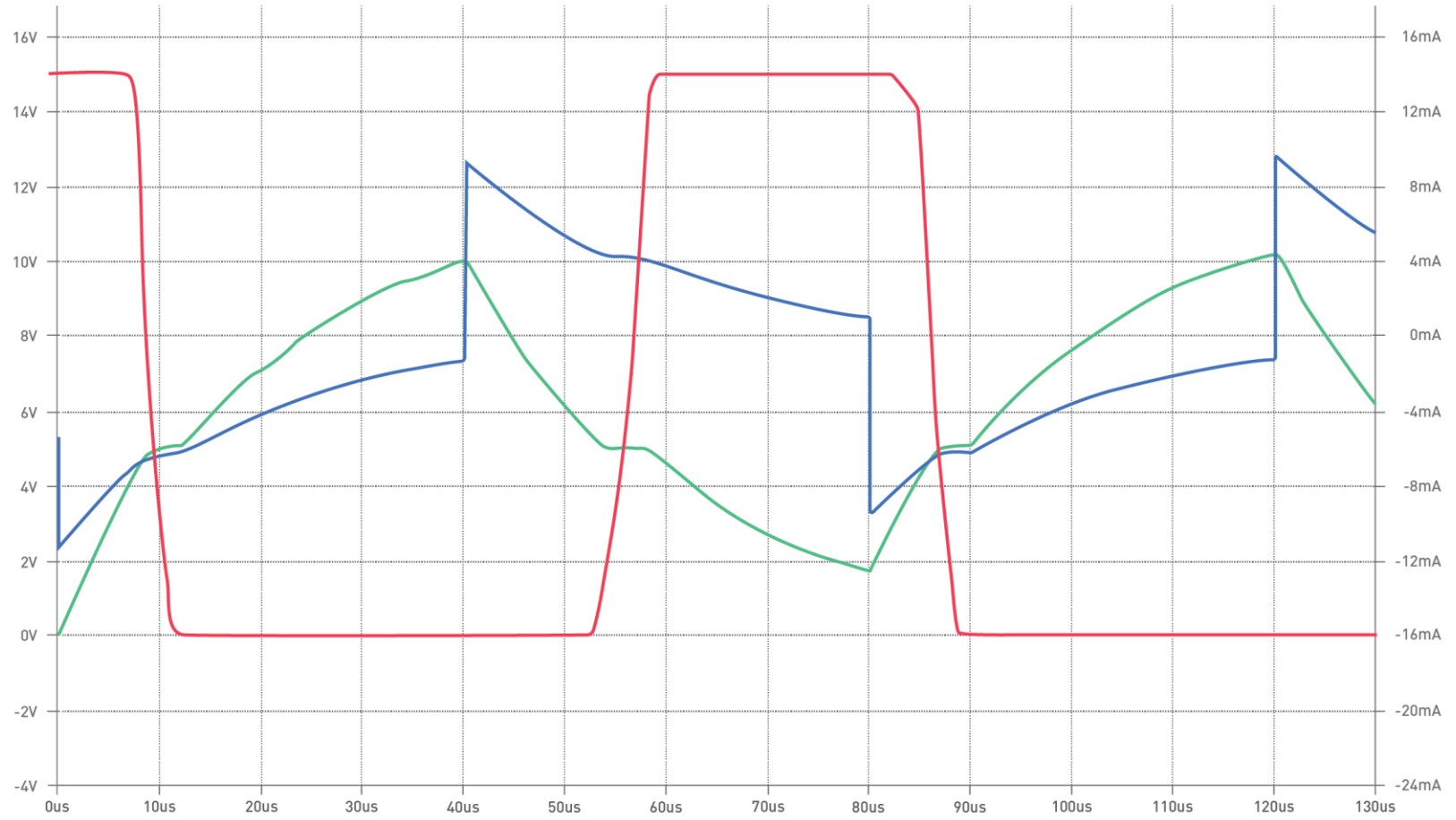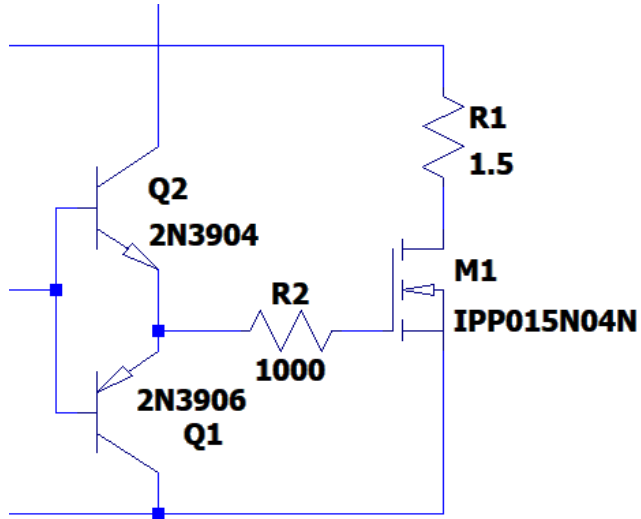

Red: Drain Voltage  
Green: Gate Voltage  
Blue: Gate Current





# False Turn-On

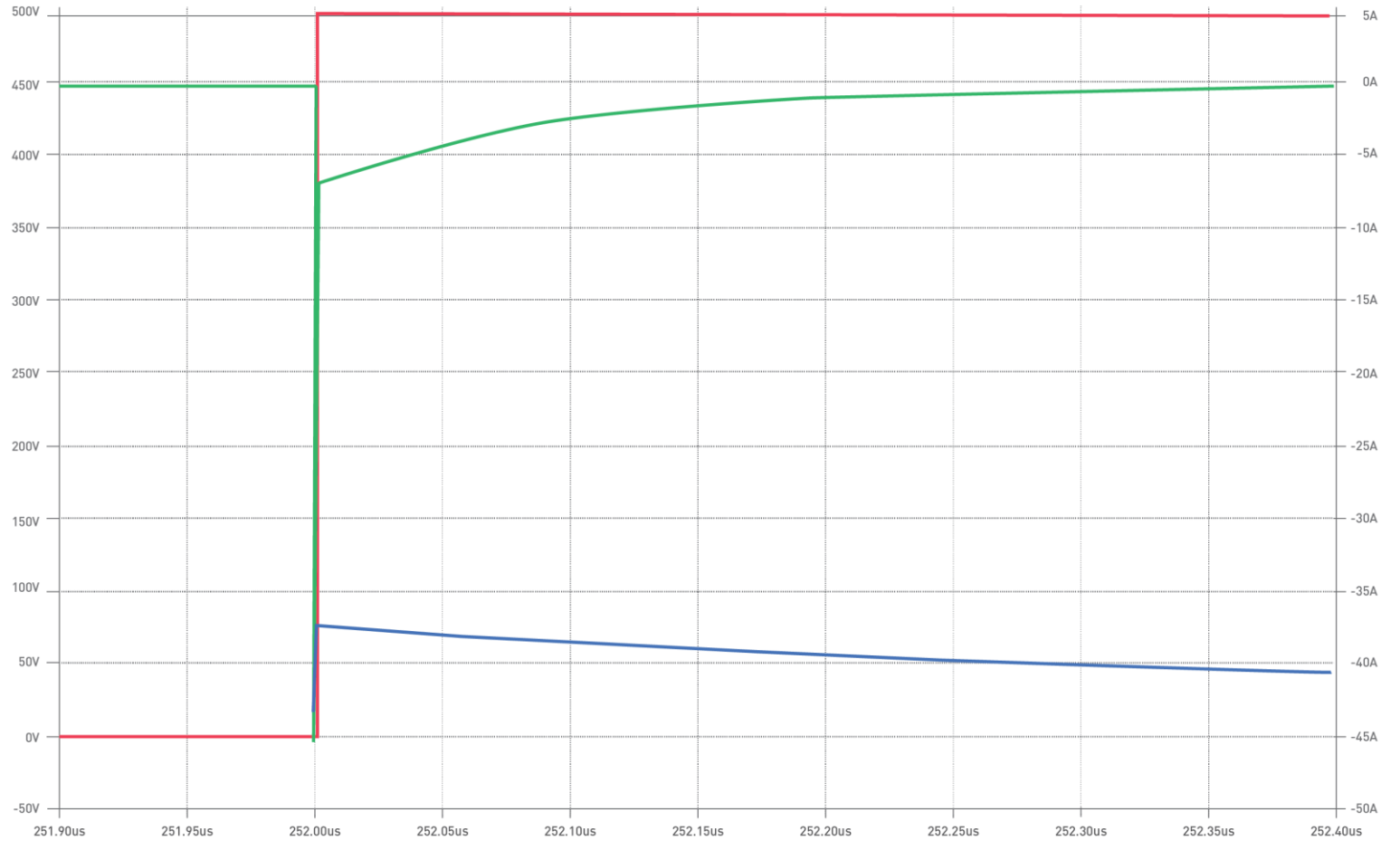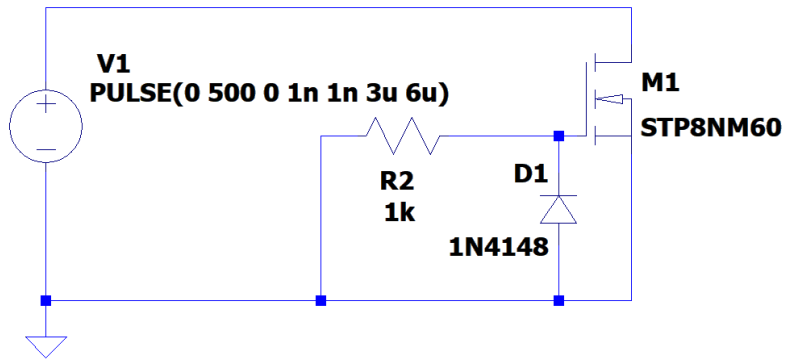


Red: Drain Voltage  
Blue: Gate Voltage  
Green: Drain Current

# Asymmetric Gate Drive

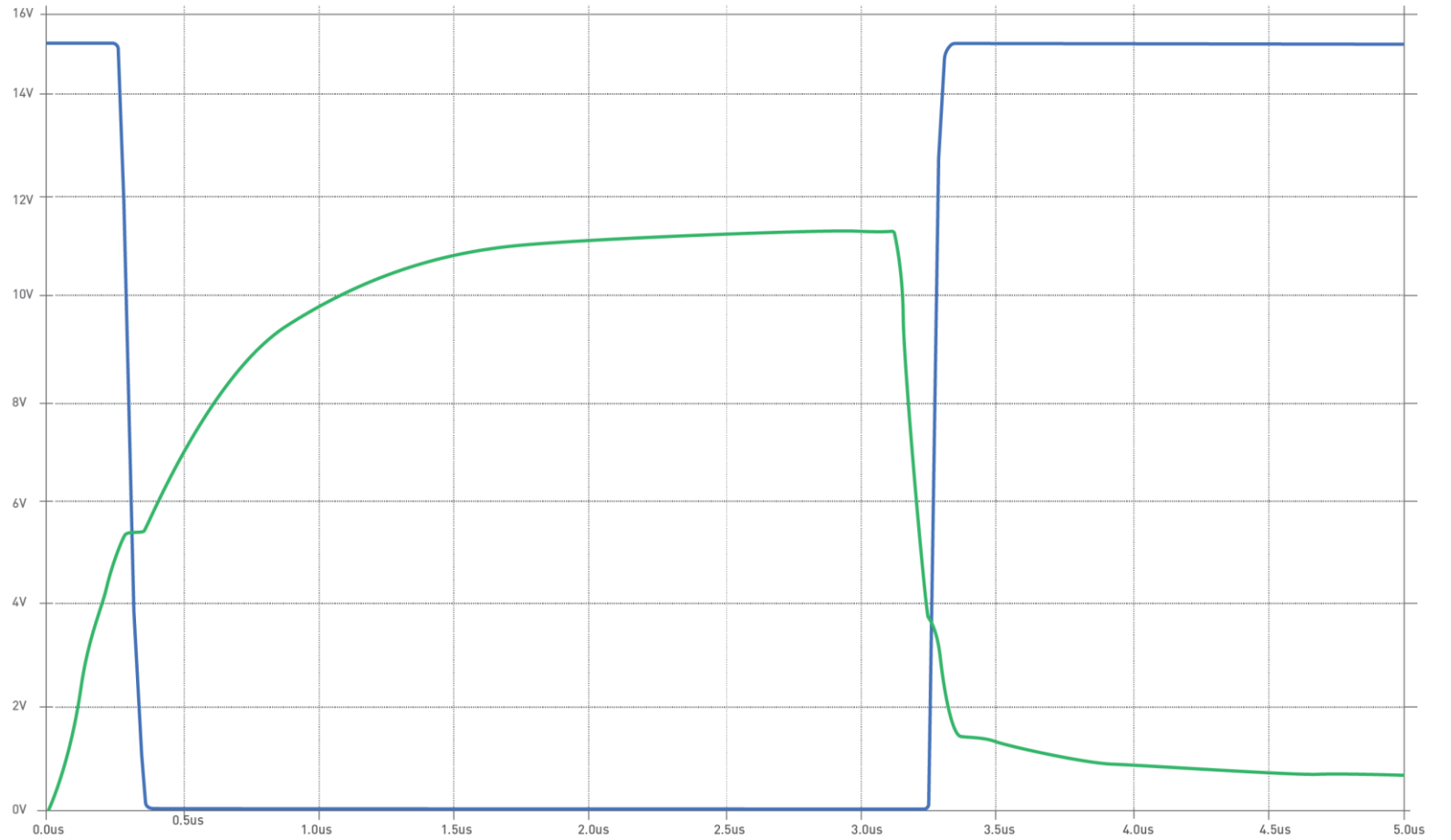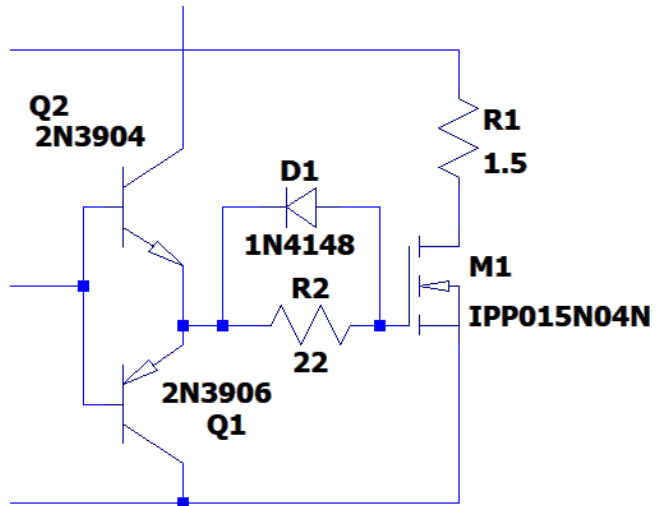



Blue: Drain Voltage  
Green: Gate Voltage

# MOSFET Switching Speed

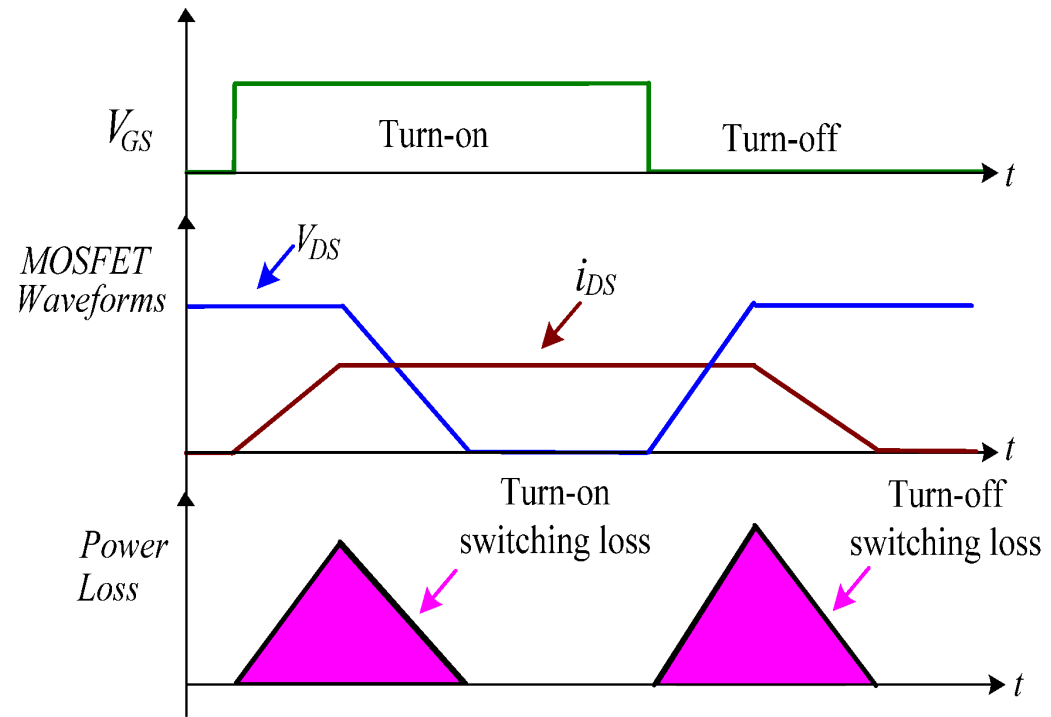


(a)

# Why Slow the Gate Down?

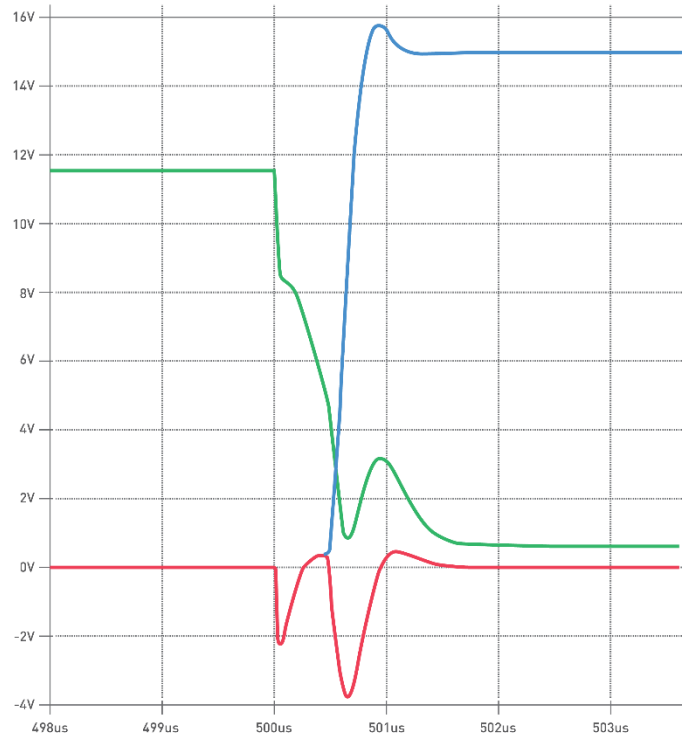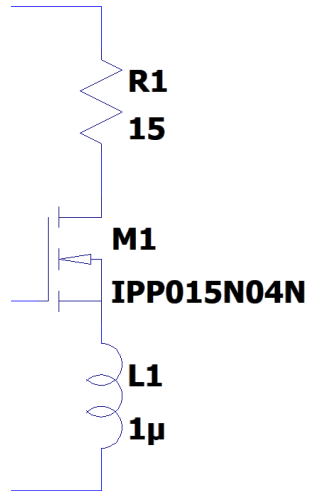





Fast

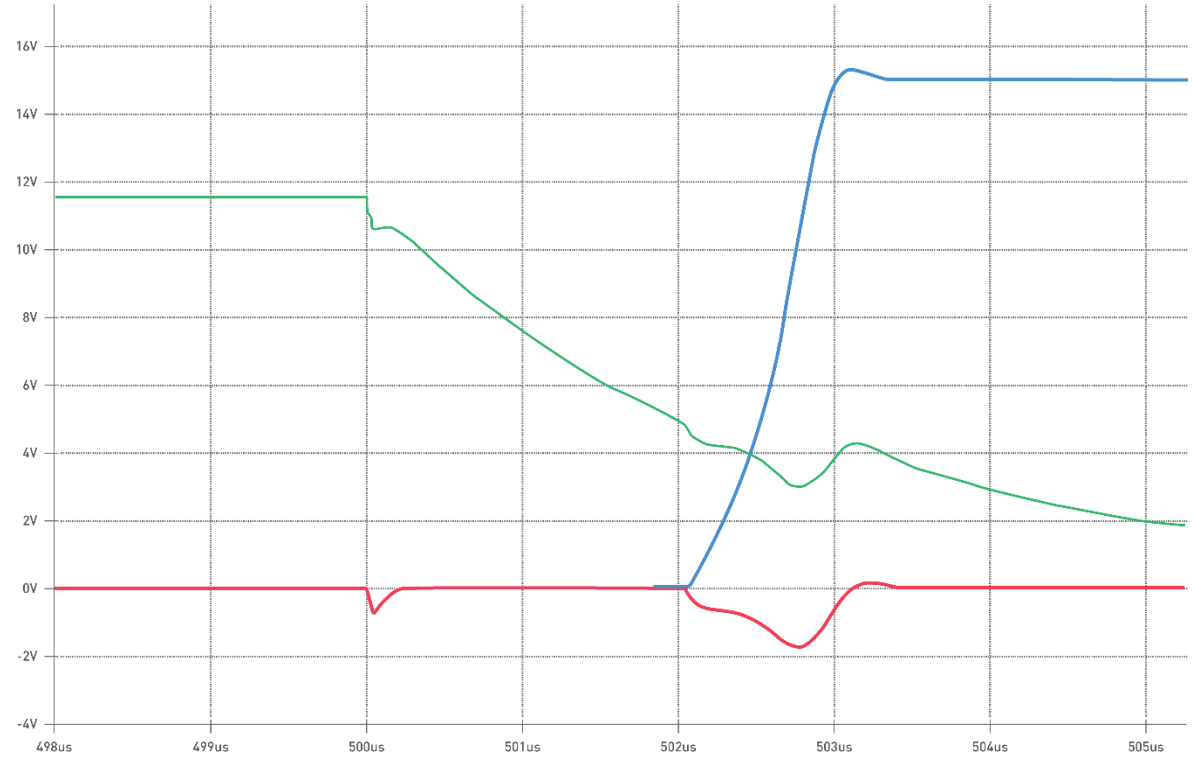




Slow

Green: Gate Voltage  
Blue: Drain Voltage  
Red: Source Voltage

# EMI Concerns

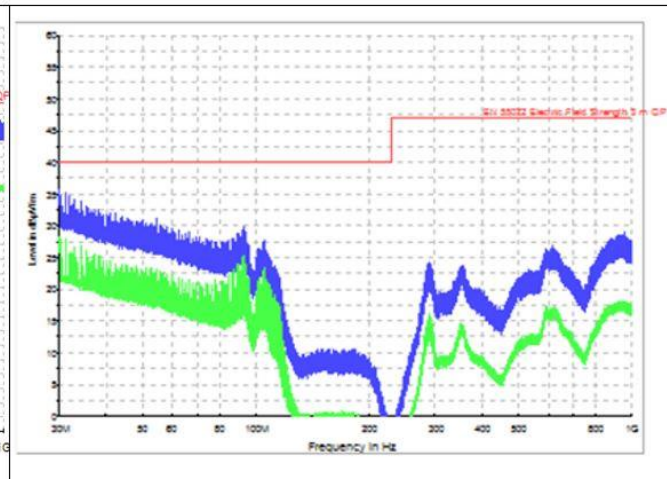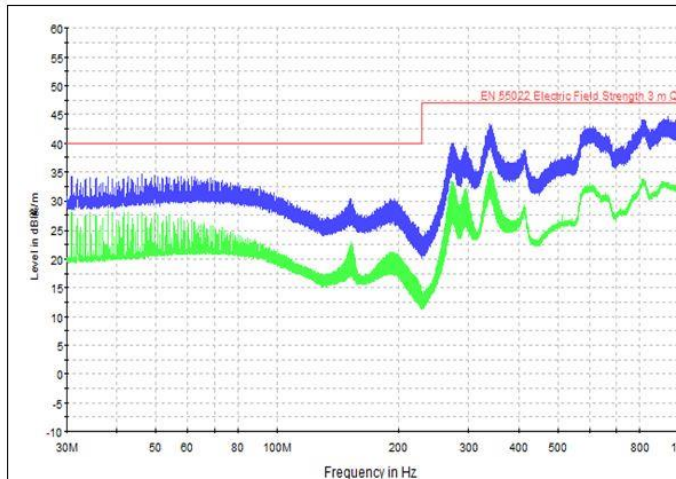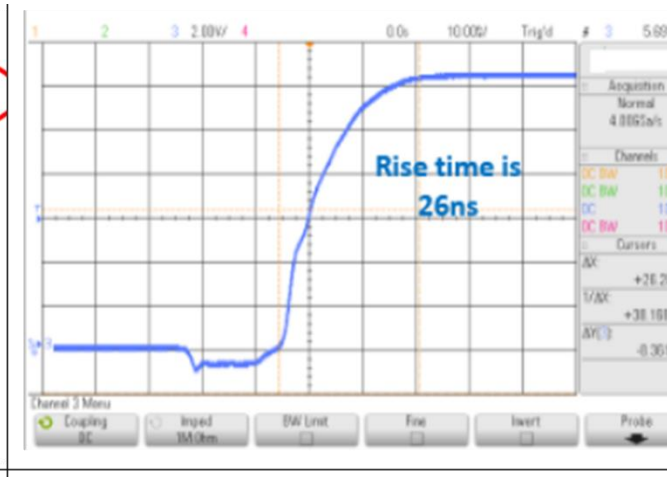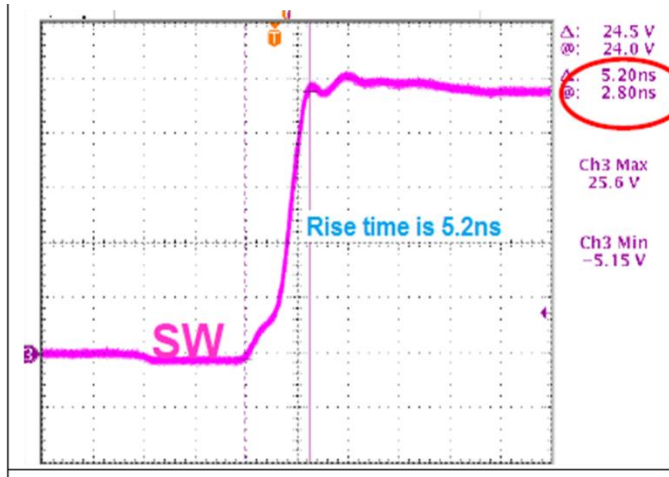

# Body Diode Reverse Recovery

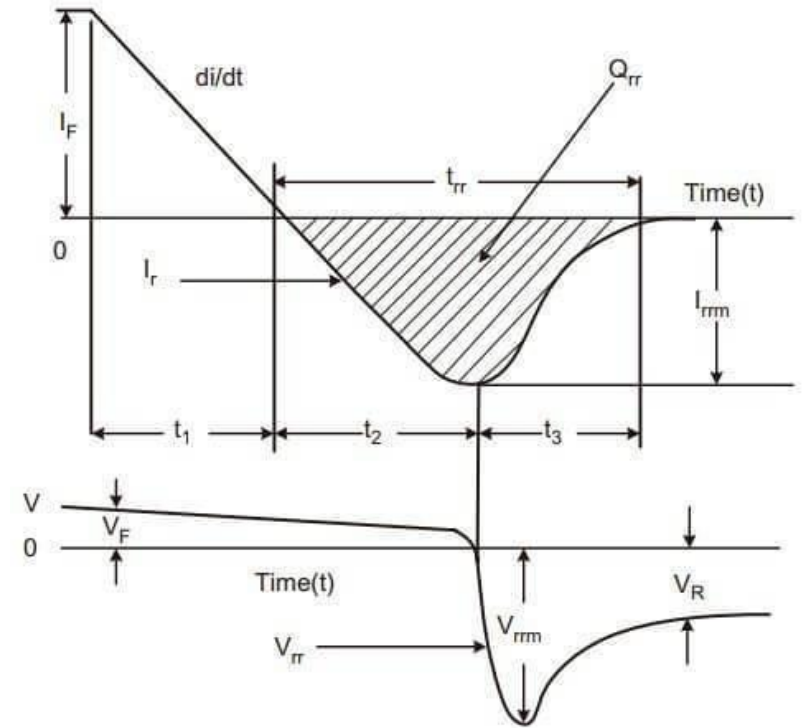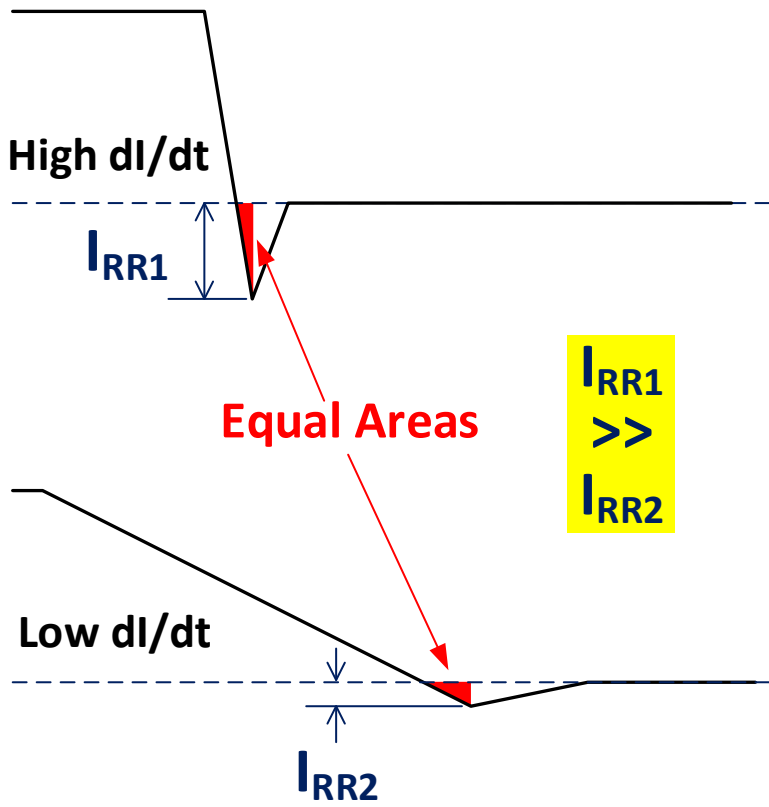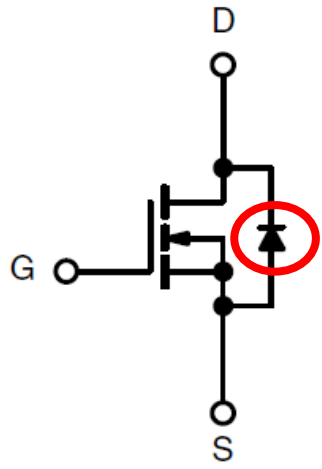

- **Key takeaways:**
  - Understand how MOSFETs work to implement a successful power circuit
  - Optimize the gate drive to control slew rate, transients, and EMI
  - Carefully design the PCB with consideration of parasitic inductances and impedances

## Q&A


Please submit questions through the “Q&A” menu option in the Zoom app

This webinar and others will be available for on-demand streaming at:


[MonolithicPower.com/webinars](https://MonolithicPower.com/webinars)



# The Body Diode

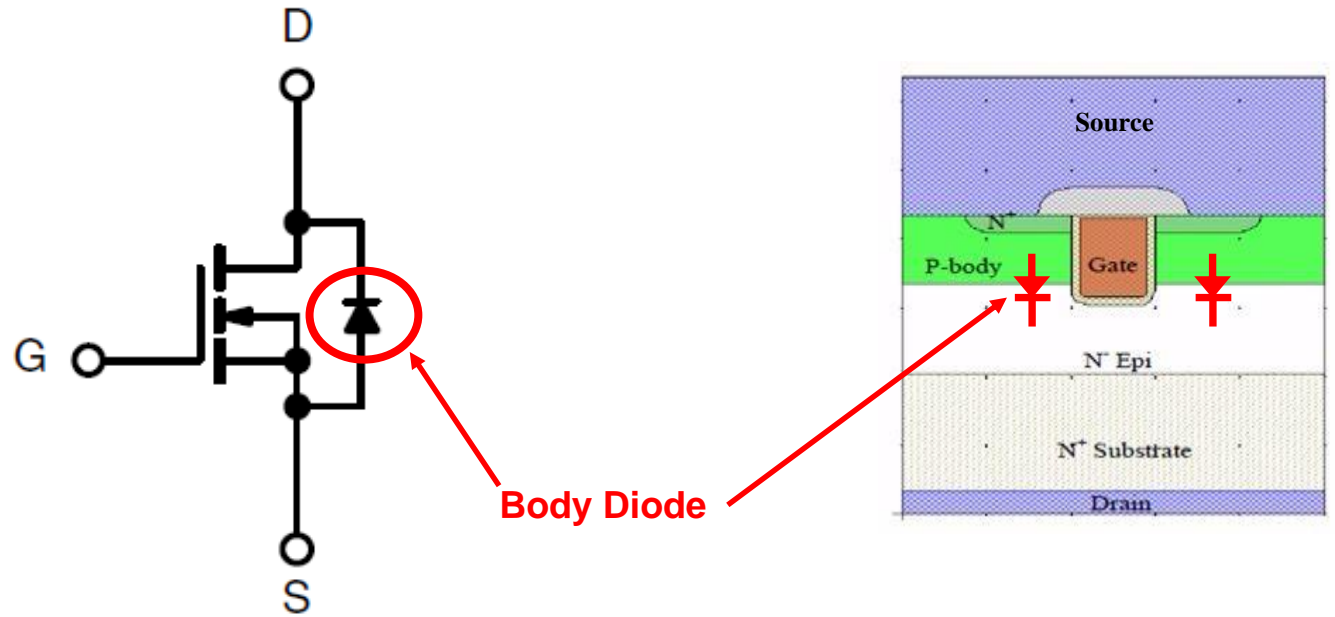


# DC Current Needed for Gate Drivers

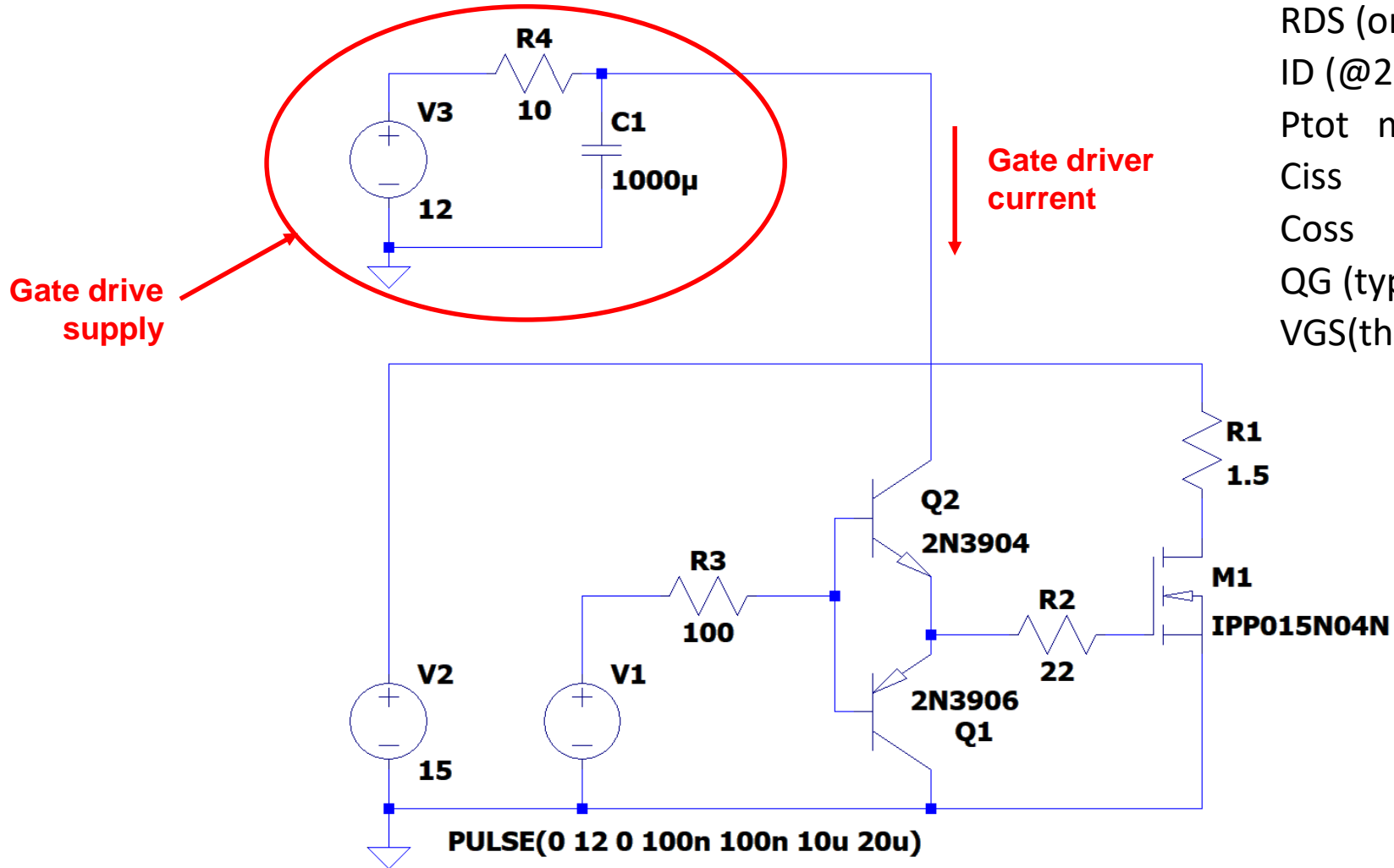

## IPP015N04N

VDS max	40.0 V
RDS (on) (@10V)	max 1.5 m $\Omega$
ID (@25°C) max	120.0 A
Ptot max	250.0 W
Ciss	15000.0 pF
Coss	4000.0 pF
QG (typ @10V)	188.0 nC
VGS(th) min / max	2.0 V / 4.0 V

# DC Current Needed for a Gate Driver

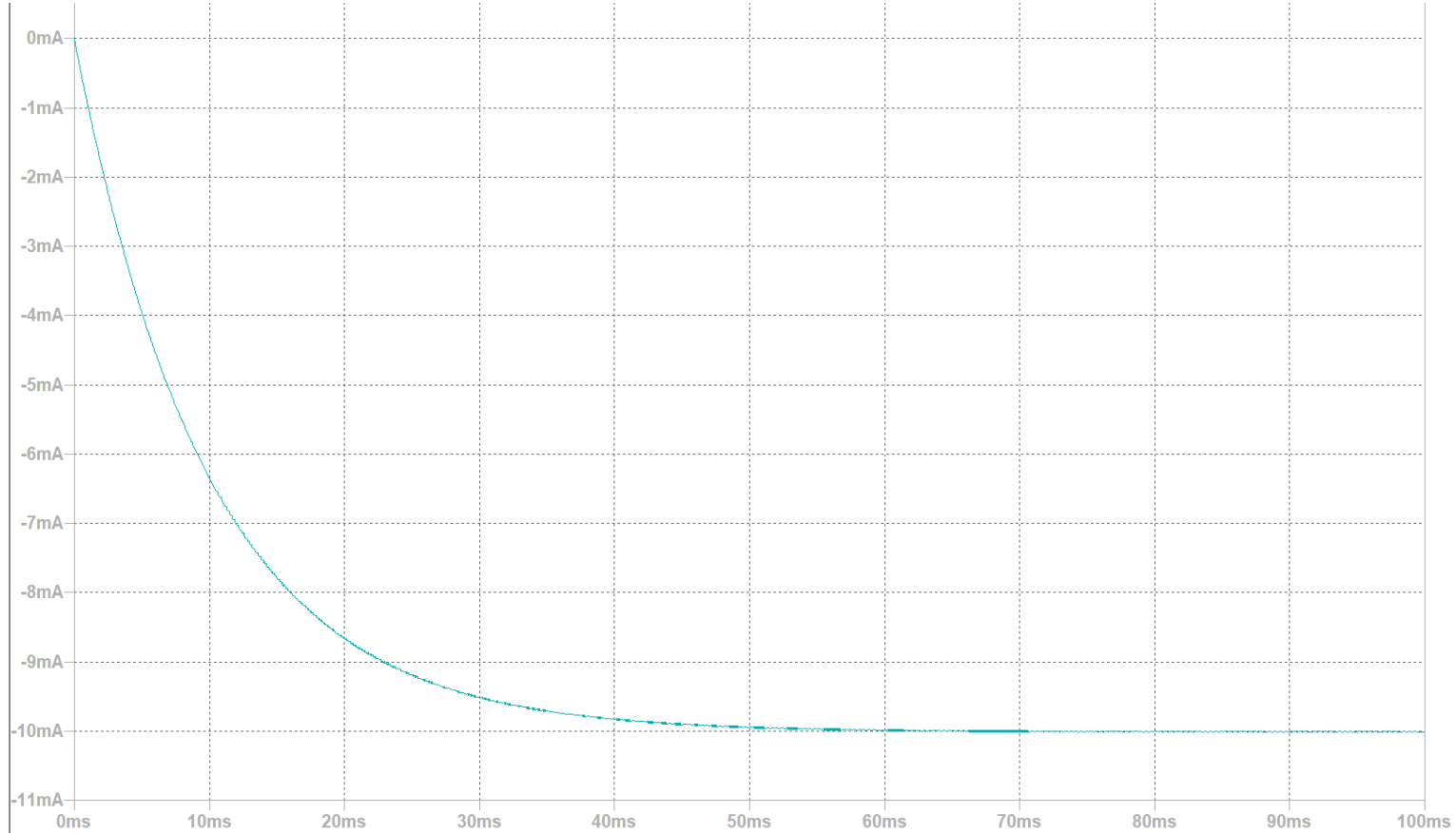

# MOSFET Ratings and Breakdown




## Absolute Maximum Ratings

$T_A = 25^\circ\text{C}$		VALUE	UNIT
$V_{DS}$	Drain-to-Source Voltage	30	V
$V_{GS}$	Gate-to-Source Voltage	$\pm 20$	V
$I_D$	Continuous Drain Current (Package Limited)	60	A
	Continuous Drain Current (Silicon Limited), $T_C = 25^\circ\text{C}$	123	
	Continuous Drain Current <sup>(1)</sup>	24	
$I_{DM}$	Pulsed Drain Current <sup>(2)</sup>	256	A
$P_D$	Power Dissipation <sup>(1)</sup>	3.1	W
	Power Dissipation, $T_C = 25^\circ\text{C}$	83	
$T_J$ , $T_{stg}$	Operating Junction Temperature, Storage Temperature	-55 to 150	$^\circ\text{C}$
$E_{AS}$	Avalanche Energy, Single Pulse $I_D = 39\text{ A}$ , $L = 0.1\text{ mH}$ , $R_G = 25\ \Omega$	76	mJ


(1) Typical  $R_{\theta JA} = 40^\circ\text{C/W}$  on a 1-in<sup>2</sup>, 2-oz Cu pad on a 0.06-in thick FR4 PCB.

(2) Max  $R_{\theta JC} = 1.5^\circ\text{C/W}$ , pulse duration  $\leq 100\ \mu\text{s}$ , duty cycle  $\leq 1\%$


# Avalanche

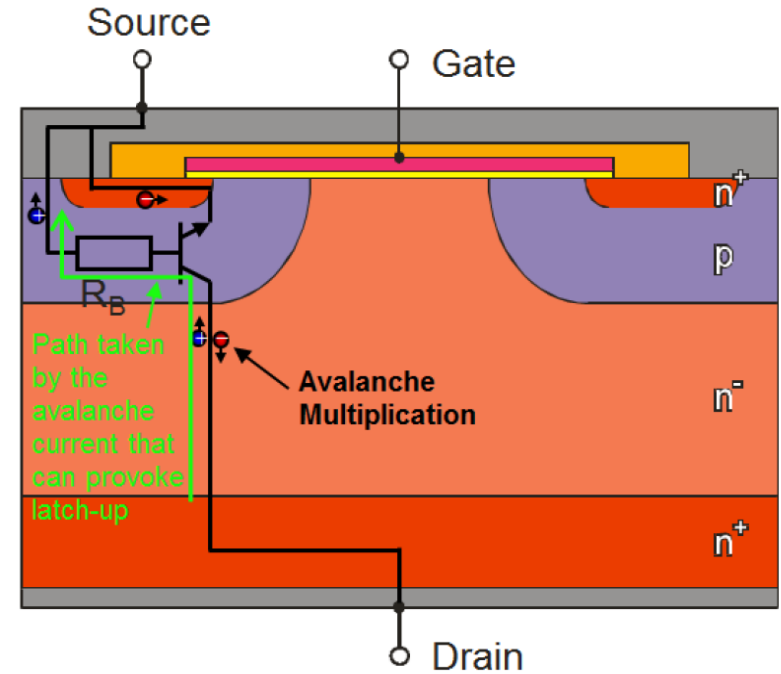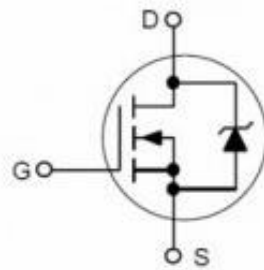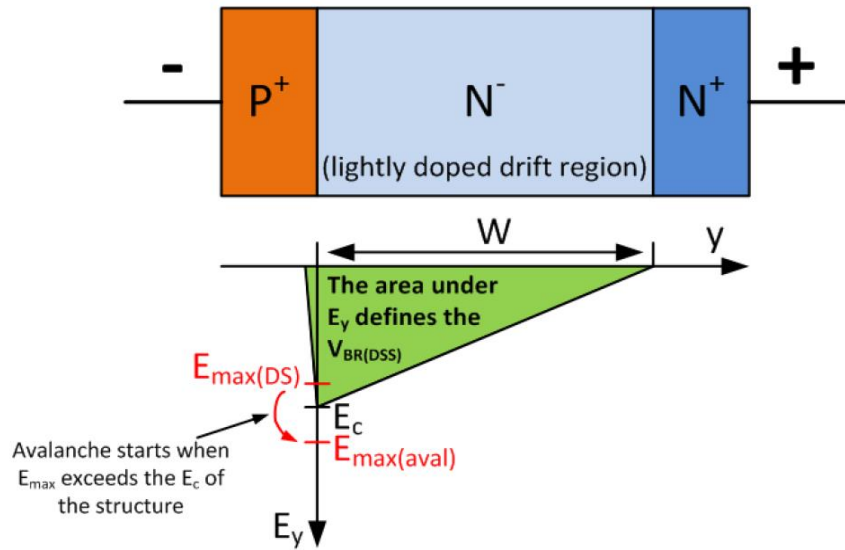

# High-Side Gate Drive

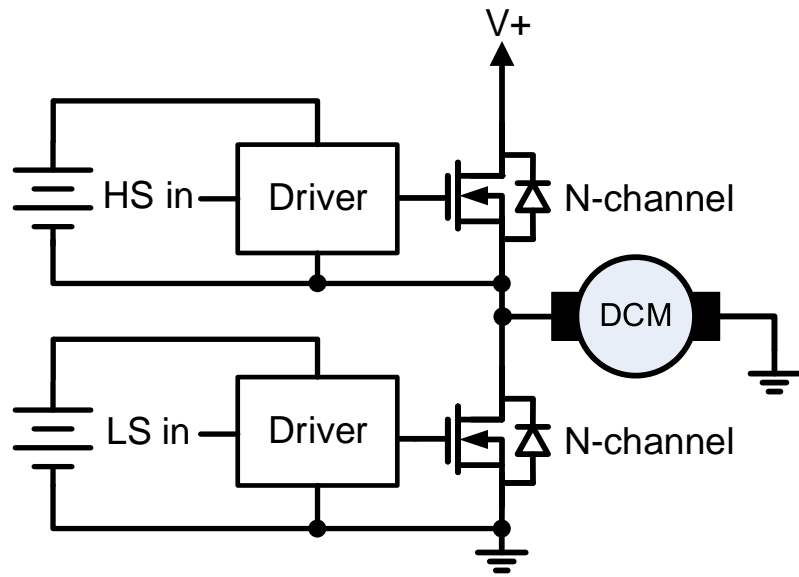


Isolated High-Side Supply

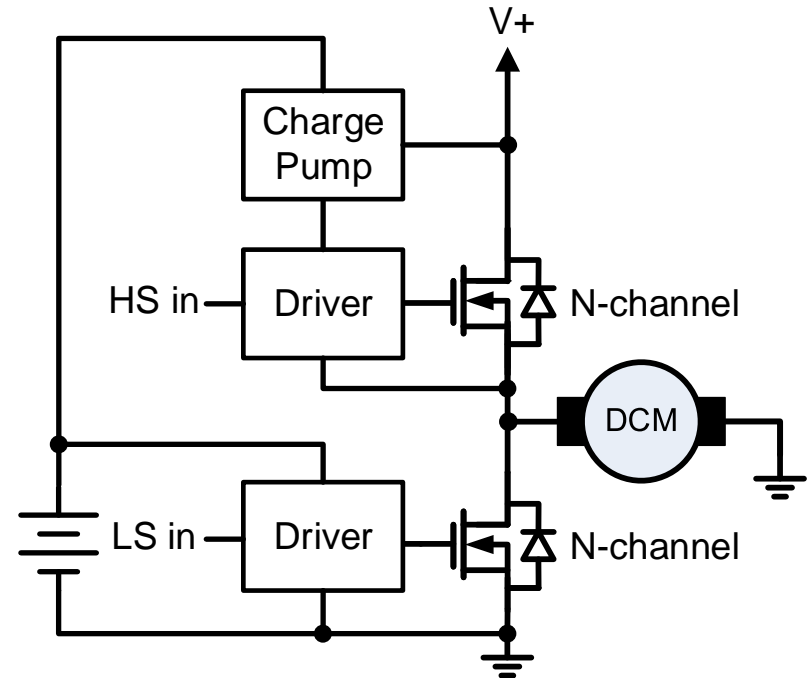


Charge Pump High-Side Supply


# Bootstrap Gate Drive

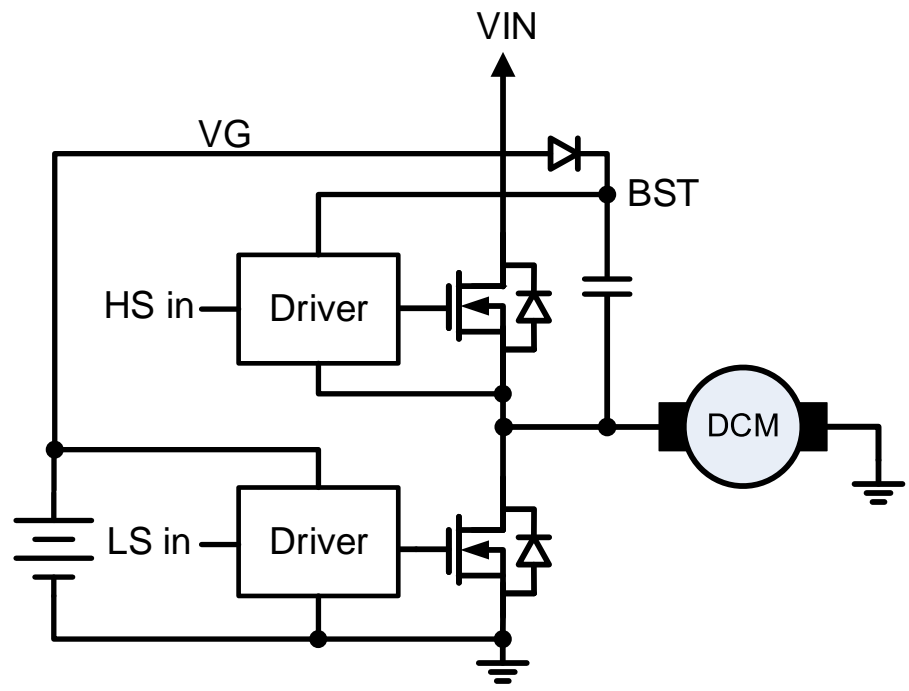


Bootstrap High-Side Supply

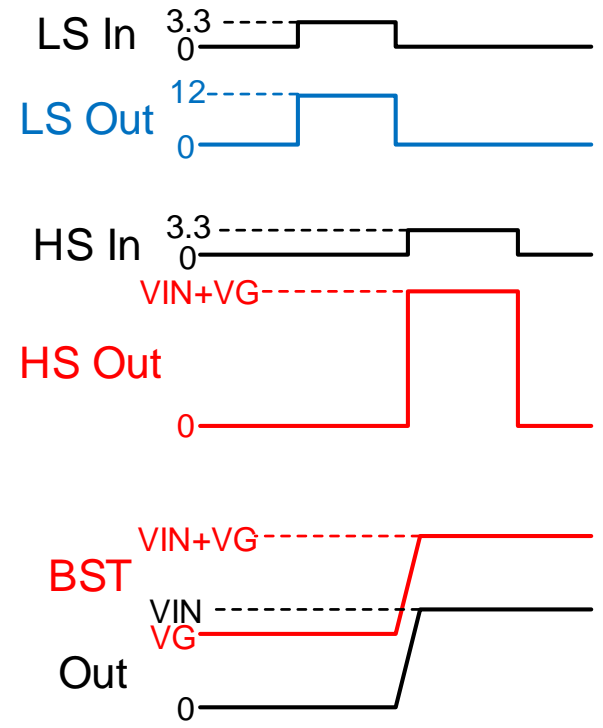
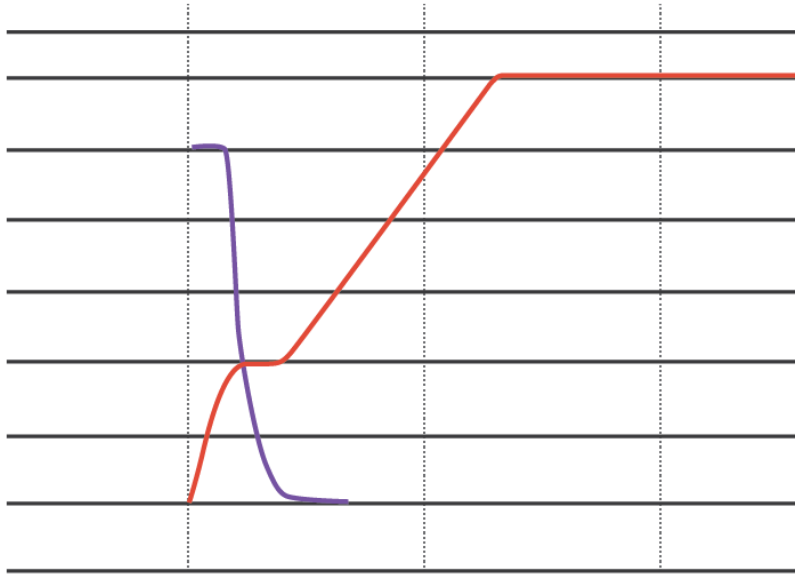
# Driving the Gate: Constant Current vs. Series Resistance



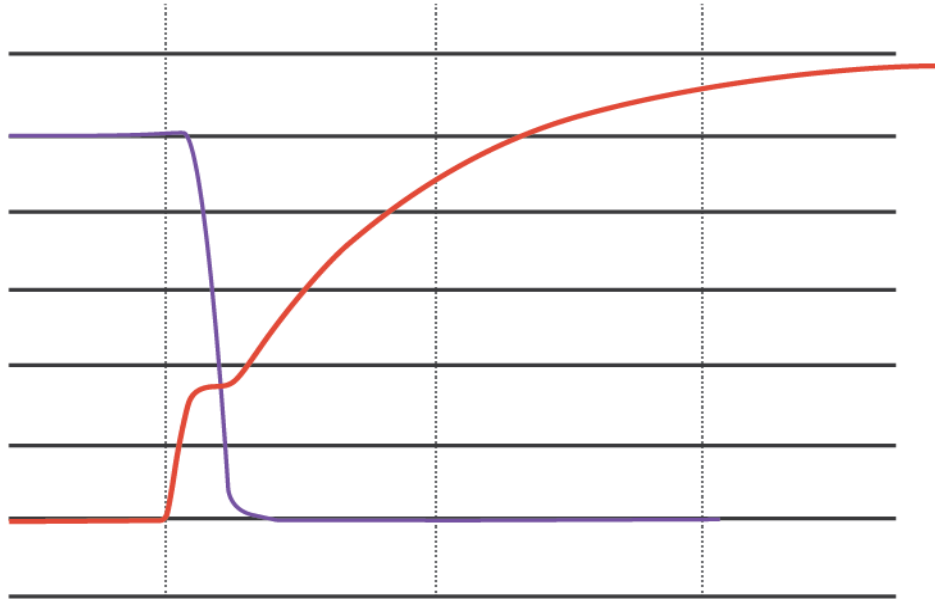**1 Amp Constant Current Gate Drive**  
(100nC - Red = gate, purple = drain, 200nS/div)



**12V Gate Drive with 12Ω Series Resistance**  
(100nC - Red = gate, purple = drain, 200nS/div)