

# Optimize Switch-Mode Power Modules to Achieve Ultra-Low ( $\mu\text{V}$ ) Ripple and Noise

Ao Sun -- Monolithic Power Systems

Xin Zhao -- Monolithic Power Systems

George Stathakis -- Monolithic Power Systems

# Background

- The growing bandwidth of wireless networks and data centers demand for **power regulators** with **high power density**, **fast load transient response**, and **high efficiency**.
- High-performance RF data converters, e.g. Xilinx Zynq UltraScale+ RFSocS which provides a comprehensive RF signal chain, are necessary for wireless applications.
- The **performance of the RF data converters** is closely coupled with the **noise level** of their power supplies. LDO is widely selected due to its low noise.
- **Switching regulator has much higher efficiency than LDO**. This paper designs a passive output filter for switching regulator, which can meet the **low noise (uV)** requirement.

# Output Voltage Ripple with Forced CCM Operation


 


Figure 1. Low Noise Filter Design

- An **ultra-small and ultra-low noise** power module, MPM3833C, is used as a design example. It features forced **CCM** operation, which brings low ripple at light load.

# Why use second stage inductive filter?

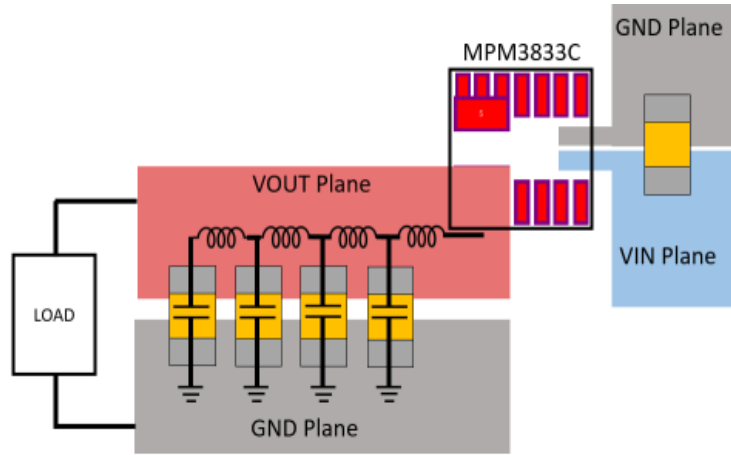


- As more capacitors are placed on the output plane, the distance from the additional capacitor to the output pin of the power module increases.
- Consequently, more **parasitic inductance** is involved in the output capacitor that is farther away from the power module.

Figure 2. Typical PCB Layout for the MPM3833C Power Module

 
# Why use second stage inductive filter?

Output voltage ripple with one 22 $\mu$ F output capacitor



- Additional output capacitor becomes less effective

4x22 $\mu$ F output capacitor

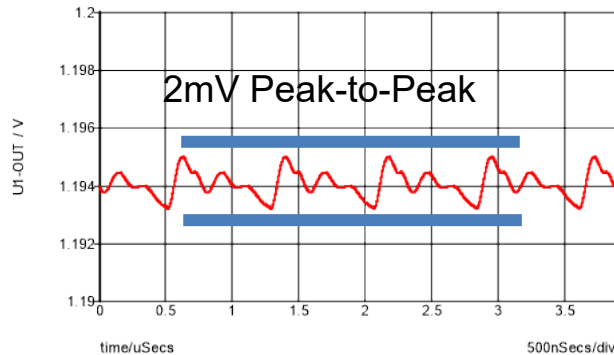

5x22 $\mu$ F output capacitor

 


Fig. 3 Output Voltage Ripple of the MPM3833C with (a) 22 $\mu$ F Output Capacitor (b) 4x22 $\mu$ F Output Capacitors and (c) 5x22 $\mu$ F Output Capacitors

# Design of the Second Stage Filter

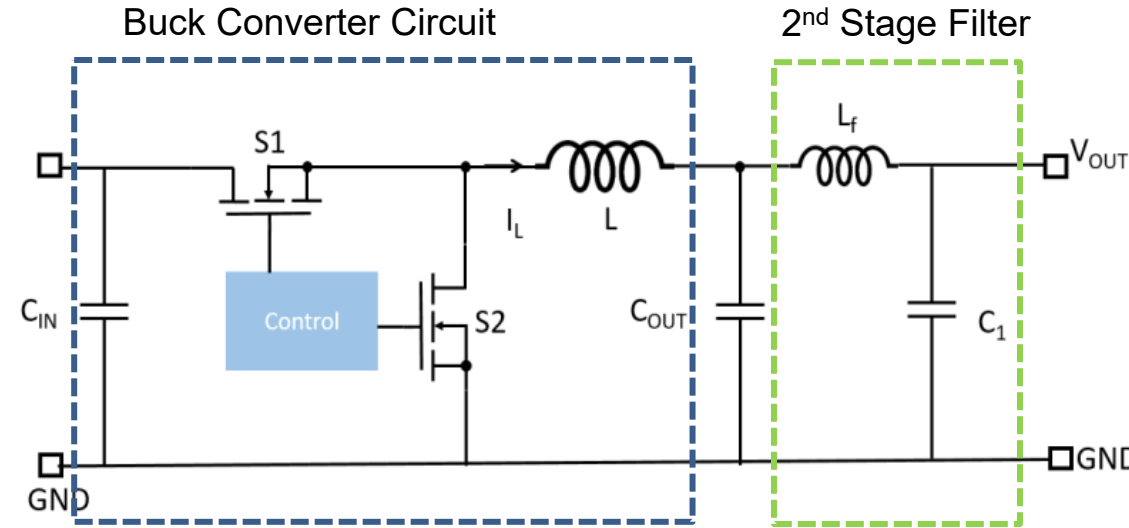



Figure 4. Second Stage LC Filter with Parallel Damping Branch [1]

- Design  $C_{OUT}$  to reduce the output voltage ripple to 5mV-10mV
- Select  $L_f$  at 0.22uH-1uH value. The inductor should be selected to have minimal DCR

$$f_0 = \frac{f_{sw}}{10^{\frac{20 \log \frac{V_{O,p-p}}{V_{1,p-p}}}{-40}}}$$

1

# Damping of the LC filter

 

- At **load transient**, the resonance between the filtering inductor and bypassing capacitor may amplify the output ripple and create undesired ringing.
- To **avoid undesired ringing** at load transient, the second stage LC filter resonance must be properly **damped**.

Figure 5. Second Stage LC Filter with Parallel Damping Branch

# Damping of the LC filter

 


Figure 6. Step Response of (a) Underdamped LC Filter and (b) Overdamped LC filter


- $R_{\text{Damp}}$  needs to satisfy 
$$R_{\text{Damp}} > 2 \sqrt{\frac{L_f}{C_2}}$$



# Design Specification for ADC rails

Rail Name	VIN	VOUT	IOUT	Target Ripple Magnitude
ADC_AVCC	5V	0.925V	2A	0.4mV
DAC_AVCC	5V	0.925V	3.5V	0.4mV
ADC_AVCCAUX	5V	1.8V	2A	5.5mV
DAC_AVCCAUX	5V	1.8V	2A	1mV
ADC_AVTT	5V	2.5V/3V	2A	5mV

# Traditional Solution – LDO Approach

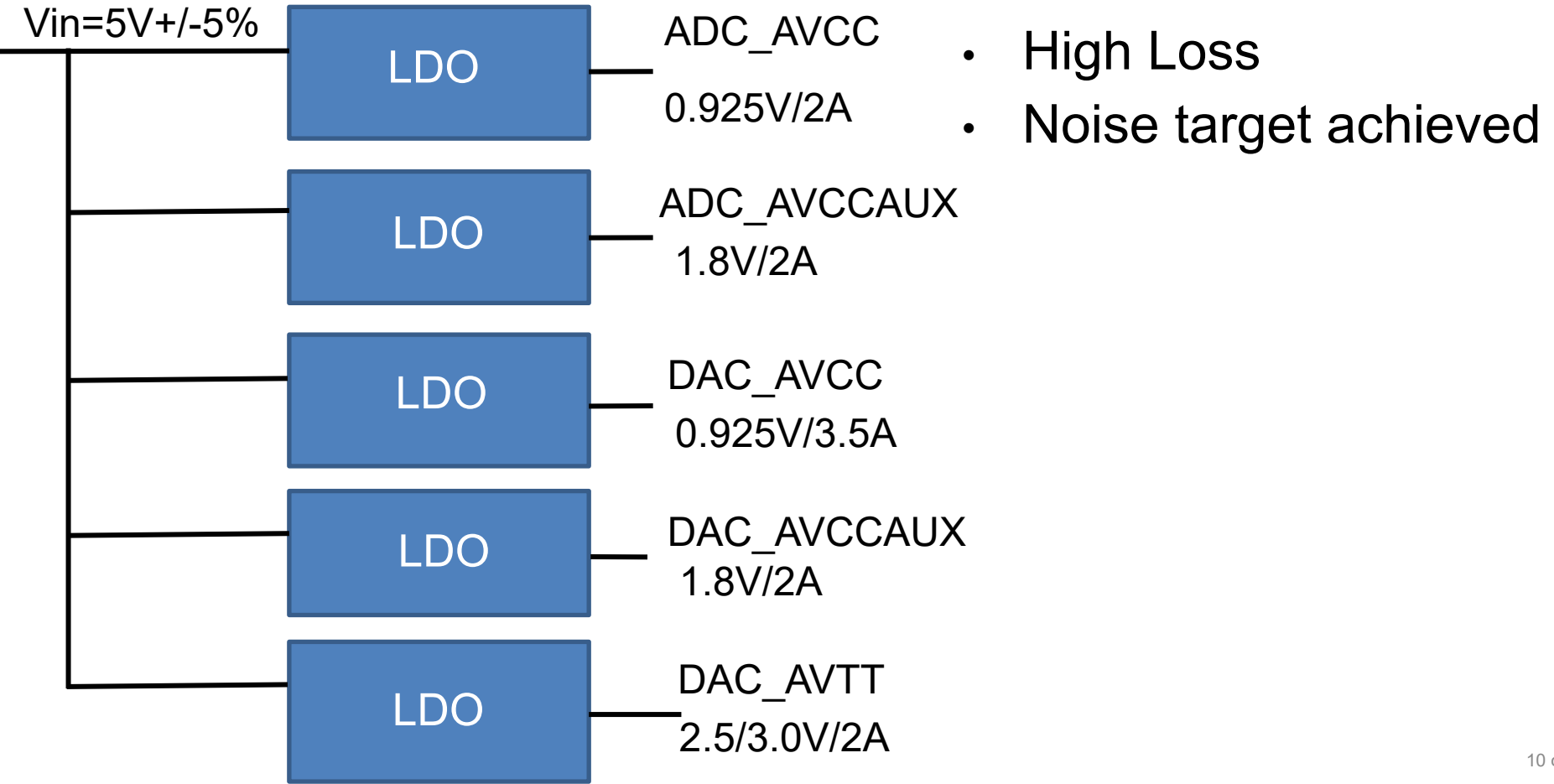

# Switch Mode Power Module + Passive Filter Solution


 


Figure 7. MPS EVREF0102 Power Module

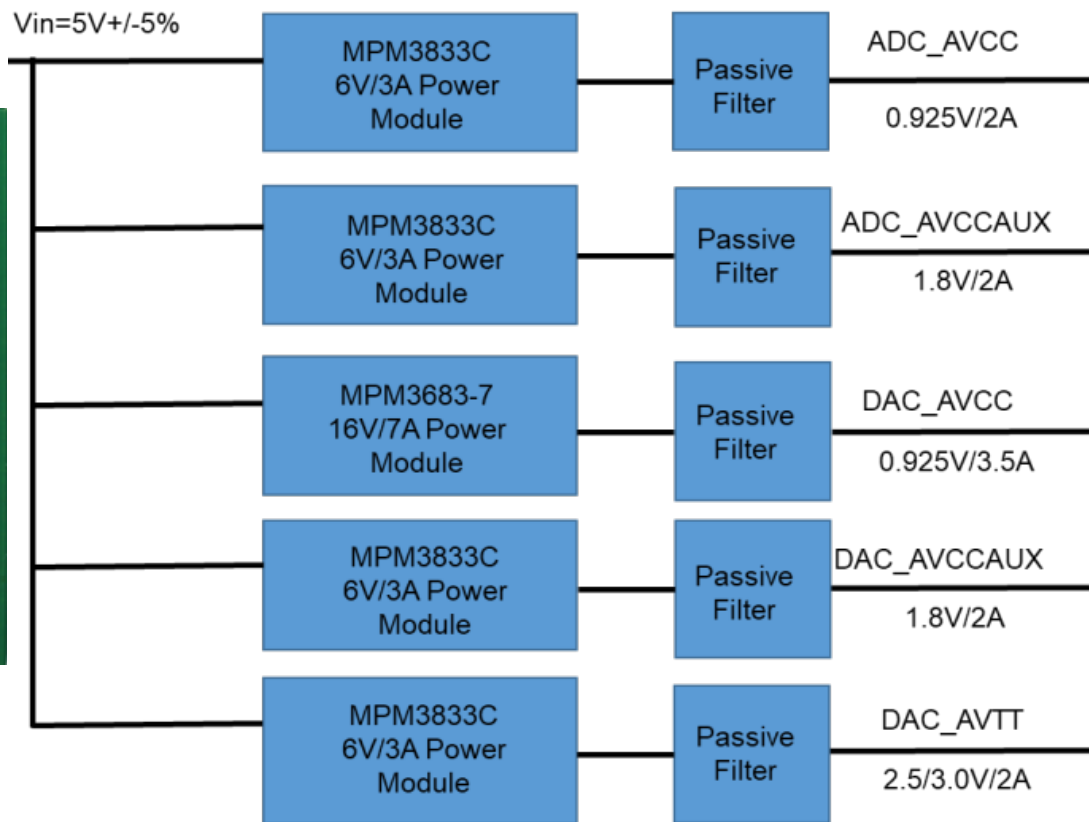

# Same Noise Performance as LDO Solution

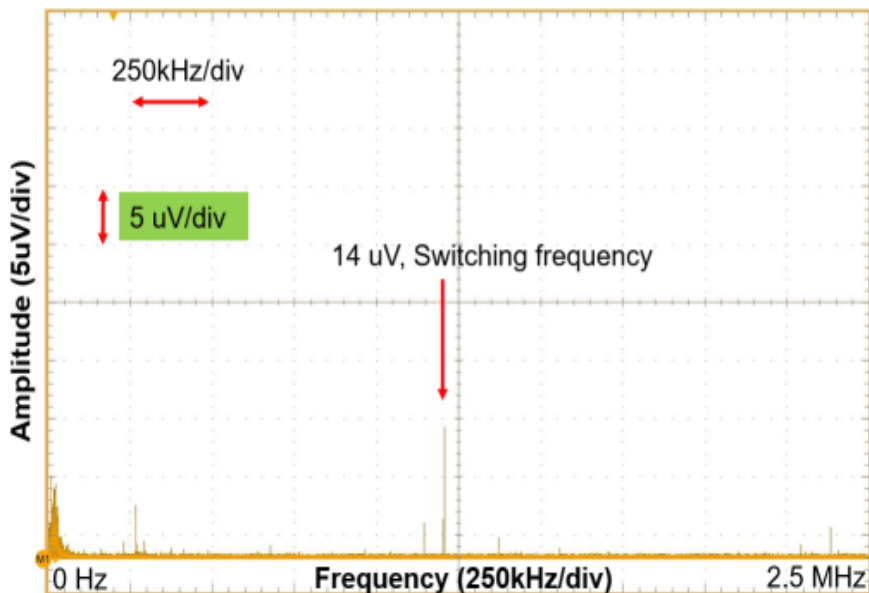


Figure 8. MPS EVREF0102 Power Module Noise Spread Spectrum

Same noise performance

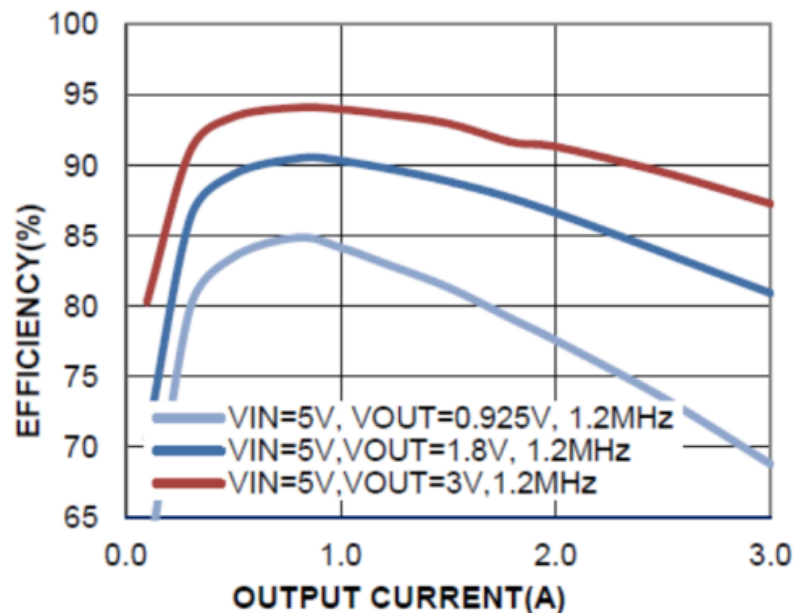



Figure 9. MPM3833C Efficiency VS. Output Current

4X more efficient than LDO

# Passive Filter Design Example

MPM3833C Converter Circuit

2<sup>nd</sup> Stage Filter

 

V <sub>IN</sub>	V <sub>OUT</sub>	I <sub>OUT</sub>	Target Ripple Magnitude
5V	0.925V	2A	20uV

## STEP 1.

Calculate Output voltage ripple with 22uF output capacitor  $C_{out}$

$$\Delta V_{C,p-p} = \frac{I_{L,p-p}}{8f_{SW}C_{OUT}} = 3.2mV$$


## STEP 2.

Calculate the resonant frequency of second stage filter which can reduce  $V_{out}$  ripple to target magnitude

$$f_0 = \frac{f_{sw}}{10^{\frac{20 \log \frac{V_{O,p-p}}{V_{1,p-p}}}{-40}}} = \frac{1.15MHz}{10^{\frac{20 \log \frac{3.2mV}{20uV}}{-40}}} = 91kHz$$

# Passive Filter Design Example

VIN	VOUT	IOUT	Target Ripple Magnitude
5V	0.925V	2A	20uV

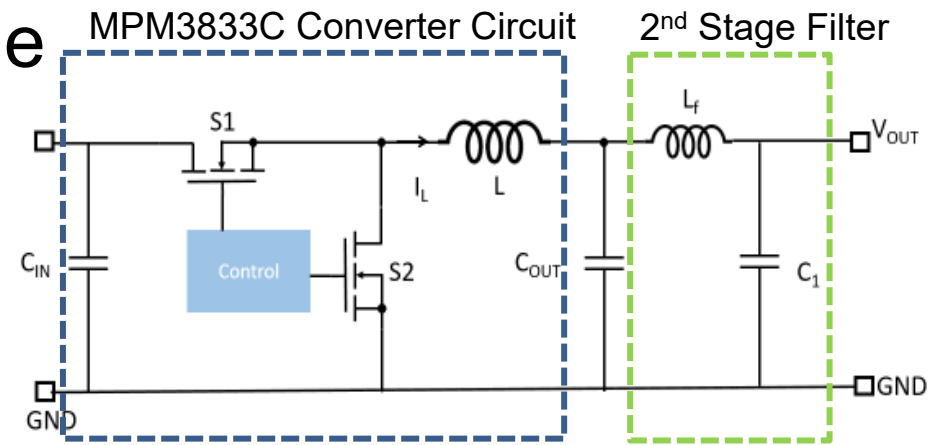

## STEP 3.

Select  $L_f = 0.24\mu H$ . The minimum second stage filter capacitance can be calculated. The significant de-rating of ceramic capacitor at DC bias should be noted.

$$C_1 = \frac{1}{4\pi^2 f_0^2 L_f} \div (0.8) = 16.25\mu F$$

## STEP 4.

In this use case, more output capacitors are used to achieve better load transient performance. The required damping resistance can be calculated

$$C_1 = 100\mu F + 47\mu F \times 5 \times 0.8 = 288\mu F$$

$$R_{Damp} > 2 \sqrt{\frac{L_f}{C_2}} = 58m\Omega$$

Thank You