

# Understanding PFC and LLC Topologies

October 2023

Webinar will begin at 5:00 PM CEST | 8:00 AM PDT | 11:00 AM EDT



# Agenda

- Understanding Power Factor Correction
- MPS Solutions for PFCs
- Understanding Resonant Power Conversion
- MPS Solutions for LLCs
- Q&A

# What Is PFC?

- PFC stands for **P**ower **F**actor **C**orrection
- **P**ower **F**actor (PF) is the ratio of active (real) power over apparent power:


$$\text{PF} = \frac{\text{active power}}{\text{apparent power}} = \frac{[\text{W}]}{[\text{V} \cdot \text{A}]}$$

- Popular analogy



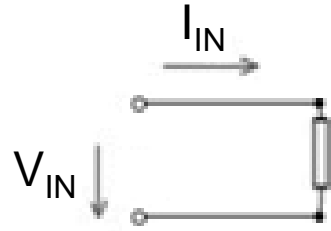
# What Is PFC?


- A PF of 1 corresponds to the resistor case:



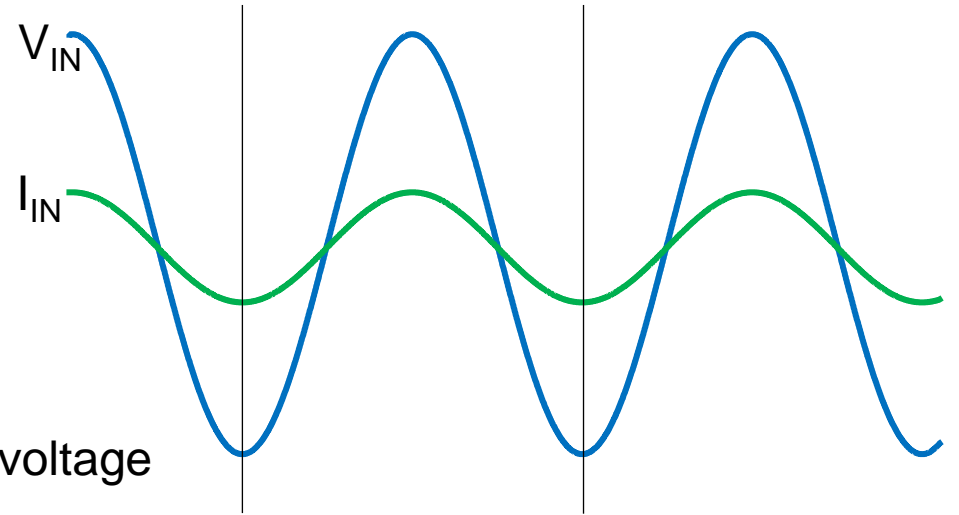
- The current is sinusoidal and in phase with the input voltage



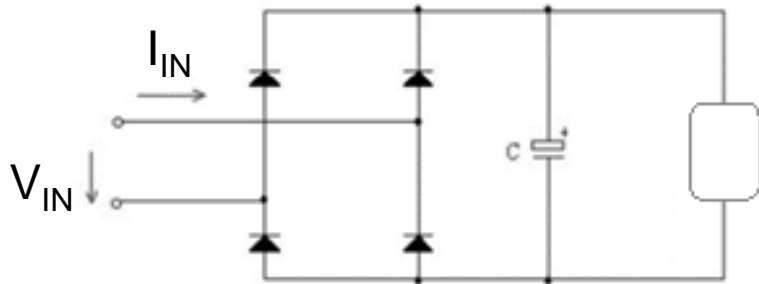- A typical power supply has a PF below 1:



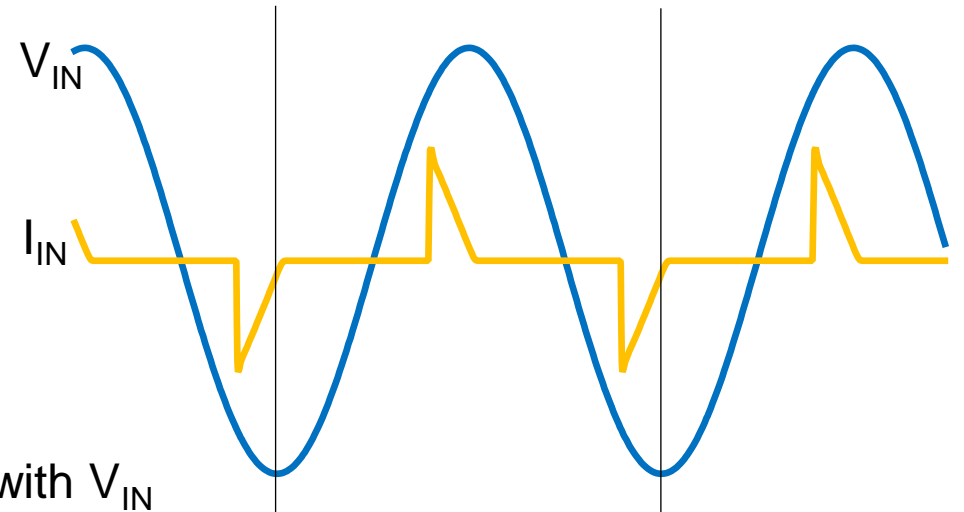- The current is not sinusoidal, and may be out of phase with  $V_{IN}$
- Larger RMS current circulates in input (higher reactive power)



# Why Is PFC Needed?

If the PF is low, more power circulates in the input wires than is used by the actual load

## → Risk of overheating of electrical wires

- At home:



3x 300W equipment with PF = 0.5  $\geq 8 A$

The same with PF = 1  $\geq 4A$

- On the distribution lines:




Happy birds!

## → Utility companies push for high PF



- Fewer power plants needed for the same equipment
- They can bill all the electricity generated!




# The Basic Concept of PFC

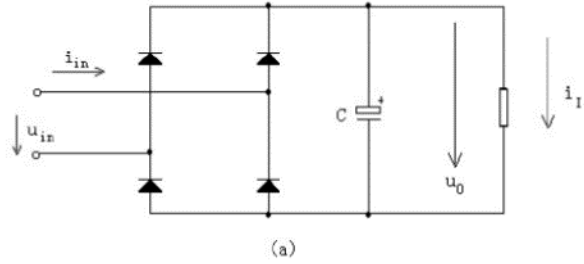

Adding PFC

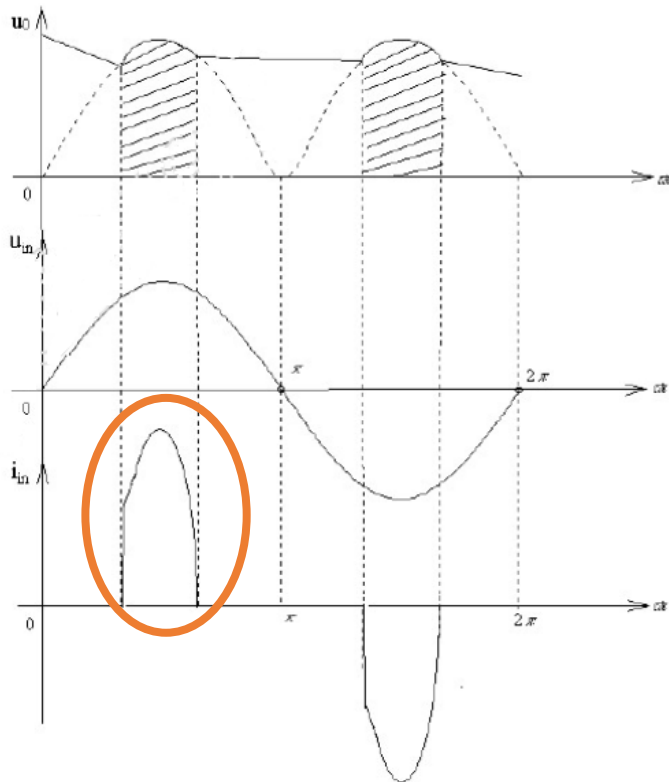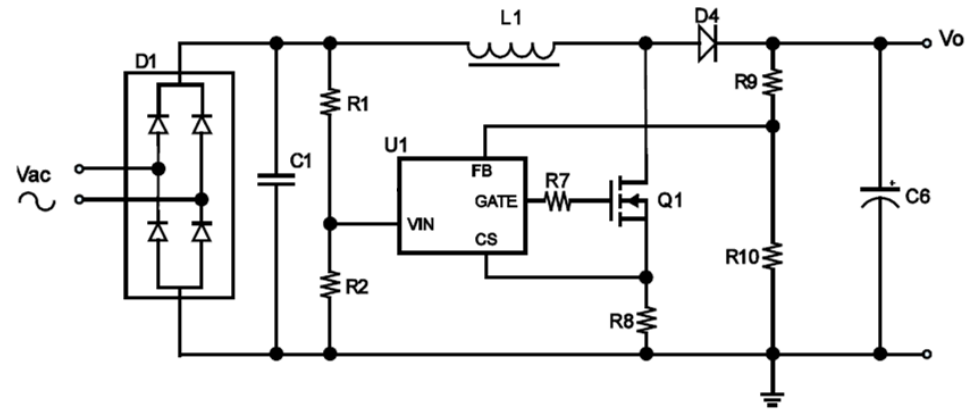


→

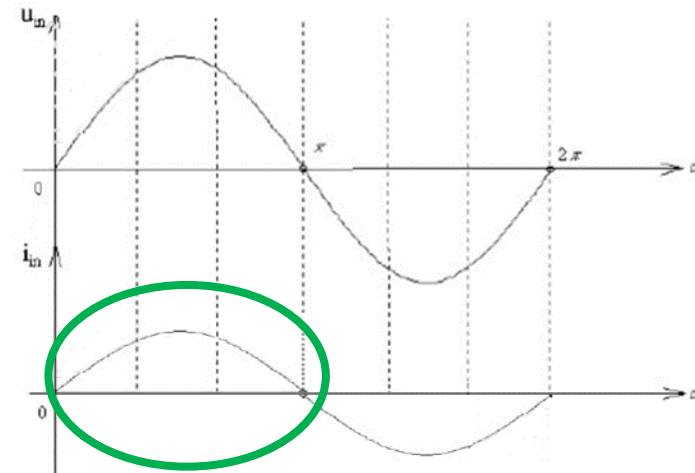

The input current follows the voltage


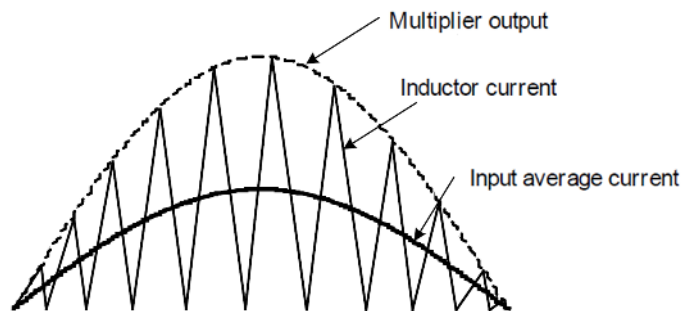
# PFC Modes of Operation

- Boundary-Conduction Mode PFC (BCM) or CrM (Critical-Conduction Mode)



Best suited for power < 300W  
Simpler architecture  
Zero-voltage switching  
Higher RMS currents

- Continuous Conduction Mode (CCM) PFC

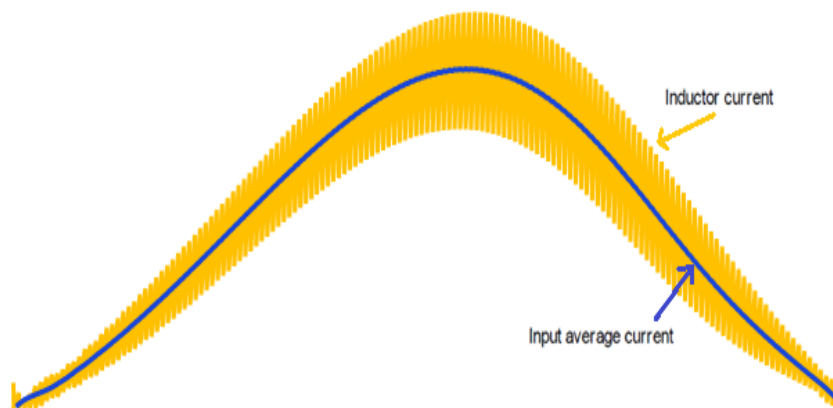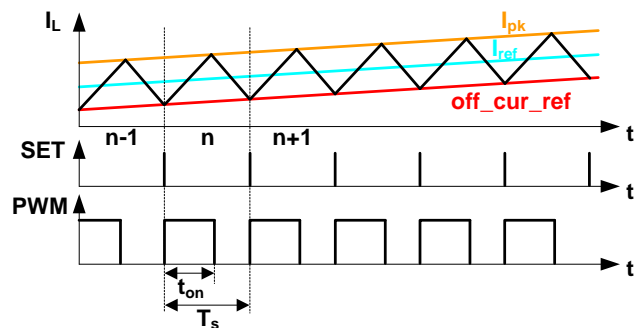

Best suited for power > 200W  
Lower RMS currents  
Hard switching  
More complex regulation loop


# PFC Modes of Operation

- Multi-Mode PFC

HR12xx

CCM or BCM at high loads

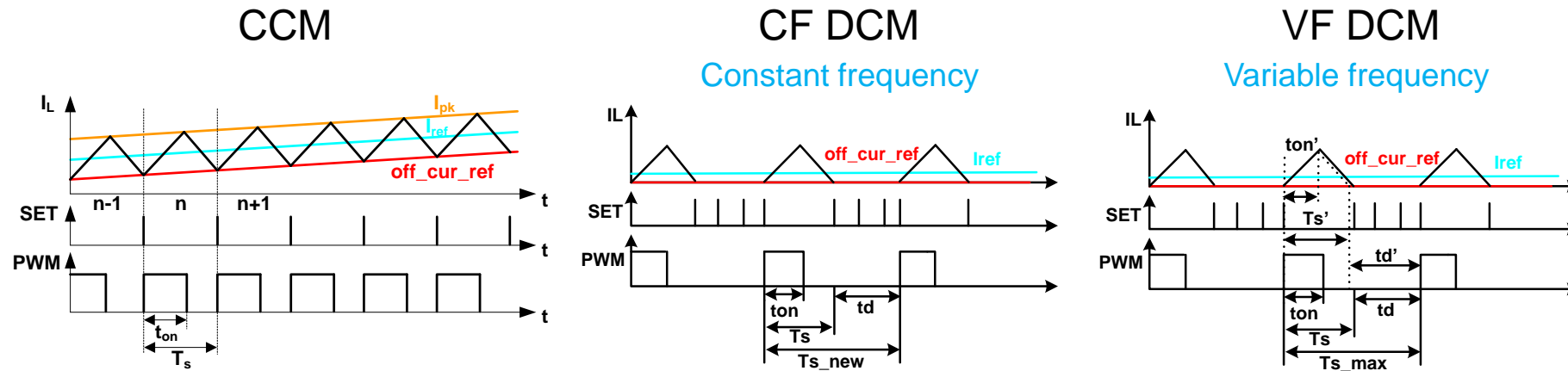→ Different DCM modes (discontinuous-conduction mode) under light loads to optimize efficiency





A set signal determines the CCM valley current point and DCM point.



# PFC Topologies


Passive:

Line Filter

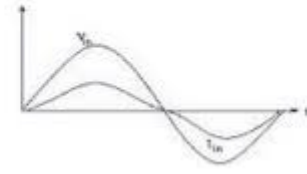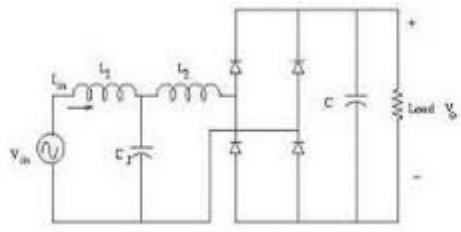

Large input inductor forces the current to be sinusoidal

Valley Fill

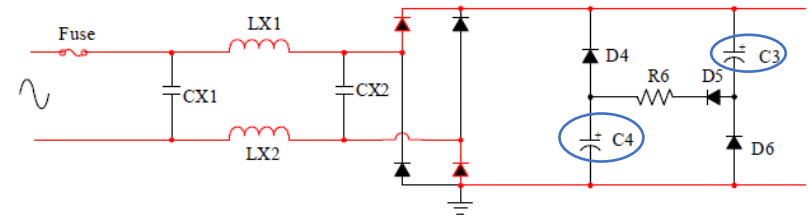


2x filtering capacitors are charged in series but discharged in parallel

Active:


Flyback (low-power, single-stage: PFC + isolated regulation)

Buck (not very common)

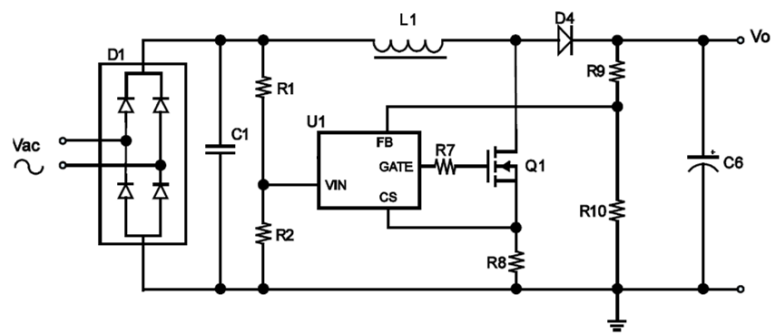Boost (most common for  $P_{OUT} > 100W$ )



High Efficiency

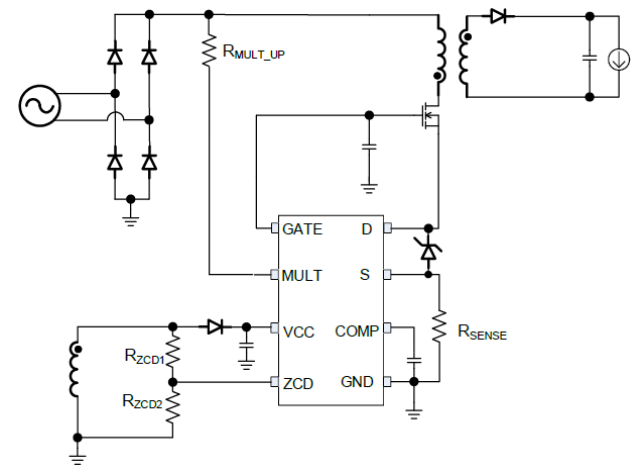

BCM flyback with Multiplier and Small Input Filtering Capacitor




# PFC Topologies

There are many more active PFC structures, most of them based on boost topology


Their main purpose is to achieve the best efficiency possible for a given output power (and price point)

For example: interleaved boost, bridgeless boost, Vienna rectifier, totem-pole, etc.

Full-Bridge Rectifier + Boost

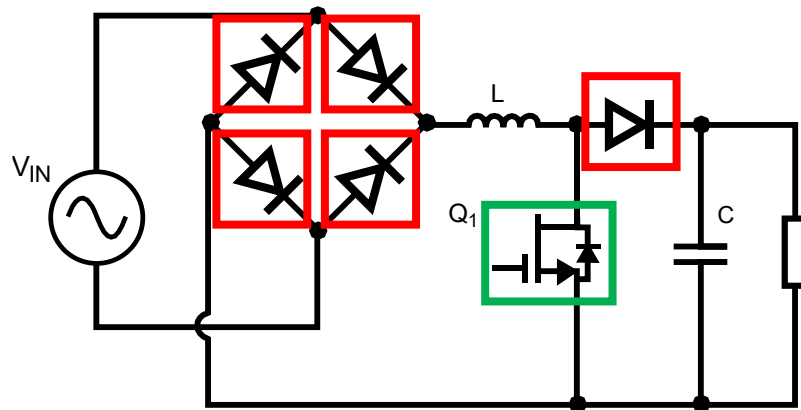

Totem-Pole Bridgeless PFC

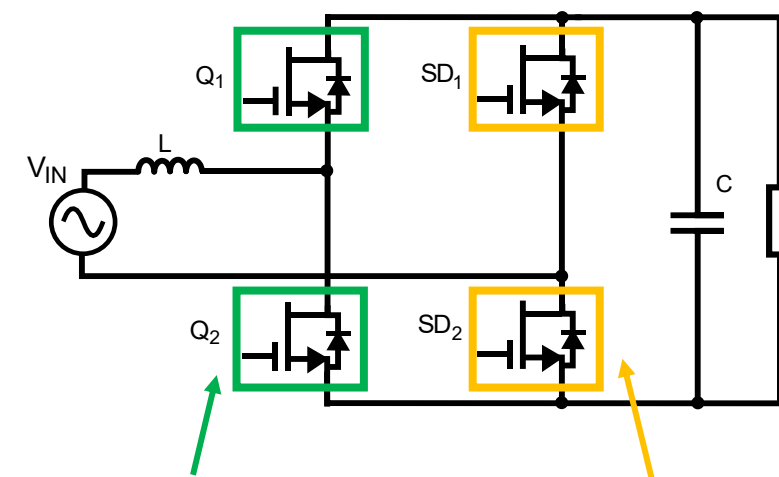

Fast Switching

$$f_{SW} = 100\text{kHz}$$


Slow Switching

$$f_{SW} = f_{GRID}$$

# Agenda

- Understanding Power Factor Correction
- **MPS Solutions for PFCs**
- Understanding Resonant Power Conversion
- MPS Solutions for LLCs
- Q&A

# MPS PFC Roadmap

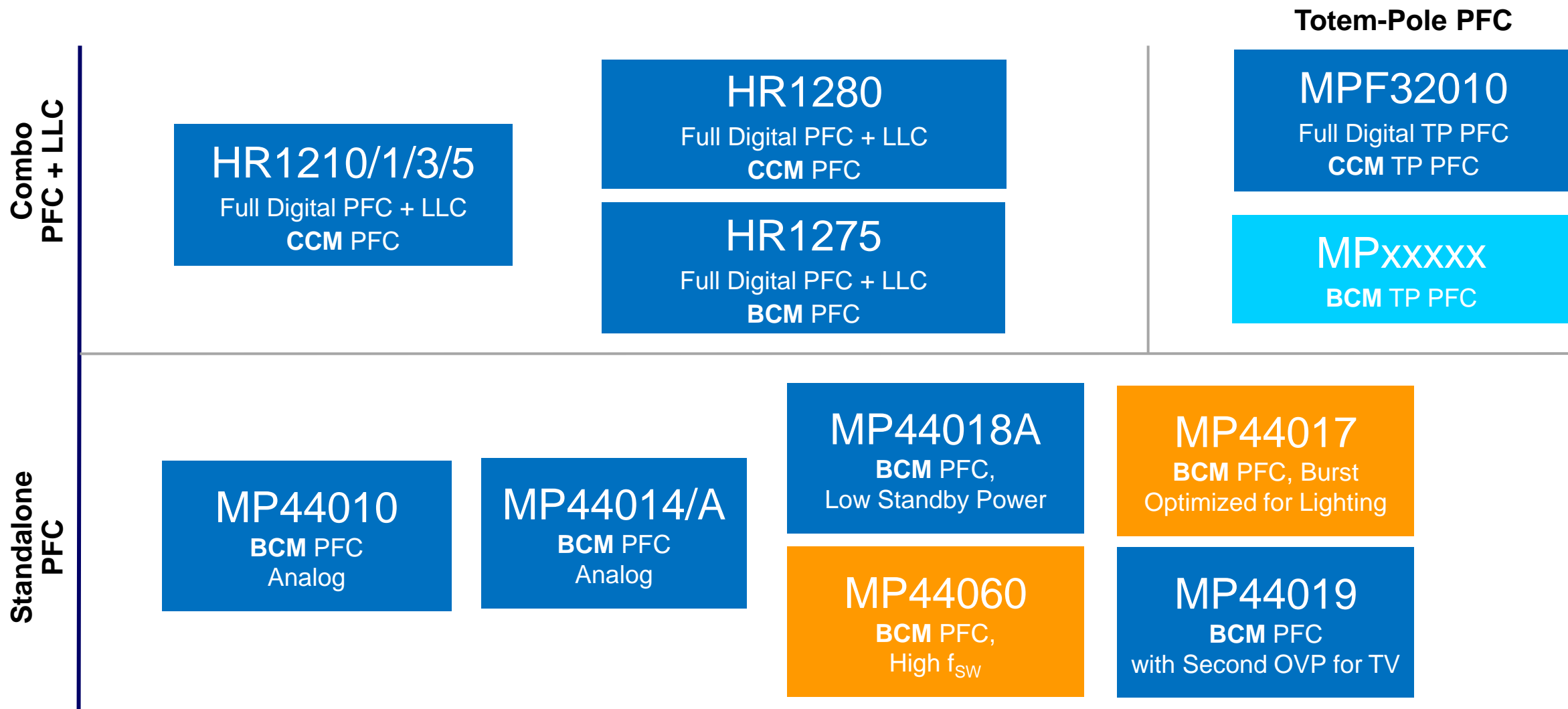

Released


Sampling

Under Design

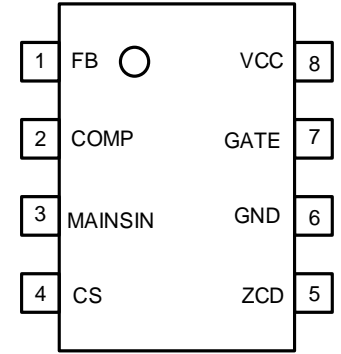
# MP44018 Key Features

- Valley Turn-On for Minimum Switching Loss
- Input Feed-Forward (Mains Compensation)
- Frequency Reduction to Reduce Switching Loss under Light-Load Conditions
- Improved THD
- Enhanced Dynamic Response
- Soft-Start/Shutdown Burst for Low Audible Noise

- Soft Start
- Under-Voltage Protection (UVP)
- Over-Voltage Protection (OVP)
- Over-Current Limit (OCL)
- Over-Current Protection (OCP)
- Brown-In (BI) and Brownout (BO)
- Open/Short Pin Protection
- Over-Temperature Protection (OTP)




**SOIC-8**  
(5mmx6.2mmx1.7mm) Package

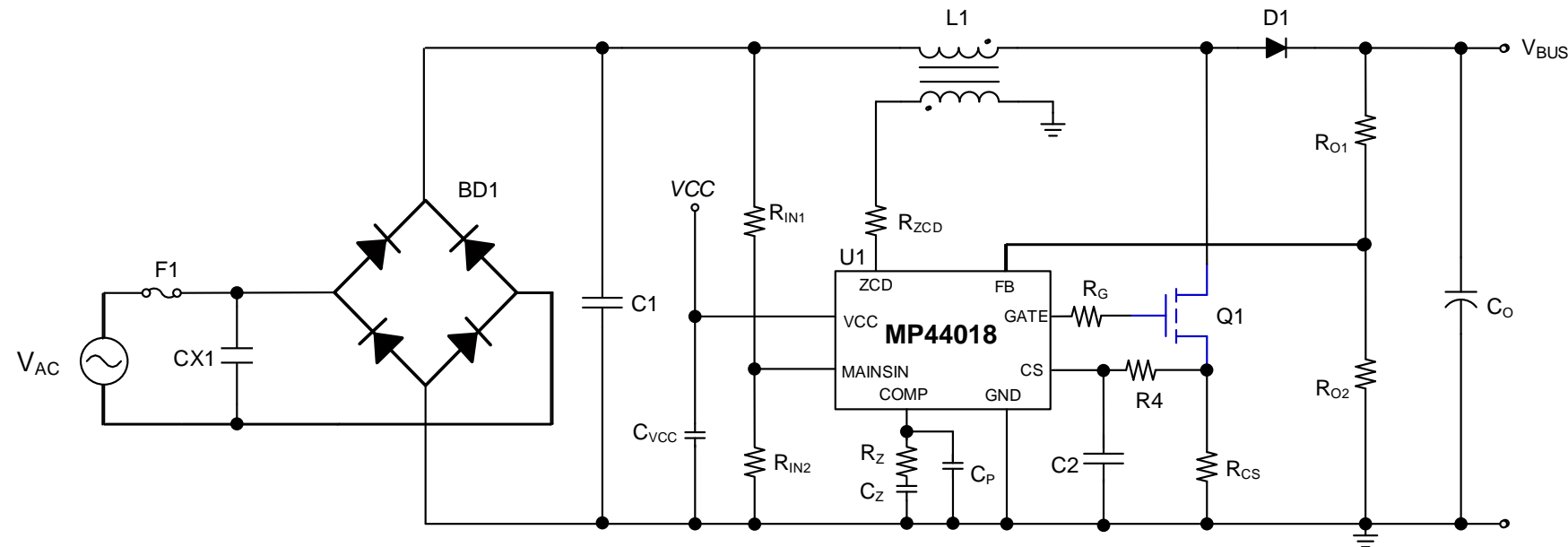



# MP44018 Enhanced Dynamic Response

## Enhanced Dynamic Response

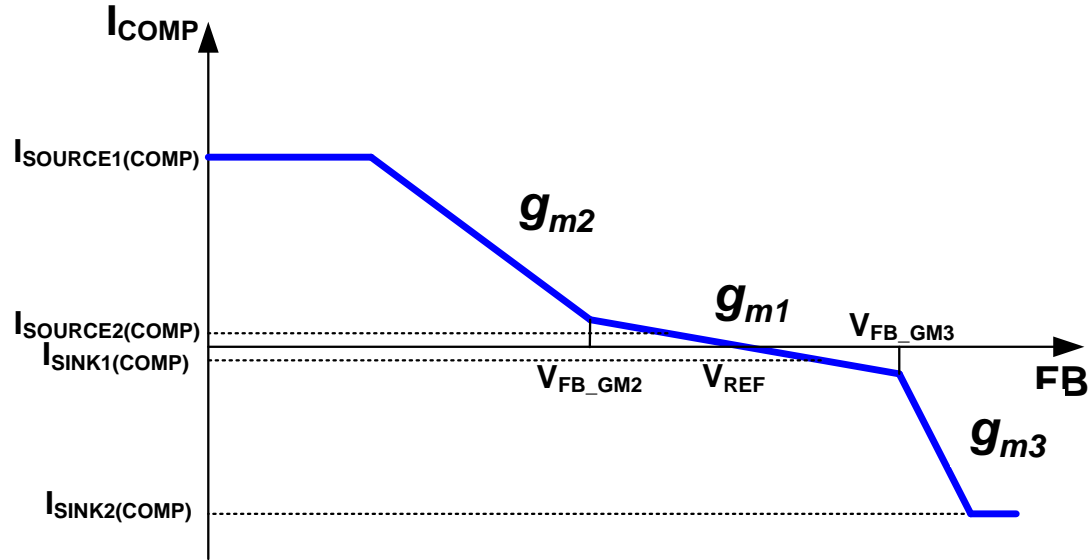

Nonlinear  $g_m$

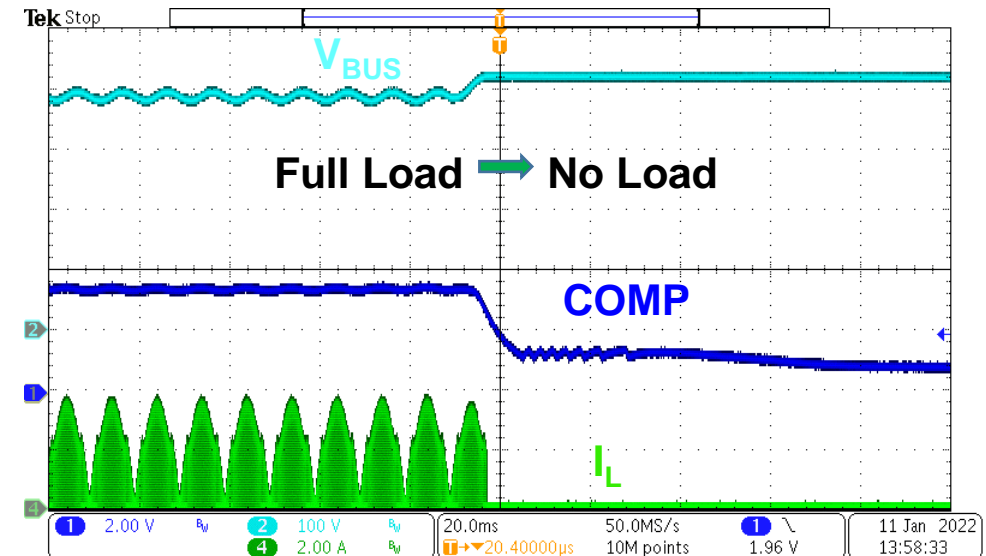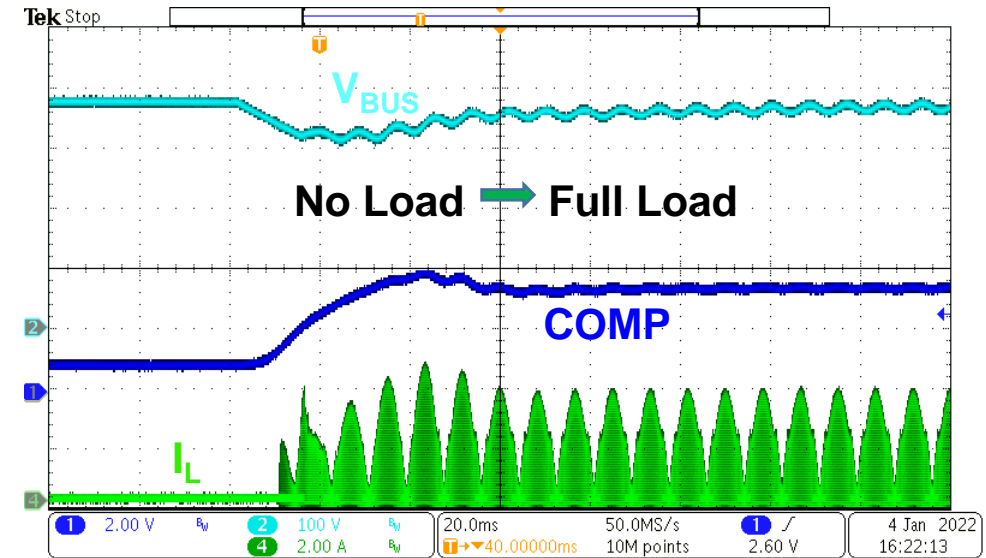- Low  $g_m$  ( $g_{m1}$ ) for better PF and THD in steady state
- High  $g_m$  ( $g_{m2}$  &  $g_{m3}$ ) for faster transient response



# MP44018 THD Improvement

	BCM (Constant-On-Time)	DCM (Variable-On-Time)
Operation Mode		
Input Current	$I_{IN1}(\theta) = \frac{ V_{AC}(\theta) }{2 \times L} \times t_{ON}(\theta) = \frac{ V_{AC}(\theta) }{R_{EQ1}}$	$I_{IN2}(\theta) = \frac{ V_{AC}(\theta) }{2 \times L} \times t_{ON}(\theta) \times D_C(\theta) = \frac{ V_{AC}(\theta) }{R_{EQ2}}$ $D_C(\theta) = \frac{t_{ON}(\theta) + t_{DMG}(\theta)}{t_{ON}(\theta) + t_{DMG}(\theta) + t_{DT}}$
Input Equivalent Impedance	$R_{EQ1} = \frac{2 \times L}{t_{ON}(\theta)}$	$R_{EQ2} = \frac{2 \times L}{t_{ON}(\theta) \times D_C(\theta)}$
Condition for PF = 1	$t_{ON}(\theta) = \varepsilon(\text{constant})$	$t_{ON}(\theta) \times D_C(\theta) = \varepsilon(\text{constant})$

A dedicated variable-on-time (VOT) control circuit is integrated and  $t_{ON}$  is calculated

# MP44018 Efficiency

## Efficiency Comparison



➤ Under light-load conditions, the MP44018's efficiency is significantly higher than previous generations





# HR1275 Key Features

## General System Features:

- Total < 85mW No-Load Power Loss (including PFC + LLC)
- HV Current Source for Start-Up
- Smart X-Capacitor Discharge when AC Dropout, Approved by IEC 62368 and IEC 60950
- Power Good (PG) Function
- External Over-Temperature Protection (OTP)
- UART Interface for Parameter Configuration
- User-Friendly GUI
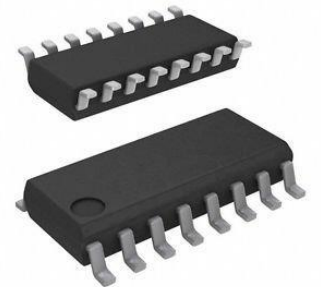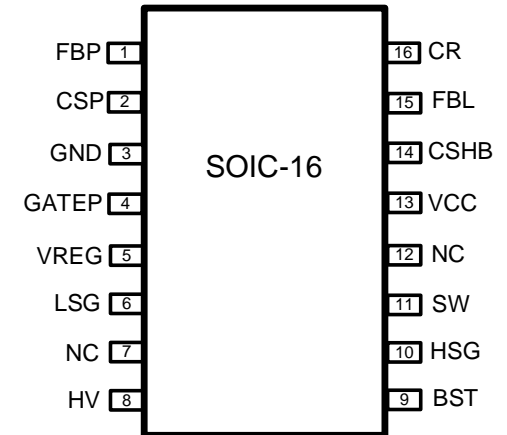
## PFC Controller:

- CrM/DCM Multi-Mode PFC Control with High Efficiency across Full Load Range
- Intelligent Valley Switching for Low Audible Noise
- Operates Up to 400kHz
- Input Capacitor Current Compensation
- THD Compensation
- Programmable Soft Burst-On for Higher Light-Load Efficiency with Low Audible Noise
- Programmable AC Input Brown-In/Brownout
- Cycle-by-Cycle Switching Current Limit
- Overload Protection (OLP), Over-Voltage Protection (OVP)




# HR1275 PFC Architecture

## Input Pins:

Pin	Descriptions
ACIN	AC input sense through an external divider resistor
ZCD	PFC valley & demagnetization time detect input. Connect to a PFC switch drain through a high-voltage capacitor
FBP	$V_{BUS}$ voltage sense through an external divider resistor
CSP	Current-limit protection



## Output Pins:

Pin	Descriptions
GATEP	PFC switch gate driver

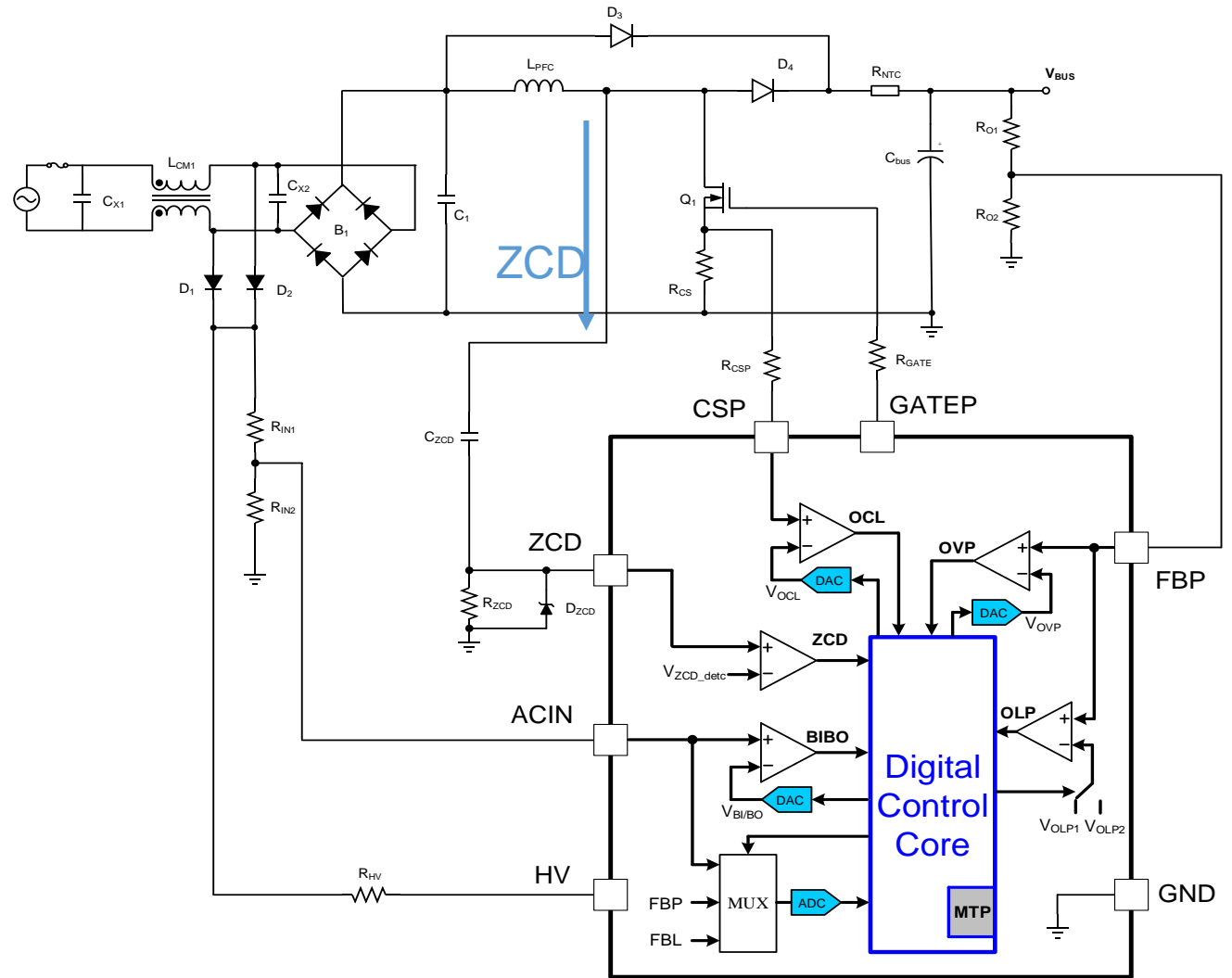



# HR1275 240W Performance

**BCM**  
High Load

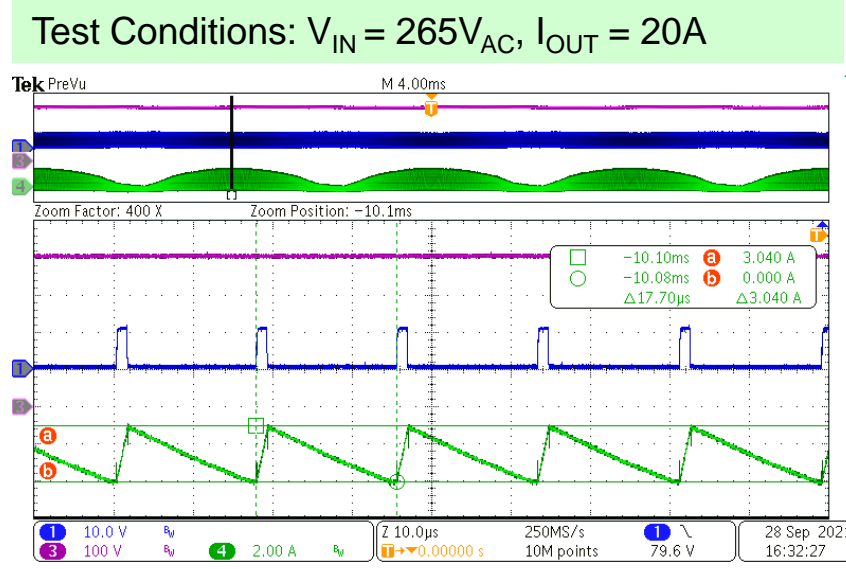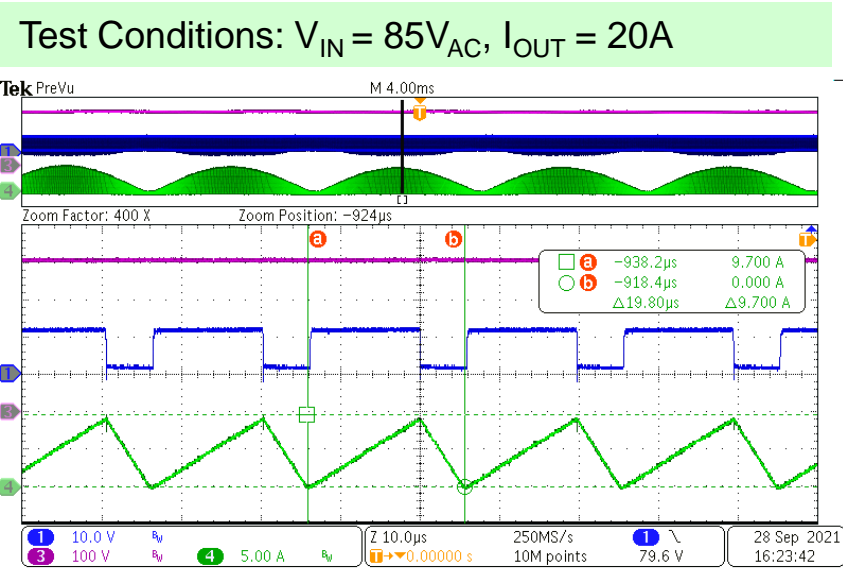

CH1: GATEP  
CH3:  $V_{BUS}$   
CH4:  $I_{PFC}$

**DCM**  
Light Load

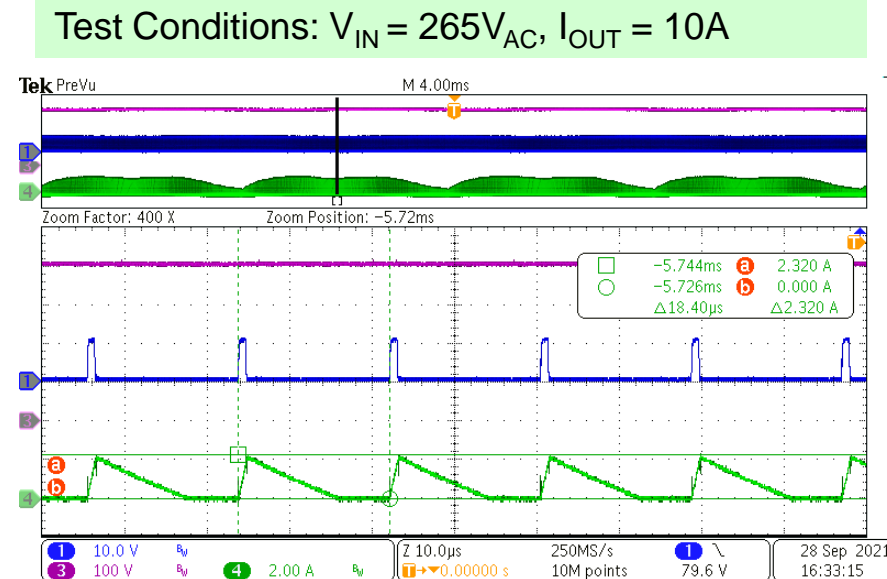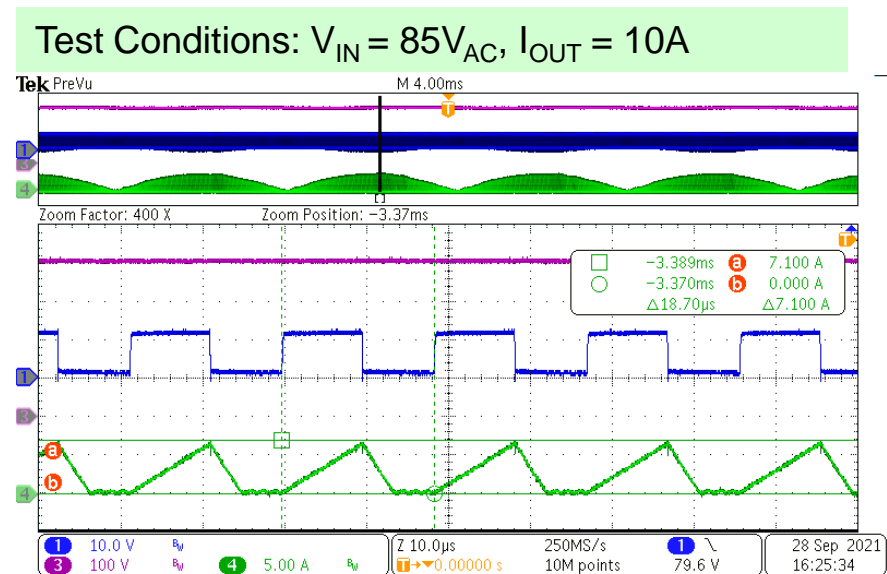


# HR121x Key Features

## System:


- **Pin < 100mW at No Load, 12V Output**
- High-Voltage Current Source for Start-Up and Smart X-Capacitor Discharger
- **Power Good (PG) Function**
- UART Interface and GUI for Parameters Configuration
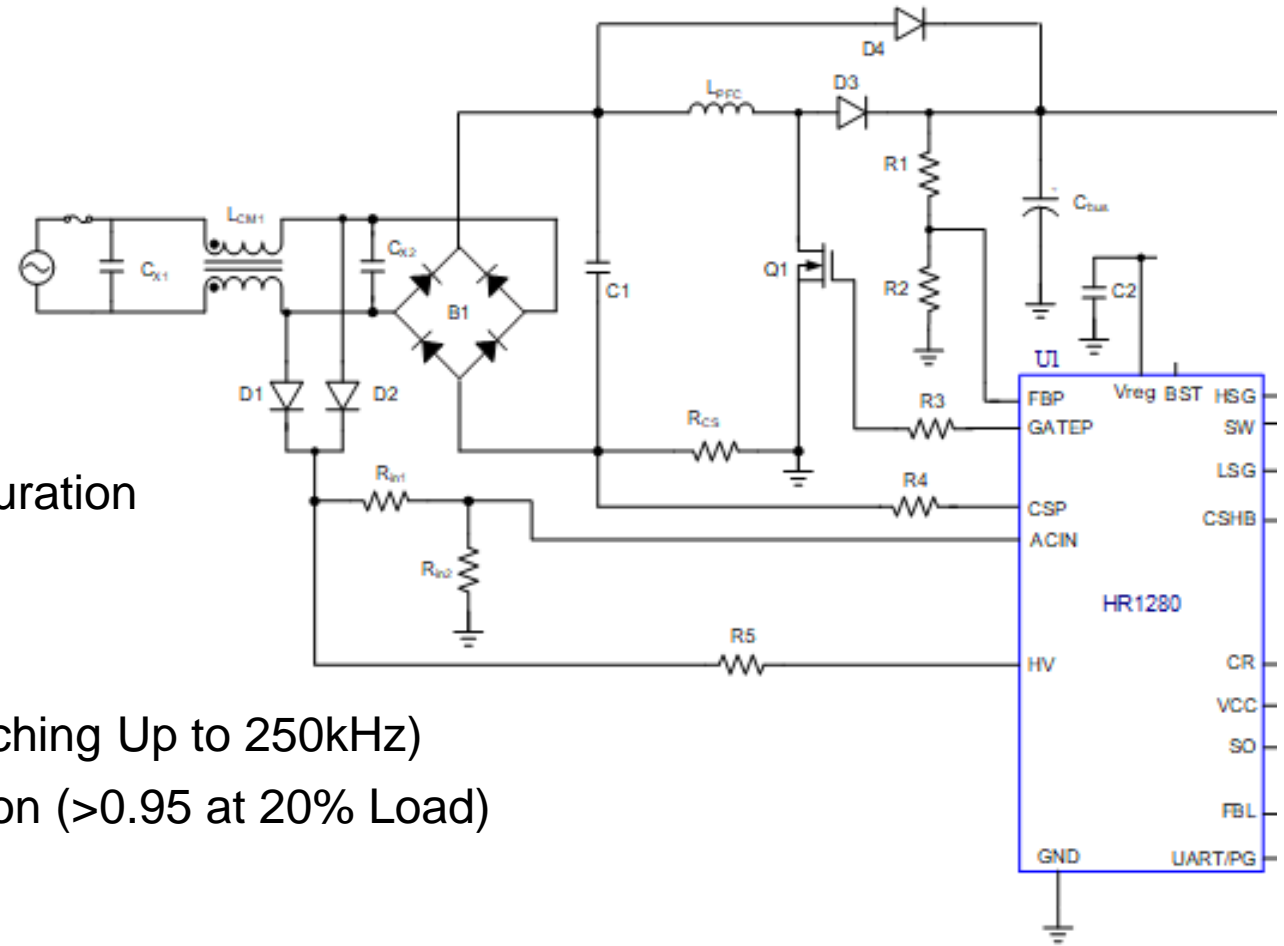
## PFC:

- **CCM/DCM Operation** of Digital PFC (Max Switching Up to 250kHz)
- High PF Due to Capacitor Current Compensation (>0.95 at 20% Load)
- Configurable Frequency Jitter to Improve EMI
- Configurable Soft Start
- Configurable Soft Burst On for Low Audible Noise
- Configurable AC Brown-In/Brownout, Overload Protection (OLP), Over-Voltage Protection (OVP), Over-Current Limit (OCL)




# HR121x PFC Control

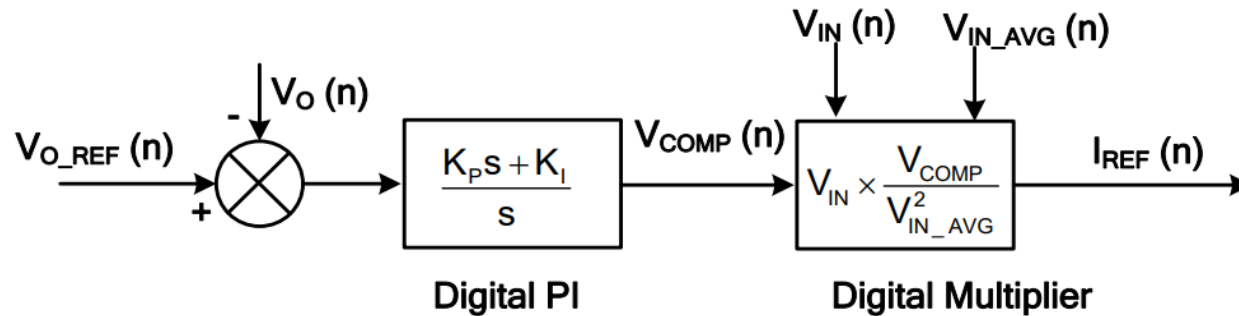
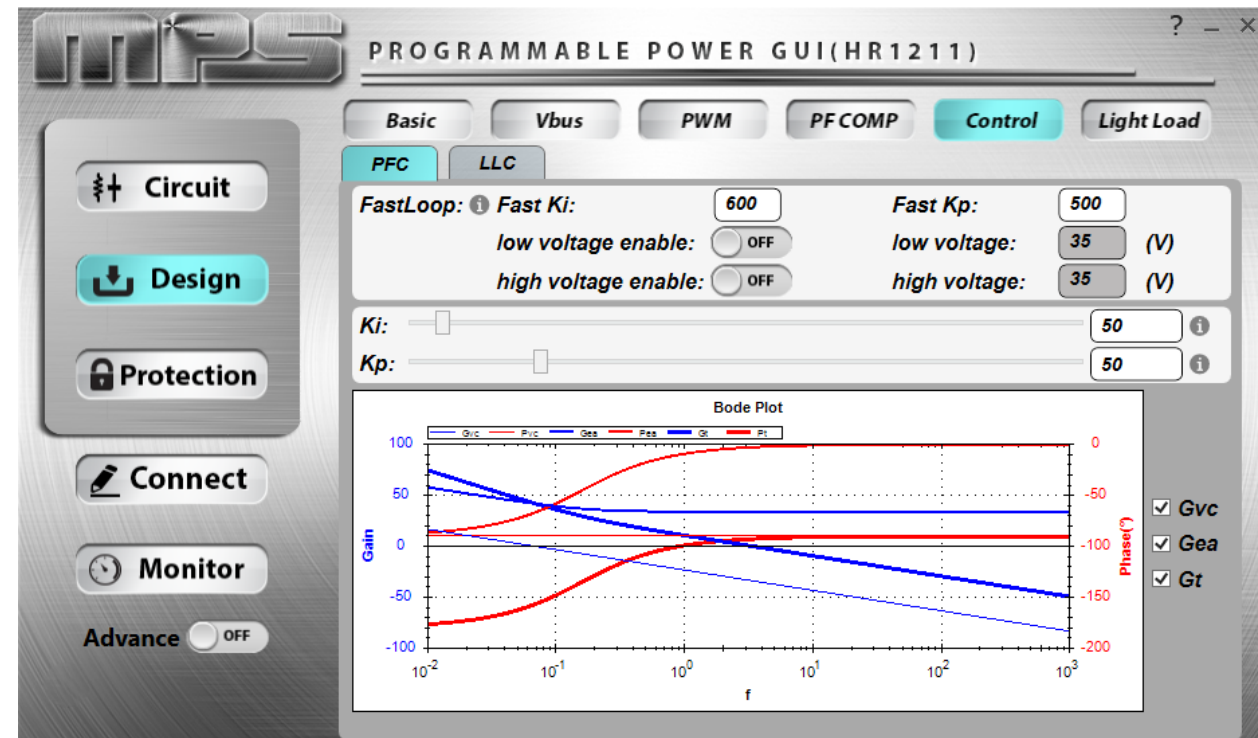
## PFC Patented Average Current Control:

- CCM for Heavy Loads
- DCM for Light Loads (Improved Efficiency)
- Digital PI Compensator
- PI Parameters Can Be Configured via the GUI
  - Directly on the Board
  - In Real Time




# Agenda

- Understanding Power Factor Correction
- MPS Solutions for PFCs
- **Understanding Resonant Power Conversion**
- MPS Solutions for LLCs
- Q&A

# Why Resonant Converters?

- When output power increases, classical and simpler structures become too inefficient




- Hard switching of power switches

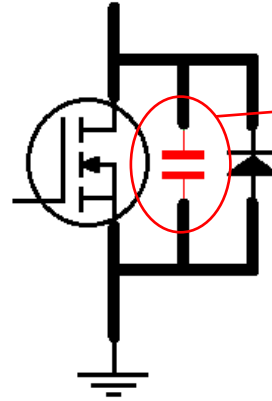

*When the switch is turned on while the parasitic capacitor is charged, losses can be high (scale up with switching frequency)*

→ **Zero-Voltage Switching (ZVS)**

- Reverse recovery time of diodes

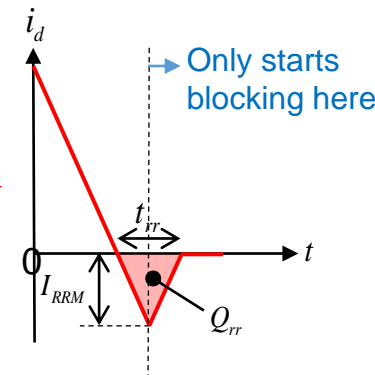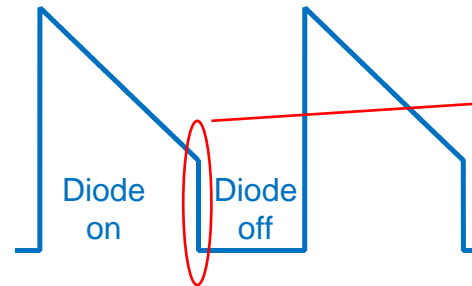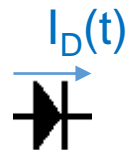


*Diodes do not start blocking voltage instantaneously when reversed*

→ **Zero-current Switching (ZCS)**

- Energy stored in transformers
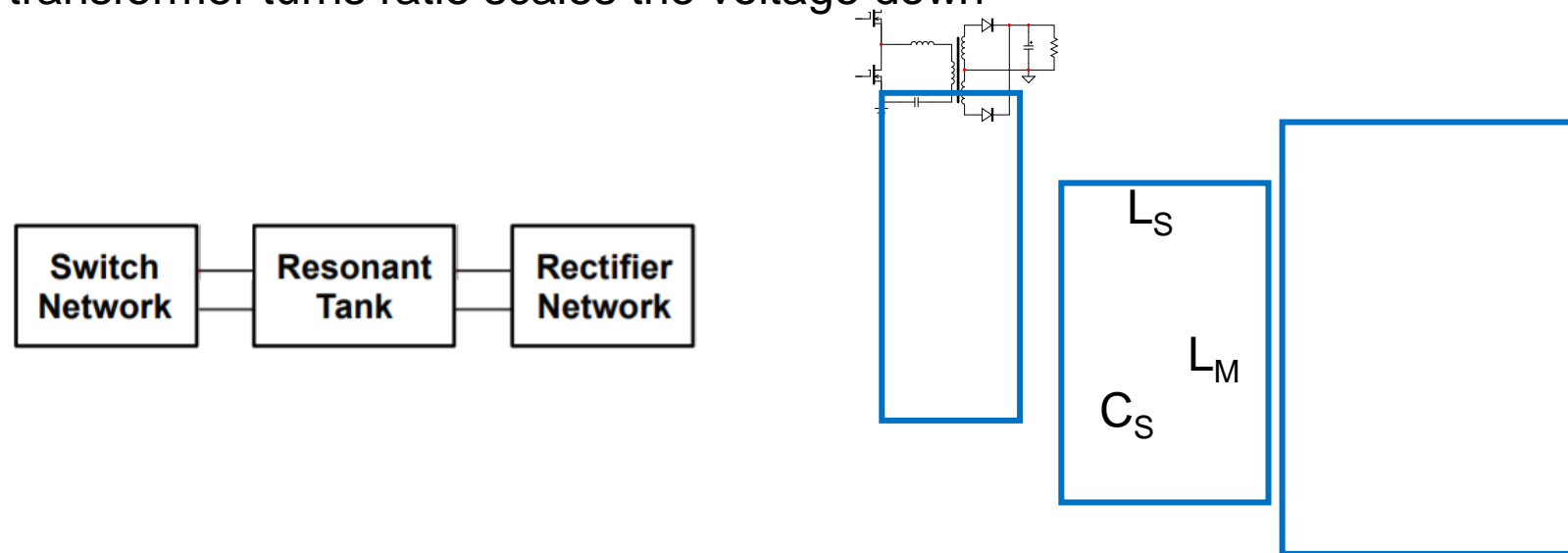
# What Is an LLC Resonant Converter?

- The LLC is a series resonant converter:
  - The magnetizing inductance ( $L_M$ ) of the transformer is one of the resonating elements
  - The leakage inductance ( $L_S$ ) of the transformer also participates in the resonance
  - Series capacitance ( $C_S$ ) is added to ensure the resonance
  - The transformer turns ratio scales the voltage down



The switching frequency controls the power transmitted to the output





# What Is an LLC Resonant Converter?

The LLC converter ensures soft switching under normal-load conditions:

- Zero-voltage switching (ZVS) for the power switches (primary side)
- Zero-current switching (ZCS) for the rectifying diodes (secondary side)

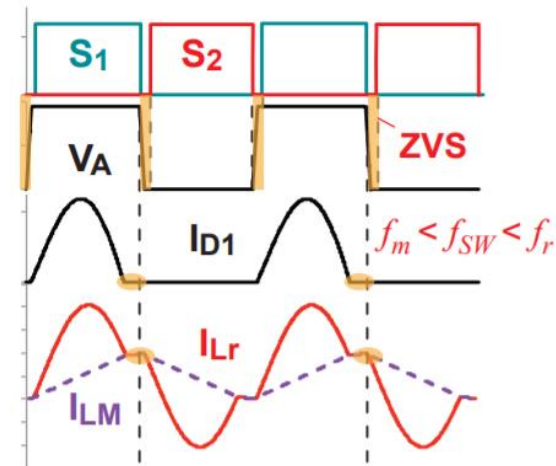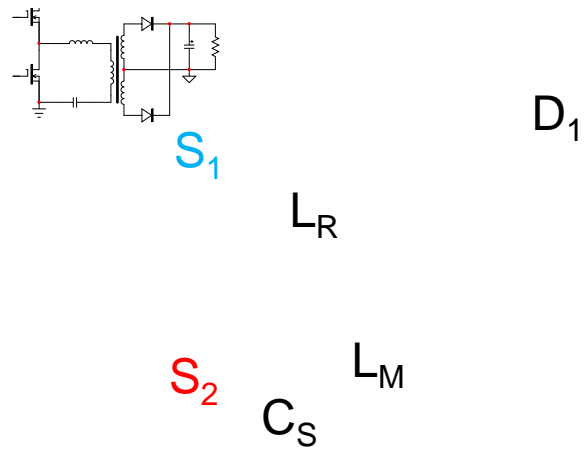It can operate at a high switching frequency to build compact converters





Limited component count + magnetics can be made compact (especially at high switching frequencies)

→ high power density
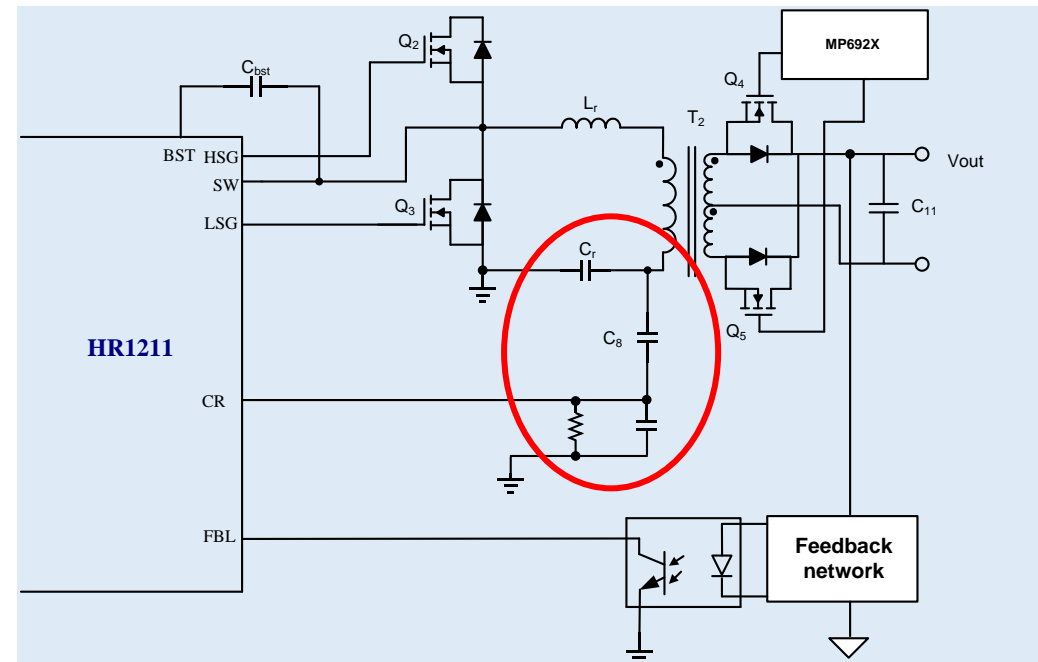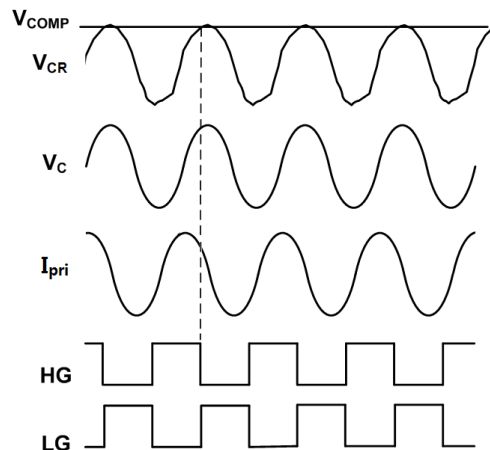
# Current-Mode LLC

- Controlling the frequency of the LLC to regulate the output leads to complicated loop compensation
- It can be made simpler by controlling the primary peak current cycle-by-cycle  
→ current-mode control
- By monitoring the voltage across the resonant capacitor, the controller has access to the current information


$$\Delta V_{C_r} = \frac{1}{C_r} \int i_{C_r}(t) \cdot dt$$


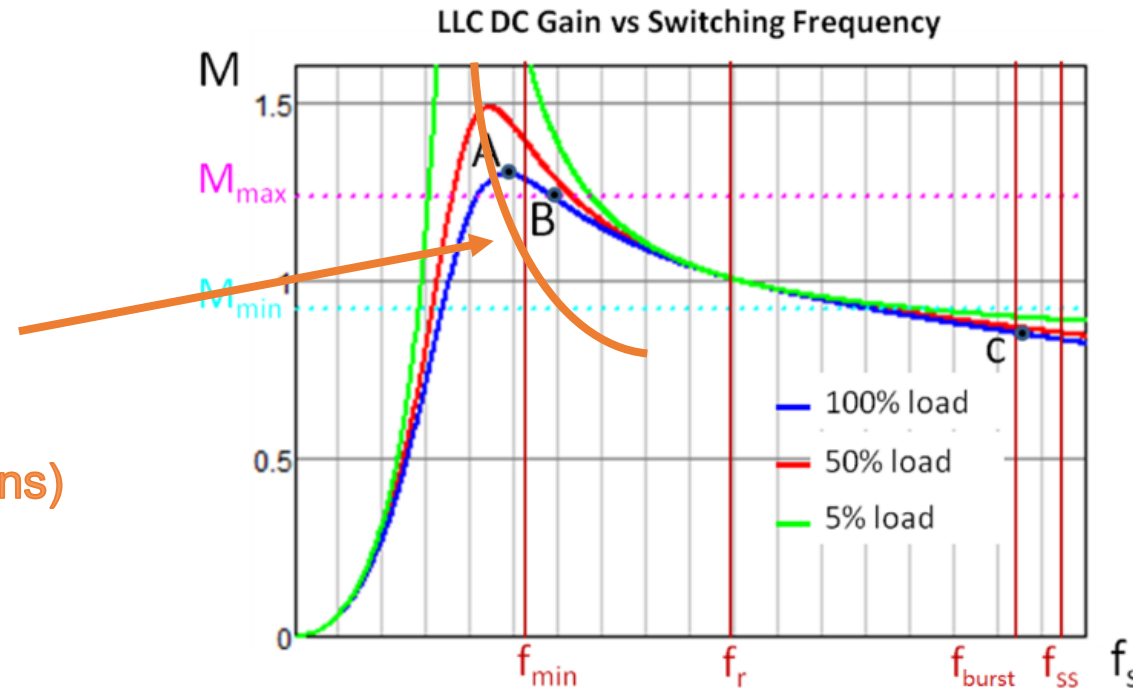
# Current-Mode LLC with Frequency Control

Based on first-harmonic approximation (FHA), the DC gain can be controlled by adjusting the switching frequency

The control law inverts itself below a certain frequency  
→ Avoid changing regions (capacitive vs. inductive regions)




Due to its limited DC gain range, the LLC converter does not easily accommodate large input and output voltage variations:

- Fits well with the PFC front-end stage (stable, constant input voltage for the LLC stage)
- Not adapted to all applications (better for constant voltage outputs)

# Agenda

- Understanding Power Factor Correction
- MPS Solutions for PFCs
- Understanding Resonant Power Conversion
- **MPS Solutions for LLCs**
- Q&A

# MPS LLC Controllers Roadmap

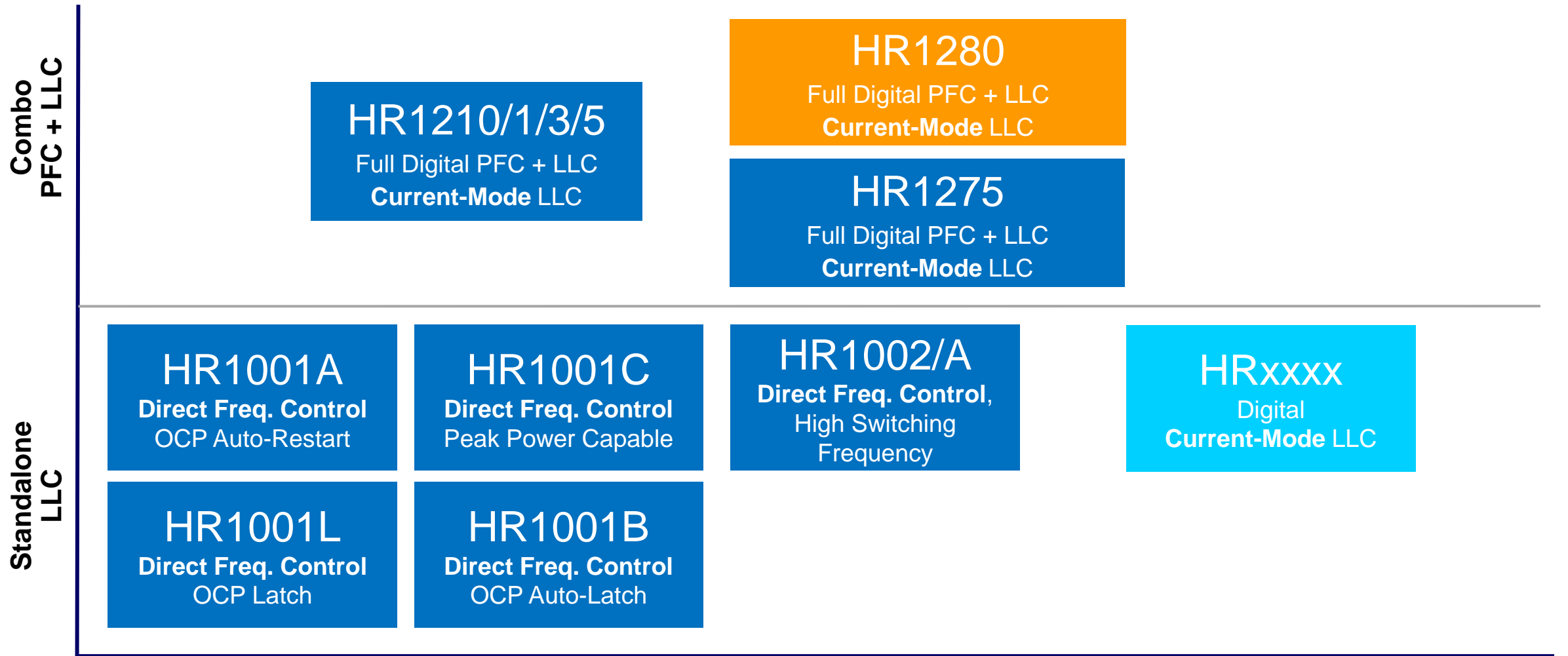


Released

Sampling

Under Design

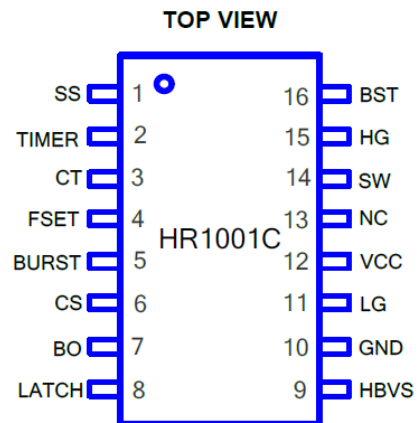
# HR1001C Key Features

- Adaptive Dead-Time Adjustment (ADTA)
- Over-Current Protection (OCP) with Configurable Delay Time for Enhanced Surge Performance
- Capacitive Mode Protection (CMP)
- 50% Duty Cycle, Variable Frequency Control for Resonant Half-Bridge Converter
- 600V High-Side Gate Driver with Integrated Bootstrap Diode



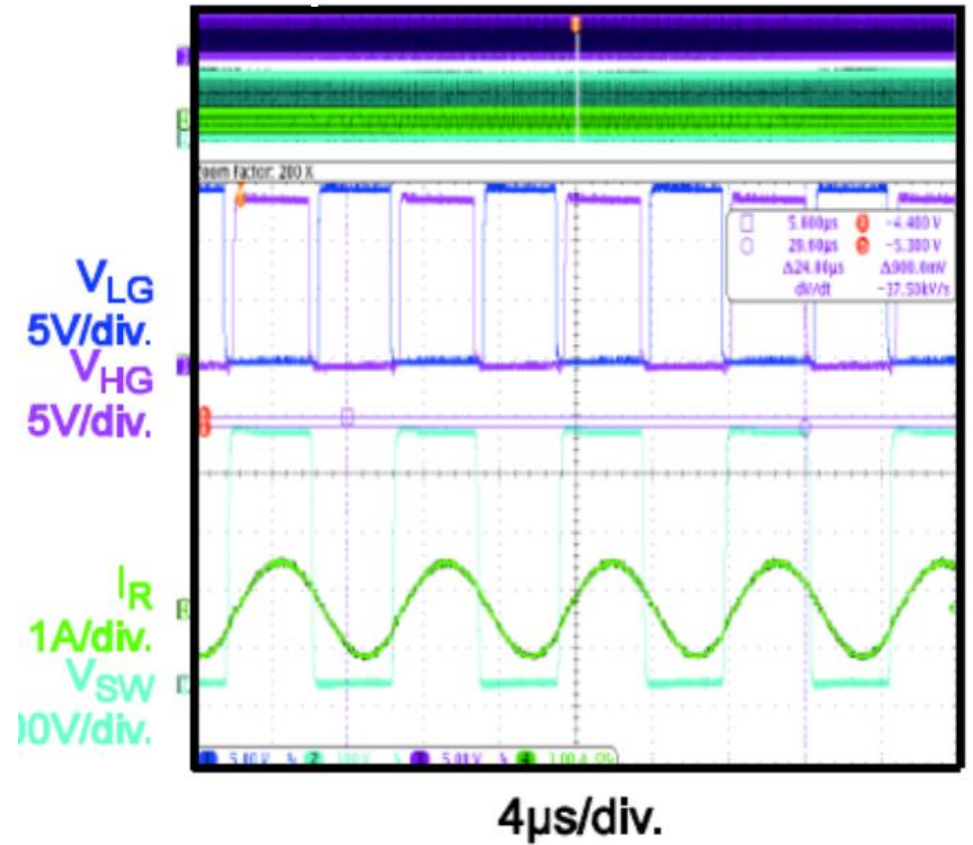
## Steady State

$V_{OUT}=24\text{ V}$ ,  $I_{OUT}=4.16\text{ A}$



# HR1001C Adaptive Dead Time

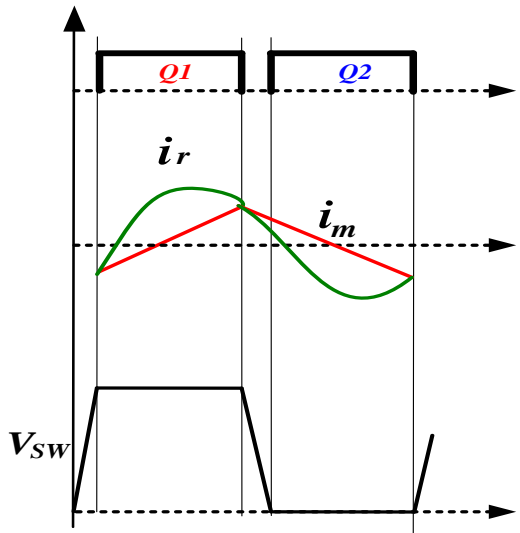


Soft switching at normal

- Low Efficiency
- Thermal Problems
- Higher Cost


$f_{sw}$  increases at light loads

$L_M$  Tolerance

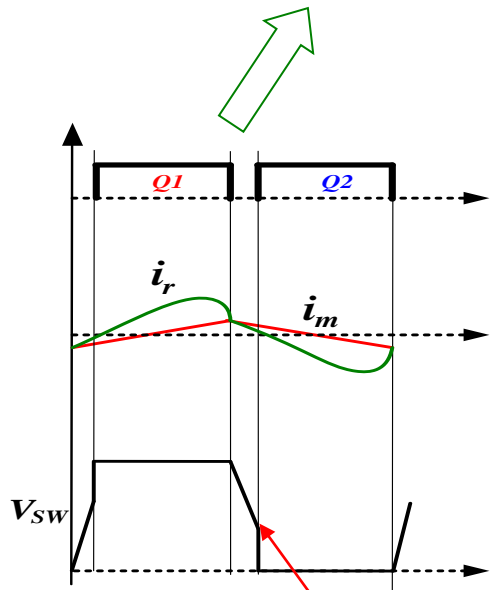

Hard Switching!

ADTA Block Diagram

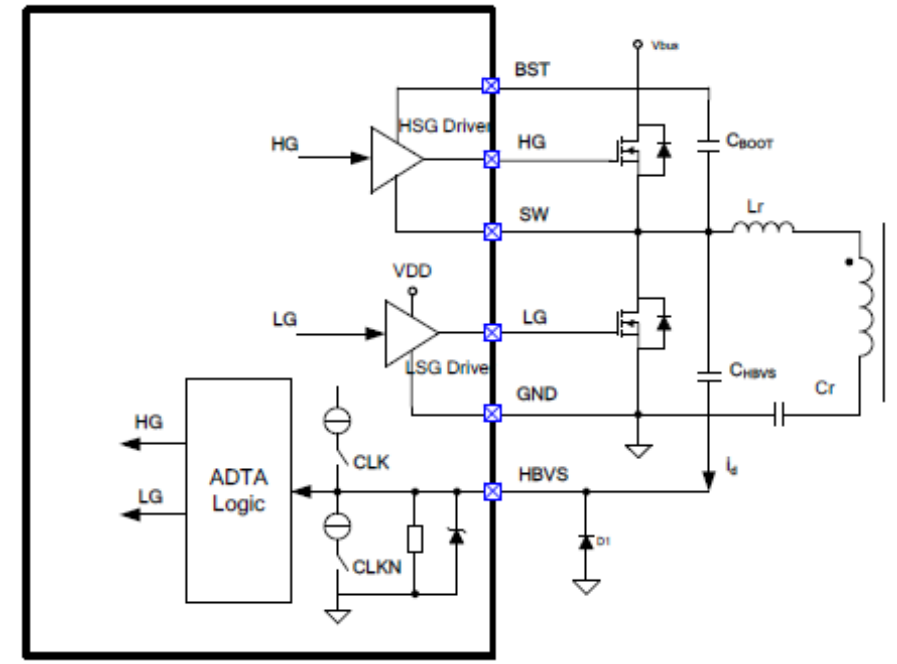

Adaptive dead time adjustment automatically ensures ZVS even under light-load conditions

→ High efficiency and low cost can be achieved with any MOSFET





# HR1275 LLC Key Features

## General System Features

- Total <85mW No-Load Power Loss
- HV Current Source for Start-Up
- Smart X-Capacitor Discharge during AC Dropout, Approved by IEC 62368 and IEC 60950
- Power Good (PG) Function
- External Over-Temperature Protection (OTP)
- UART Interface for Parameter Configuration
- User-Friendly GUI
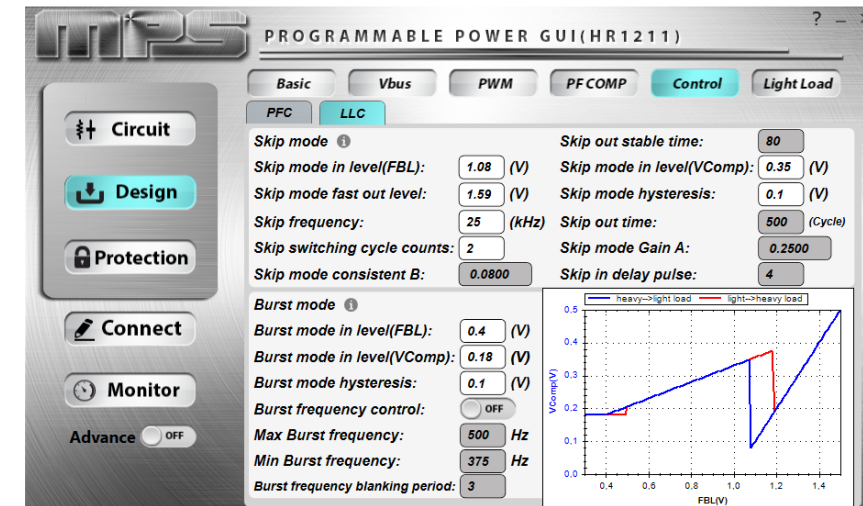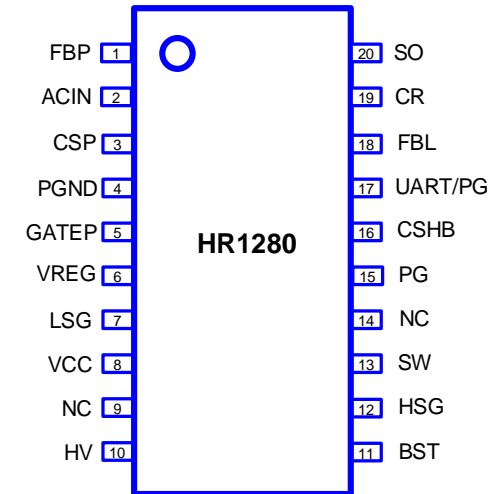
## LLC Controller


- Current Mode Control
- Precise Entry/Exit Skip/Burst Mode Control
- Adaptive Dead-Time Adjustment (ADTA) of HB LLC with Minimum and Maximum Limit
- Capacitive Mode Protection
- Operates Up to 500kHz
- Over-Current Protection (OCP) and Over-Power Protection (OPP) with Configurable Protection Behaviors





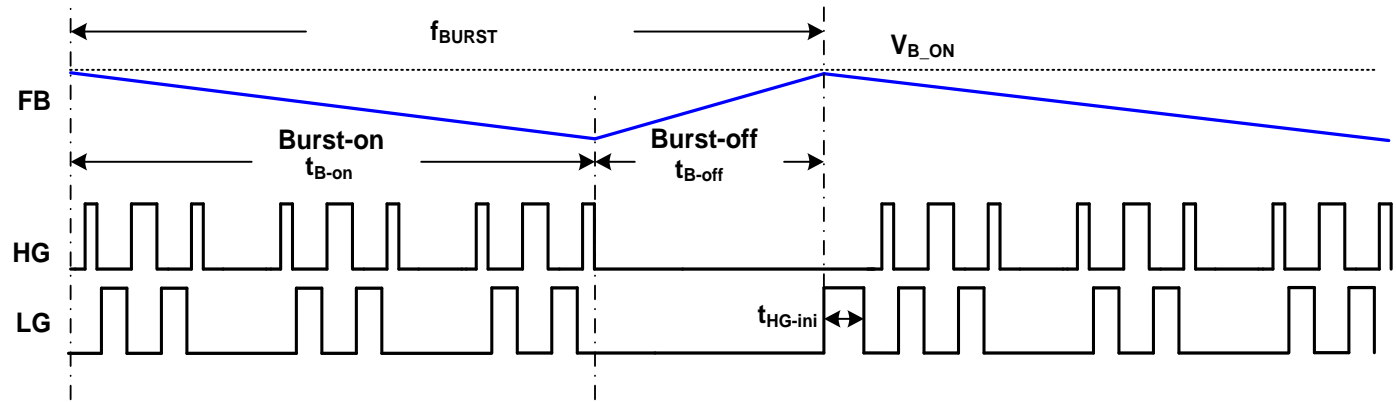
# HR1275 LLC Light-Load Burst Mode

- Configurable Fixed  $V_{COMP}$
- Configurable  $t_{H1}$  and  $t_{L1}$
- Configurable Skip Frequency
- PWM On/Off Based on the FBL Voltage:  
Burst-On/Off Level
- Burst Frequency Control
- FBL Pull-Up Resistor Control for Power Saving



## Operation Current in Burst Mode:


PN	HR1275	HR1280	HR1211
IC Consumption	1.2mA	1.3mA	2.2mA

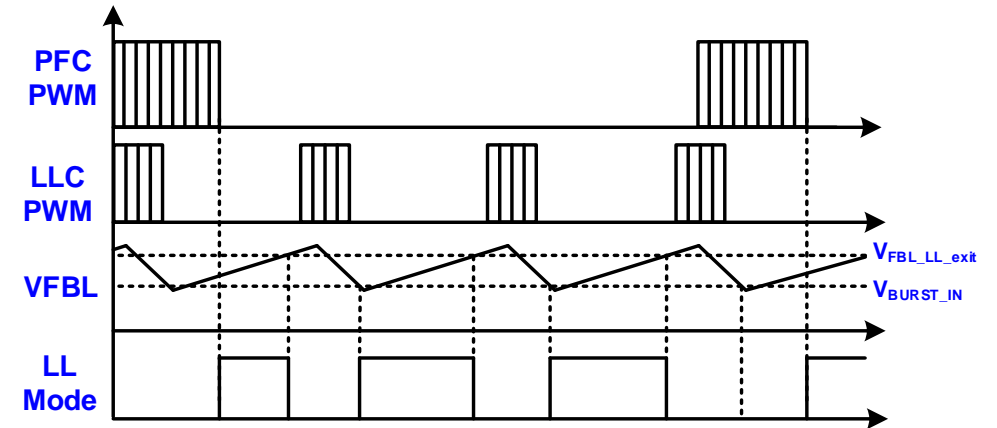

## HR1275 No-Load Standby Power:

$V_{IN}$	85V <sub>AC</sub>	115V <sub>AC</sub>	230V <sub>AC</sub>	265V <sub>AC</sub>
No Load Consumption (mW)	73.9	75.1	82.2	84.8

# HR12xx Start-Up Strategy

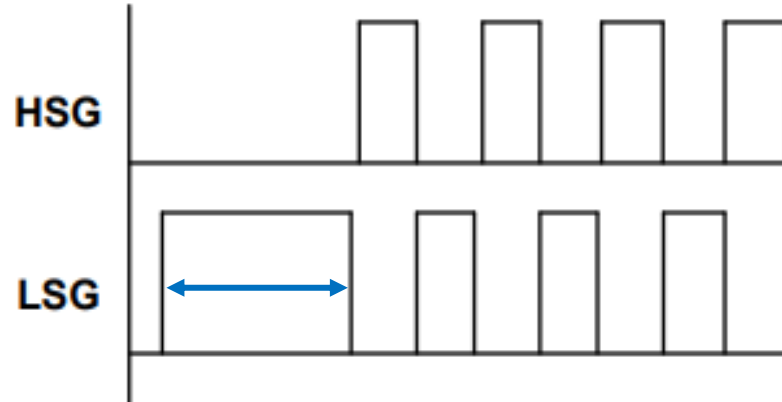


## Start-Up:

- The low-side gate (LSG) turns on first to charge the BST capacitor
- Then, the high-side gate (HSG) and LSG turn on and off alternatively
- Soft start is achieved by starting with a high switching frequency, then reducing it until the feedback (FB) loop takes over
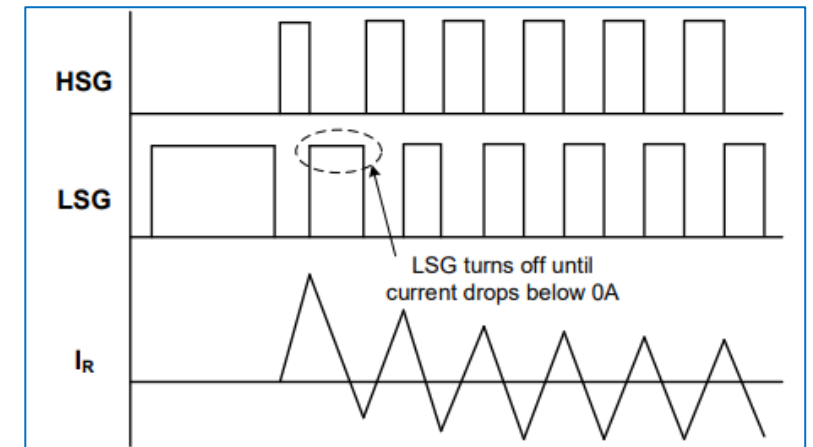
## Note:


- The first LSG pulse duration can be configured by the GUI

- During start-up, there is an imbalance in the resonant capacitor voltage, which can induce hard switching
- To avoid hard switching, the LSG driver does not turn off until the resonant tank current drops below zero ( $V_{CSHB} < V_{CSNR}$ )



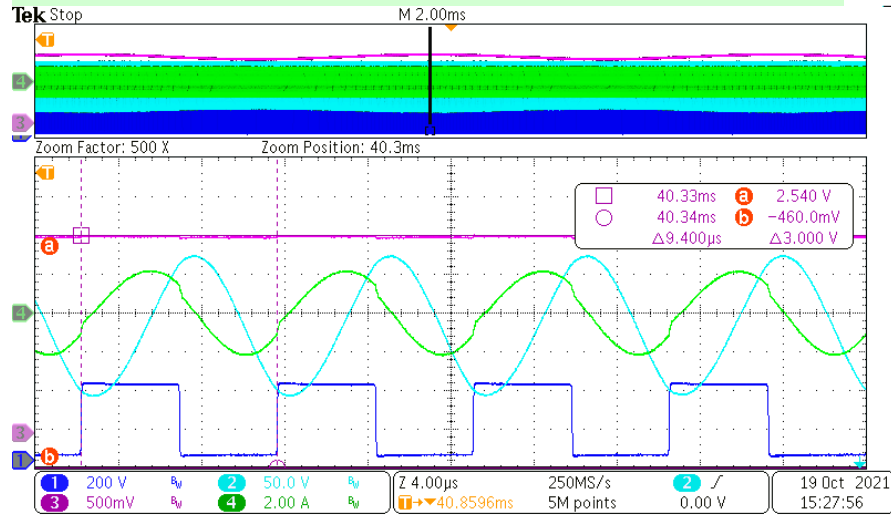
# HR1275 LLC Waveforms


Test Conditions:  $V_{IN} = 220V_{AC}$ ,  $I_{OUT} = 20A$



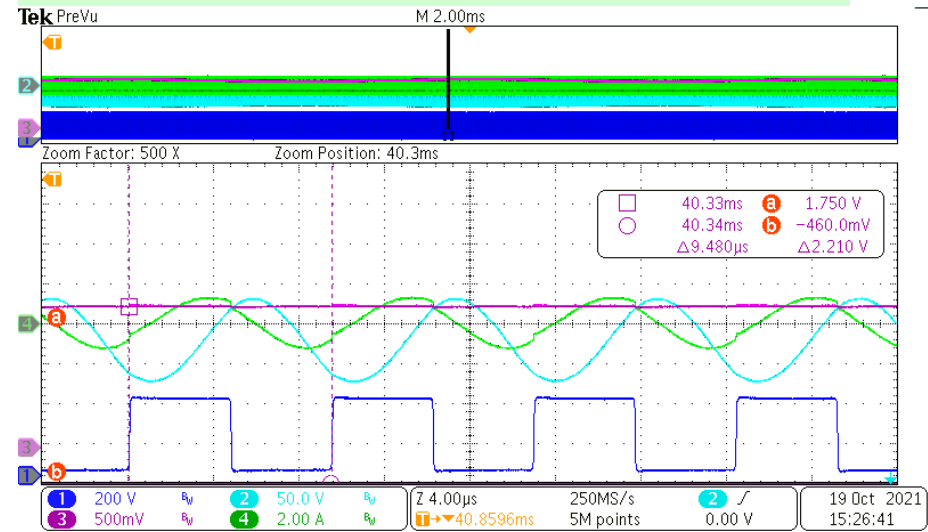
Test Conditions:  $V_{IN} = 220V_{AC}$ ,  $I_{OUT} = 10A$



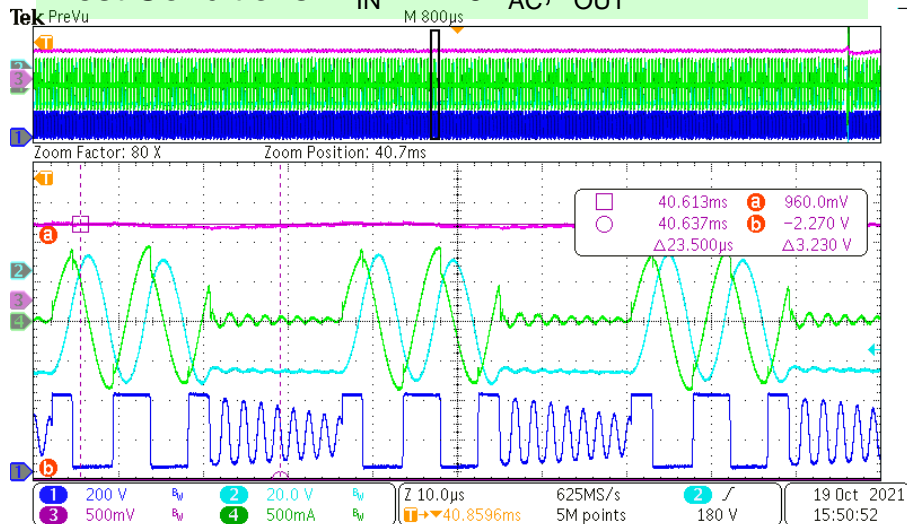Test Conditions:  $V_{IN} = 220V_{AC}$ ,  $I_{OUT} = 2A$



Test Conditions:  $V_{IN} = 220V_{AC}$ ,  $I_{OUT} = 1A$

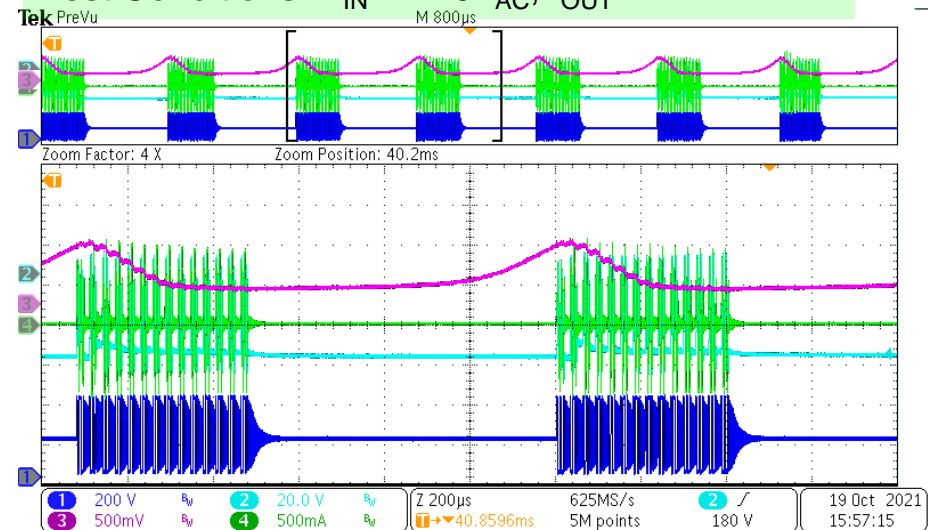

CH1: SW  
 CH2:  $V_{CR}$   
 CH3: FBL  
 CH4:  $I_R$



High Load

Burst  
 Light Load

# MPS LLC Design Tool

## LLC Design Tool

### MPS LLC Tool


The MPS LLC Tool will help you to define a value for the resonant tank (formed by  $L_r$ ,  $C_r$  and  $L_m$ ) to ensure that the converter is working on the quasi resonant region achieving soft switching. The tool will suggest a design solution depending on the Input-Output specification but the user can modify the key parameters.

LLC converters are becoming more and more famous because of their ability to achieve high power densities with low losses. This behaviour is achieved by means of soft switching techniques. The one most commonly used in this type of converter is zero voltage switching (ZVS). What the designer must guarantee is that once the transistor switches, the voltage of the drain source ( $V_{ds}$ ) must be close to zero. Then the switching losses (known as the product of  $V_{ds}$  by the transistor current) are drastically reduced. Obtaining this scenario within all input-output conditions is not an easy task. MPS with this tool wants to speed up the design process of this type of converters.



Tutorial

How to use the tool ▾

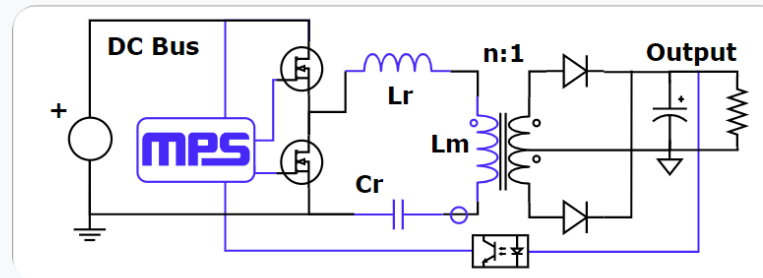

### Specifications

Define your input and output circuit specifications:

Input		Output	
Minimum Voltage [V]	Maximum Voltage [V]	Voltage [V]	Overload [%]
<input type="text" value="360"/>	<input type="text" value="410"/>	<input type="text" value="12"/>	<input type="text" value="10"/>
Typical Voltage [V]	Resonance Frequency [kHz]	Current [A]	Auxiliary Power [W]
<input type="text" value="380"/>	<input type="text" value="100"/>	<input type="text" value="55"/>	<input type="text"/>

Peak Mg

Specifications

<https://www.monolithicpower.com/en/design-tools/design-tools/llc-design-tool.html>



# MPS LLC SR Controllers Roadmap

## Dual Synchronous Rectification (SR) Controllers for LLC

LLC SR Driver

MP6922A  
30mV  $V_{DS}$   
Dual SR

MP6923  
15mV  $V_{DS}$   
Dual SR

MP6922  
70mV  $V_{DS}$   
Dual SR

MP6925/A  
High-Efficiency Dual SR

MP6926  
High-Frequency  
LLC SR

MP6928A  
Fast Turn-Off, Intelligent  
Dual SR

- Target to high power density PD markets



Released

Sampling



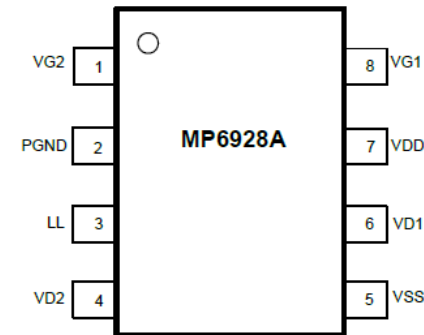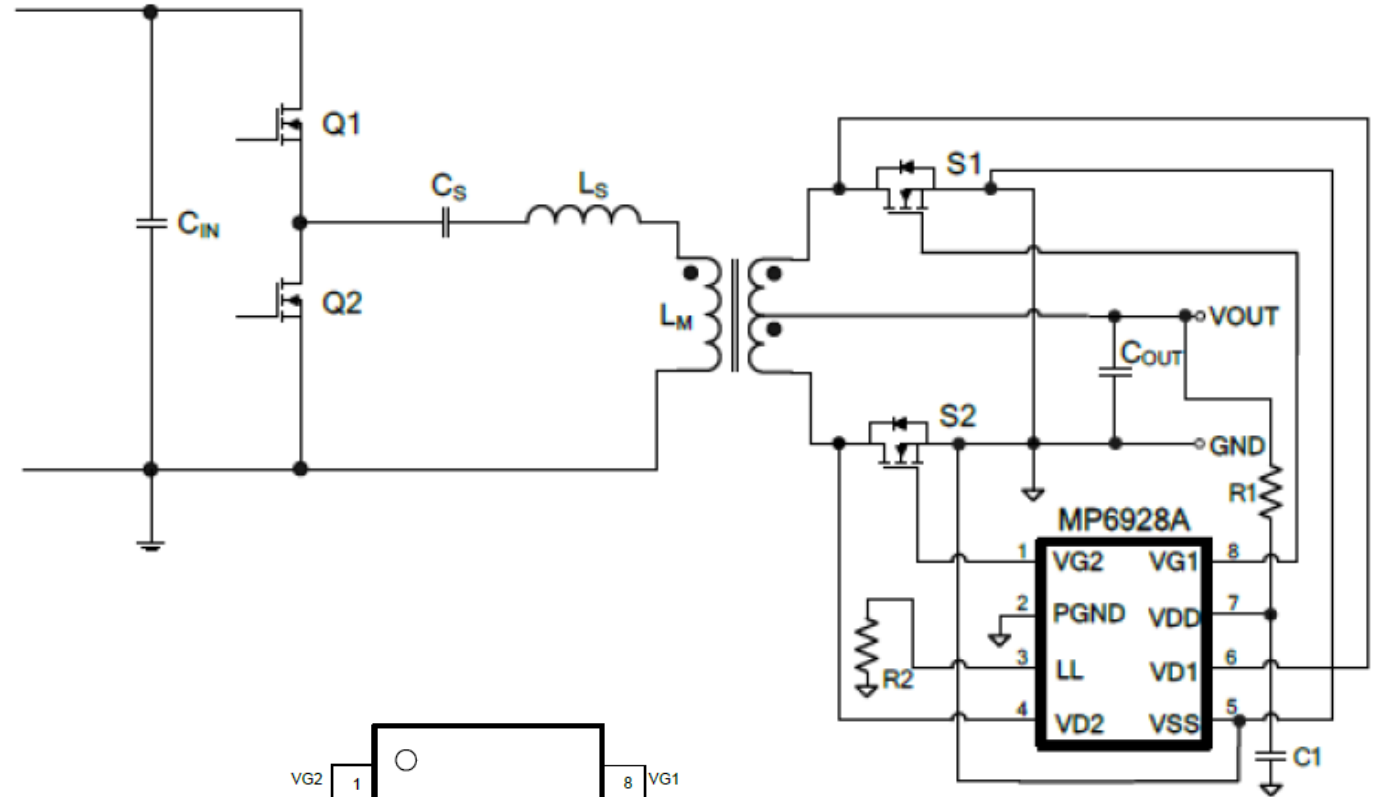
# MP6928A Key Features

- Works with 12V Standard and 5V Logic-Level FETS
- Fast Turn-Off Total Delay
- 4.3V to 35V Wide  $V_{DD}$  Operating Range
- Tolerant to 200V Drain-to-Source Voltage
- <math>150\mu\text{A}</math> Quiescent Current ( $I_Q$ )
- Supports High-Side and Low-Side Rectification



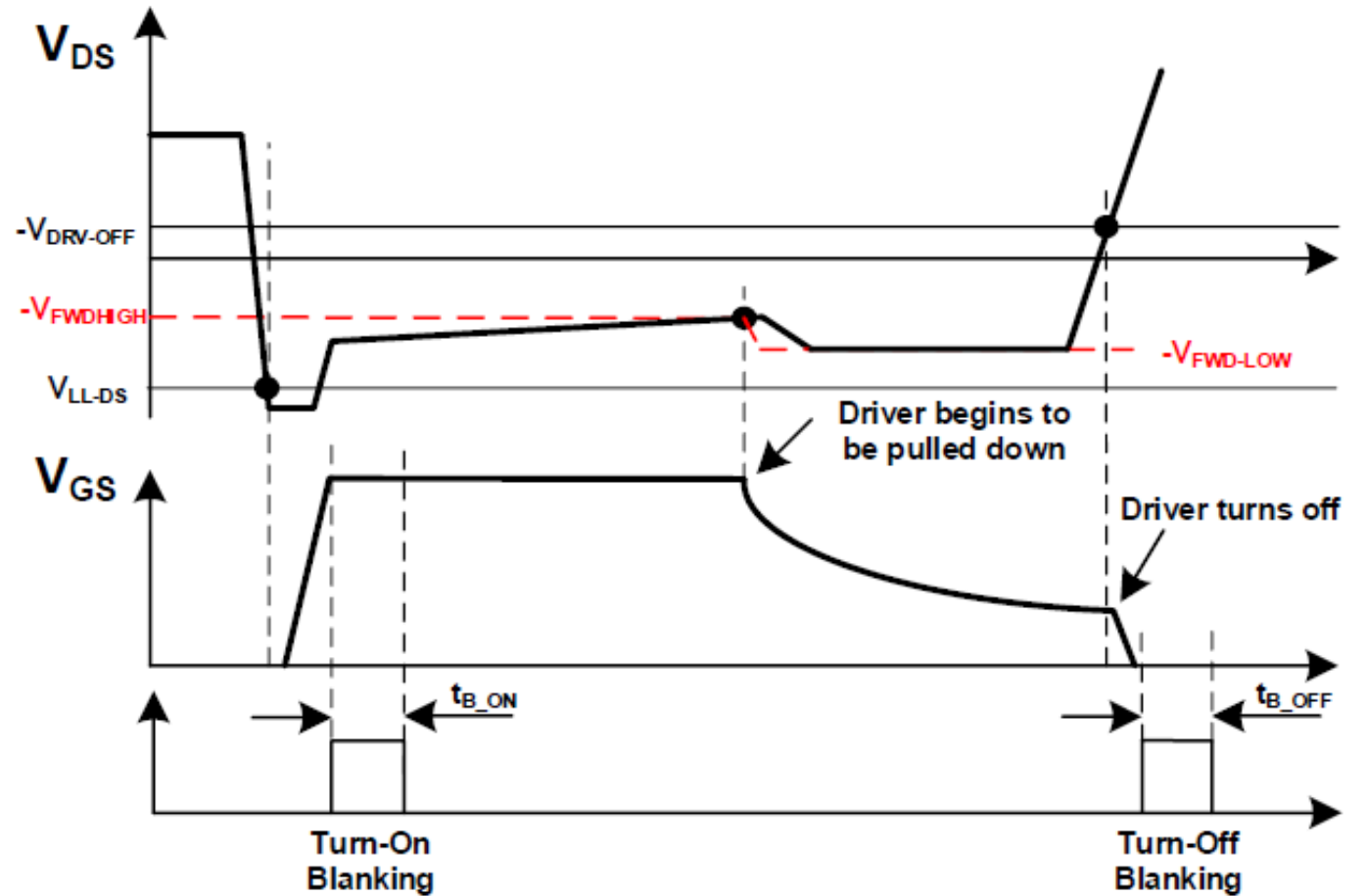
# MP6928A Adaptive Forward Voltage

- Fast Turn-Off Speed (About 35ns)
- Supports CCM, DCM, and BCM Modes
- Light-Load Function to Latch Off the Gate Driver under Light-load Conditions, Limiting the Current to 85 $\mu$ A
- Drives two N-channel MOSFETs, Adaptive Forward Voltage Drop Regulation



# HR1211 Reference Design Examples

## USB PD 3.1 240W

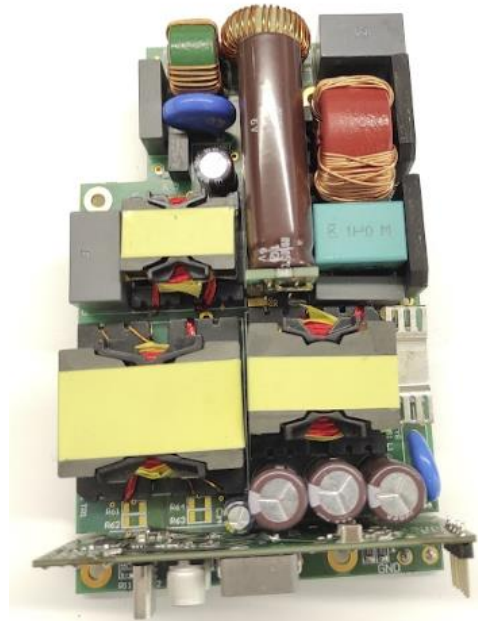

Parameter	Specifications
Input Voltage Range	100V <sub>AC</sub> to 265V <sub>AC</sub>
Output Voltage Range	3.3V <sub>DC</sub> to 48V <sub>DC</sub>
Output Current	Up to 5A
Efficiency	>94%
Power Factor	>98%
Conducted Emissions	Meets Class-B EN55032 Standards

## 600W Battery Charger



Parameter	Specifications
Input Voltage Range	85V <sub>AC</sub> to 265V <sub>AC</sub>
Output Voltage Range	35V <sub>DC</sub> to 58.8V <sub>DC</sub> (±1.5%)
Output Current	10A (±1.5%)
Efficiency	>92%
Power Factor	>98%
Conducted Emissions	Meets Class-B EN55032 Standards



# Agenda

- Understanding Power Factor Correction
- MPS Solutions for PFCs
- Understanding Resonant Power Conversion
- MPS Solutions for LLCs
- Q&A

**Thank you!**

[monolithicpower.com](https://monolithicpower.com)